



**EC/EE/CS & IT/IN**

**Digital Electronics**

**Combinational  
Circuit**

**MULTIPLEXER**



**LECTURE NO. 4**

**Chandan Jha Sir (CJ Sir)**

बिना संघर्ष कोई महान नहीं होता  
बिना कुछ किये जय जय कार नहीं होता  
जब तक नहीं पड़ती हथोड़े की चोट  
तब तक कोई पत्थर भी  
लोगों के लिए भगवान नहीं होता



## ABOUT ME



- **Cleared Gate Multiple times with double Digit Rank (AIR 23, AIR 26)**
- **Qualified ISRO Exam**
- **Mentored More then 1 Lakhs+ Students (Offline & Online)**
- **More then 250+ Motivational Seminar in various Engineering College including NITs & Some of IITs**



**Chandan Jha**

## DON'T CARE CONDITION

Combination of inputs on which the output may or may not depends are called don't care condition.

Sunday → 6:00 PM.  
Evening



**Ex. 9.** Find the minimized Boolean expression for the function given as  
 $f(A, B, C) = \sum m(0, 2, 3, 4) + \sum d(1, 6, 7)$

A \ BC					
		00	01	11	10
0	0	1	x	1	1
	1	1		x	x

**Ex. 10.** Find the minimized Boolean expression for the function given as  
 $f(A, B, C, D) = \sum m (0, 2, 4, 6, 7, 8, 10, 11, 12, 14, 15) + \sum d(1,3)$

$AB \backslash CD$	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	1	X	X	1
$\bar{A}B$ 01	1		1	1
$AB$ 11	1		1	1
$A\bar{B}$ 10	1		1	1

$C + \bar{D}$

Ans



**Ex. 11** Find the minimized Boolean expression for the function given as  $f(A, B, C, D) = \sum m(0, 3, 6, 7, 9, 14) + \sum d(1, 4, 5, 11, 13, 15)$

AB \ CD				
	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	1	X	1	
$\bar{A}B$ 01	X	X	1	1
$AB$ 11		X	X	1*
$A\bar{B}$ 10		1*	X	

BC

$\bar{A}\bar{C} + BC + W$

Ans

Product of Sum

POS FORM Question



Ex. 12. Find the minimized Boolean expression for the function given as  
 $f(A, B, C) = \pi M(0, 2, 3, 4, 6, 7)$

Method-①

POS

		BC			
		$B+C$ $\bar{B}\bar{C}$ 00	$B+\bar{C}$ $\bar{B}C$ 01	$\bar{B}+C$ $B\bar{C}$ 11	$\bar{B}+\bar{C}$ $BC$ 10
A	$\bar{A}$	0			
A	A	1			

C (points to  $\bar{B}\bar{C}$  and  $B\bar{C}$ )  
B (points to  $\bar{B}C$  and  $BC$ )

$\bar{B} \cdot C$

Method ②

		BC			
		$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$B\bar{C}$ 11	$BC$ 10
A	$\bar{A}$	0			
A	A	1			

C (points to  $\bar{B}\bar{C}$  and  $B\bar{C}$ )  
B (points to  $\bar{B}C$  and  $BC$ )

$\bar{F} = \bar{C} + B$

$F = \overline{\bar{C} + B} = \bar{\bar{C}} \cdot \bar{B} = B \cdot C$

Ans

$$f(A, B, C) = \prod M(0, 2, 3, 4, 6, 7) \rightarrow \text{POS.}$$

$$= \sum m(1, 5)$$

$A \backslash BC$					
		$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
$\bar{A}$	0	0	1	0	0
$A$	1	0	1	0	0

$\bar{B}C$   
=


$A\bar{B}C$   
=





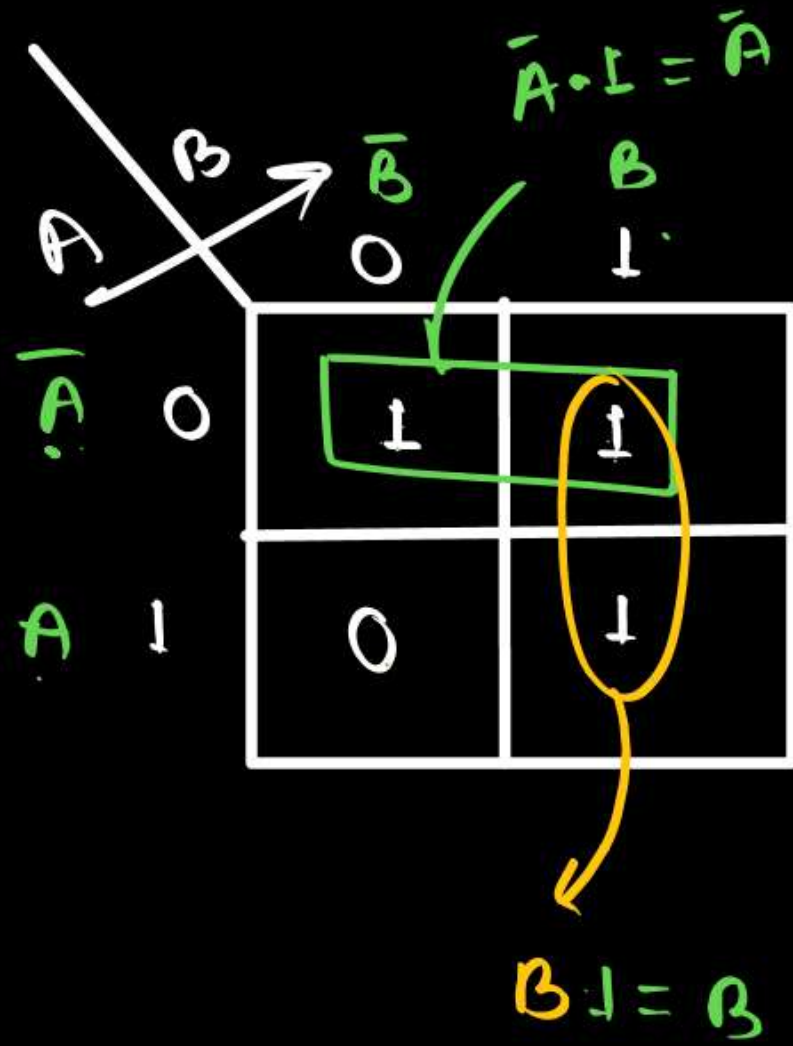
$$(\bar{A} + \bar{B} + \bar{D}) \cdot (\bar{A} + \bar{C}) \cdot (A + C + D) \cdot (B + D) \cdot (C + \bar{D})$$





$$f(A, B) = \bar{A}\bar{B} \cdot 1 + \bar{A}B \cdot 1 + A\bar{B} \cdot 0 + AB \cdot 1$$

$$= \sum m(0, 1, 3)$$

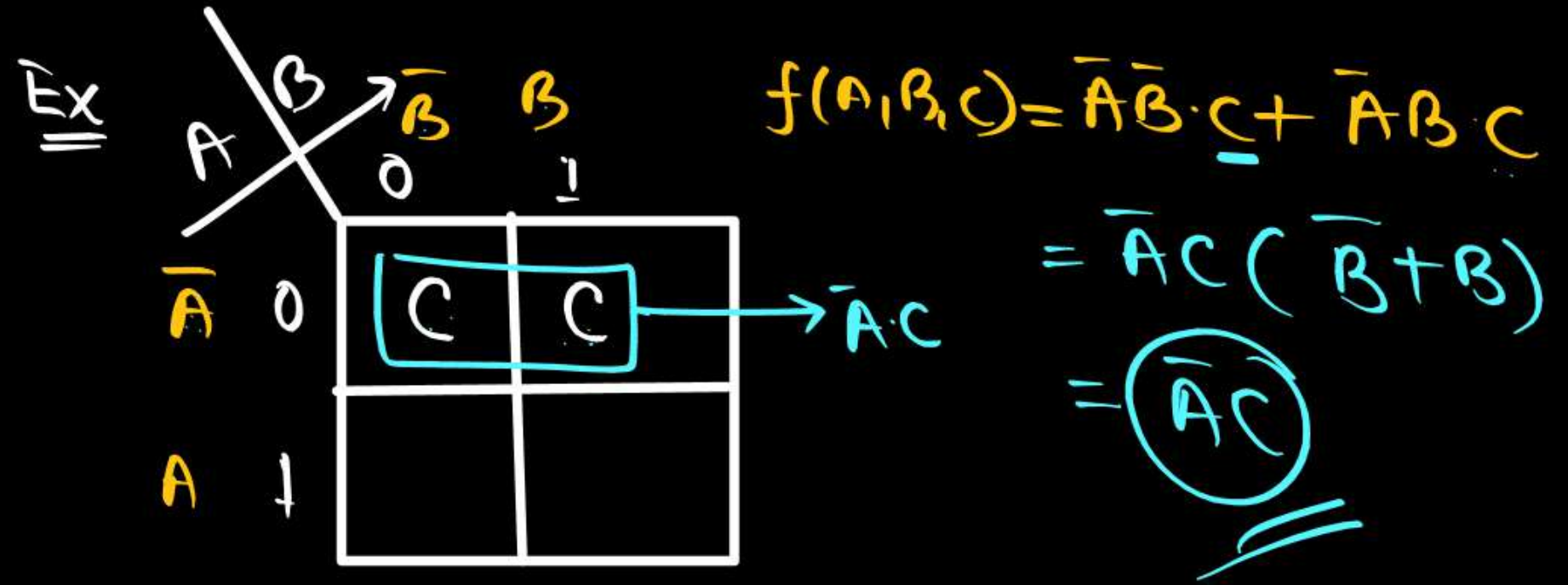

$\bar{A}C$   
 And

		BC			
		$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
A	$\bar{A}$ 0	1	1		
	A 1			1	1

→ standard canonical

$$Q \quad f(A, B, C, D) = \bar{A}\bar{B}\bar{C} \cdot 1 + \bar{A}\bar{B}C \cdot 1 + ABCD + AB\bar{C}\bar{D}$$

$$f(A, B, C, D) = \bar{A}\bar{B}\bar{C}(\bar{D} + D) + \bar{A}\bar{B}C(\bar{D} + D)$$

$$+ ABCD + AB\bar{C}\bar{D}$$

$$= \overset{0000}{\bar{A}\bar{B}\bar{C}\bar{D}} + \overset{0001}{\bar{A}\bar{B}\bar{C}D} + \overset{0010}{\bar{A}\bar{B}C\bar{D}} + \overset{0011}{\bar{A}\bar{B}CD} + \overset{1100}{AB\bar{C}\bar{D}} + \overset{1101}{ABCD}$$

$$= \sum m(0, 1, 2, 3, 13, 15)$$

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 13, 15)$$

$AB \backslash CD$					
		$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$	00	1	1	1	1
$\bar{A}B$	01				
$AB$	11		1	1	
$A\bar{B}$	10				

$\bar{A}\bar{B}$

$ABD$

$$= \bar{A}\bar{B} + ABD$$

Ans



$\overline{A}\overline{B} \cdot 1$   
 $A \cdot 1$

$A \backslash BC$	$\overline{B}\overline{C}$ 00	$\overline{B}C$ 01	$BC$ 11	$B\overline{C}$ 10
$\overline{A}$ 0	1	1		
$A$ 1			1	1

$\rightarrow ABD$

$\overline{A}\overline{B} + ABD$

Ans

Q  $f(A, B, C, D) = \overline{A}\overline{B}\overline{C} \cdot 1 + \overline{A}\overline{B}C \cdot 1 + ABCD + AB\overline{C}\overline{D}$

3 Variable

Implicants , Prime Implicants, Essential Prime Implicants

$$= \sum m(0, 1, 3, 6, 7)$$

**Ex**  $f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC + ABC$

$\swarrow$ $BC$	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
$\bar{A}$ 0	1	1	1	
$A$ 1			1	1

$$= \bar{A}\bar{B} + AB + \bar{A}C \checkmark$$

Implicants = 5

Prime Implicants = 4

Essential prime

Implicants = 2

$\swarrow$ $BC$	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
$\bar{A}$ 0	1	1	1	
$A$ 1			1	1

$$= \bar{A}\bar{B} + AB + BC \checkmark$$



Ex



A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
	00	01	11	10
$\bar{A}$ 0	1	1		1
A 1		1	1	1

$$= \bar{A}\bar{B} + B\bar{C} + AC \quad \checkmark$$

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
	00	01	11	10
$\bar{A}$ 0	1	1		1
A 1		1	1	1

$$= \bar{A}\bar{C} + \bar{B}C + AB \quad \checkmark$$

Implicants = 6

Prime Implicants = 6

EPI = 0

Ex



$$= \bar{A}\bar{C}D + \bar{A}BC + AB\bar{C} + ACD$$

AB \ CD					
		$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$	00		1		
$\bar{A}B$	01		1	1	1
$AB$	11	1	1	1	
$A\bar{B}$	10			1	

RPI

$$I = 8$$

$$PI = 5$$

$$EPI = 4$$

$$RPI = 1$$

$AB \backslash CD$

	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	1	1		
$\bar{A}B$ 01		1	1	
$AB$ 11			1	1
$A\bar{B}$ 10				1

$$I = 7$$

$$PI = 6$$

$$EPI = 2$$





**Darr**  
ke aage  
**Jeet**  
hai



# Designing of Combinational Circuit

Step 1. Find the number of inputs & output

Step 2. Write the truth table.

Step 3. Write the logical Expression.


Step 4. Minimize the logical Expression.

Step 5. Hardware Implementation.



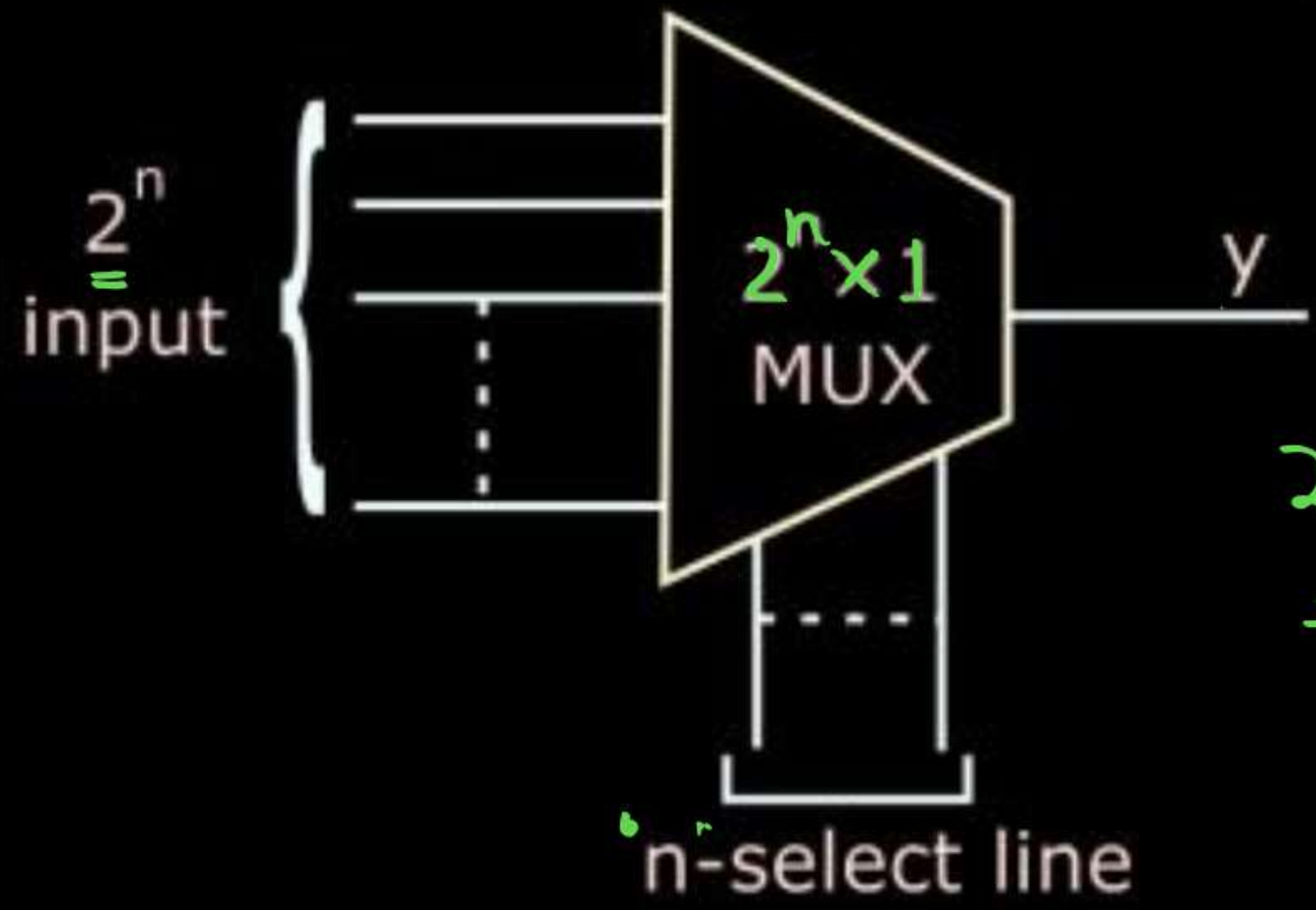
# MULTIPLEXER

→ MUX → universal logic ✓  
→ MUX → AND-OR logic ✓



$2^n \rightarrow 1$

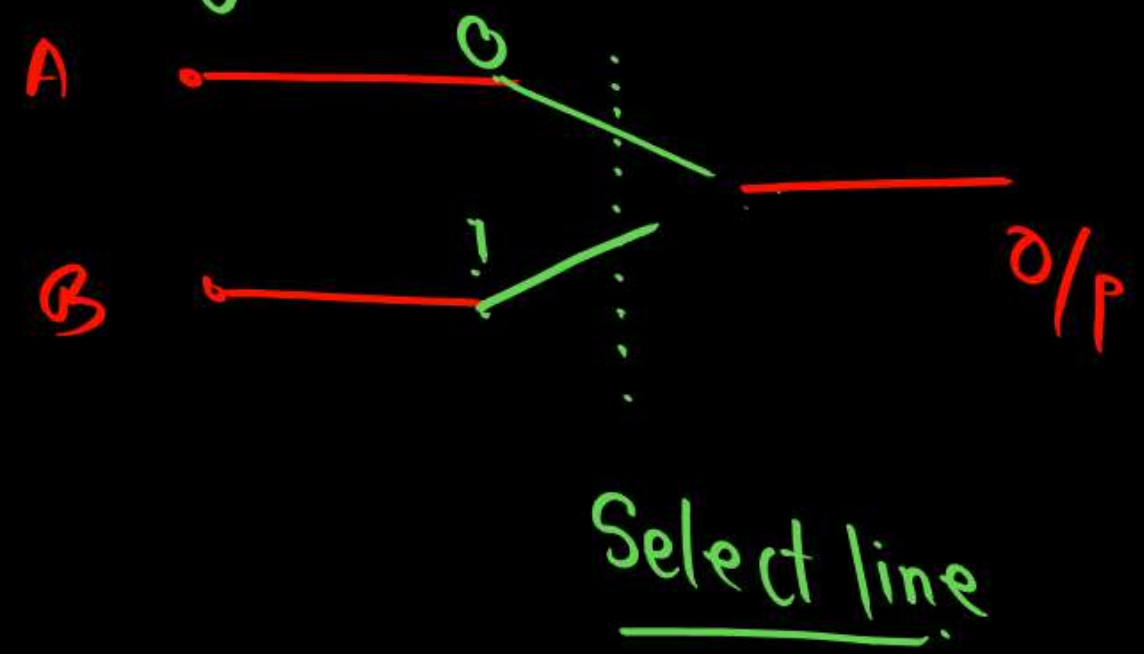


$x = 0, 1$   
 $2$



Ex. 1. Design a 2 x 1 MUX?

Step-1. Number of input 2 outputs

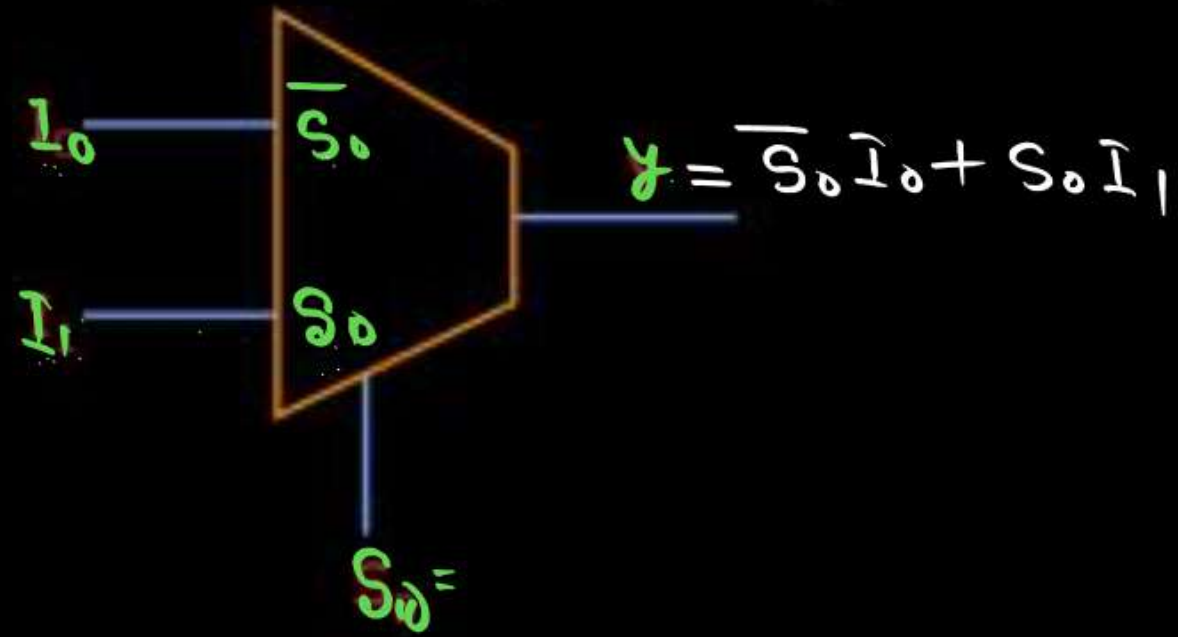

Step 2. Truth table.

$S_0$	$Y$
0	$I_0$
1	$I_1$

$$Y = \overline{S_0} I_0 + S_0 I_1$$

Step 3. Logical expression

$$y = \bar{S}_0 I_0 + S_0 I_1$$



Step 4. Minimization

→ SOP

Step 5. Hardware implementation

MUX → AND-OR Logic

De-MUX → AND Logic

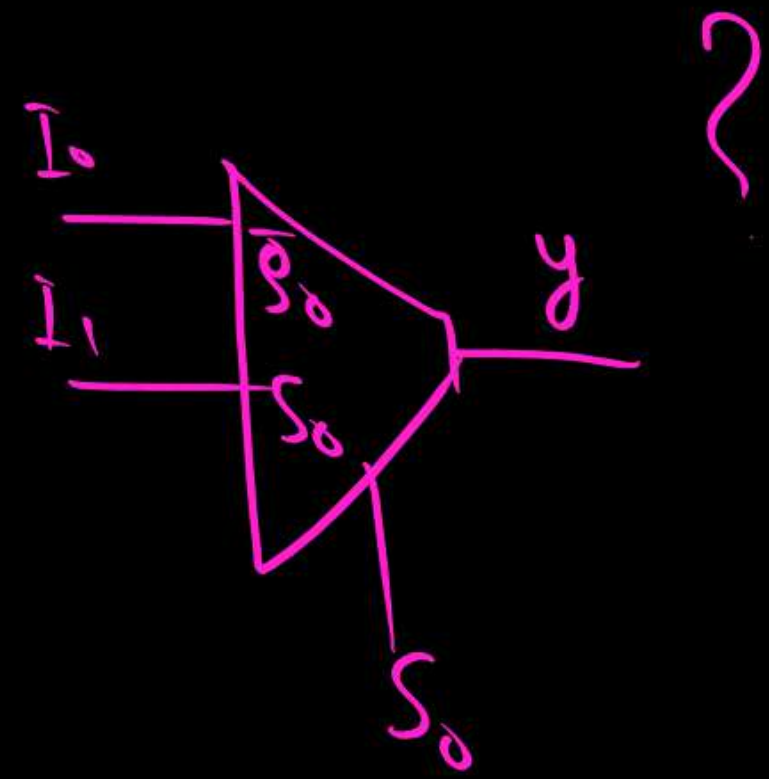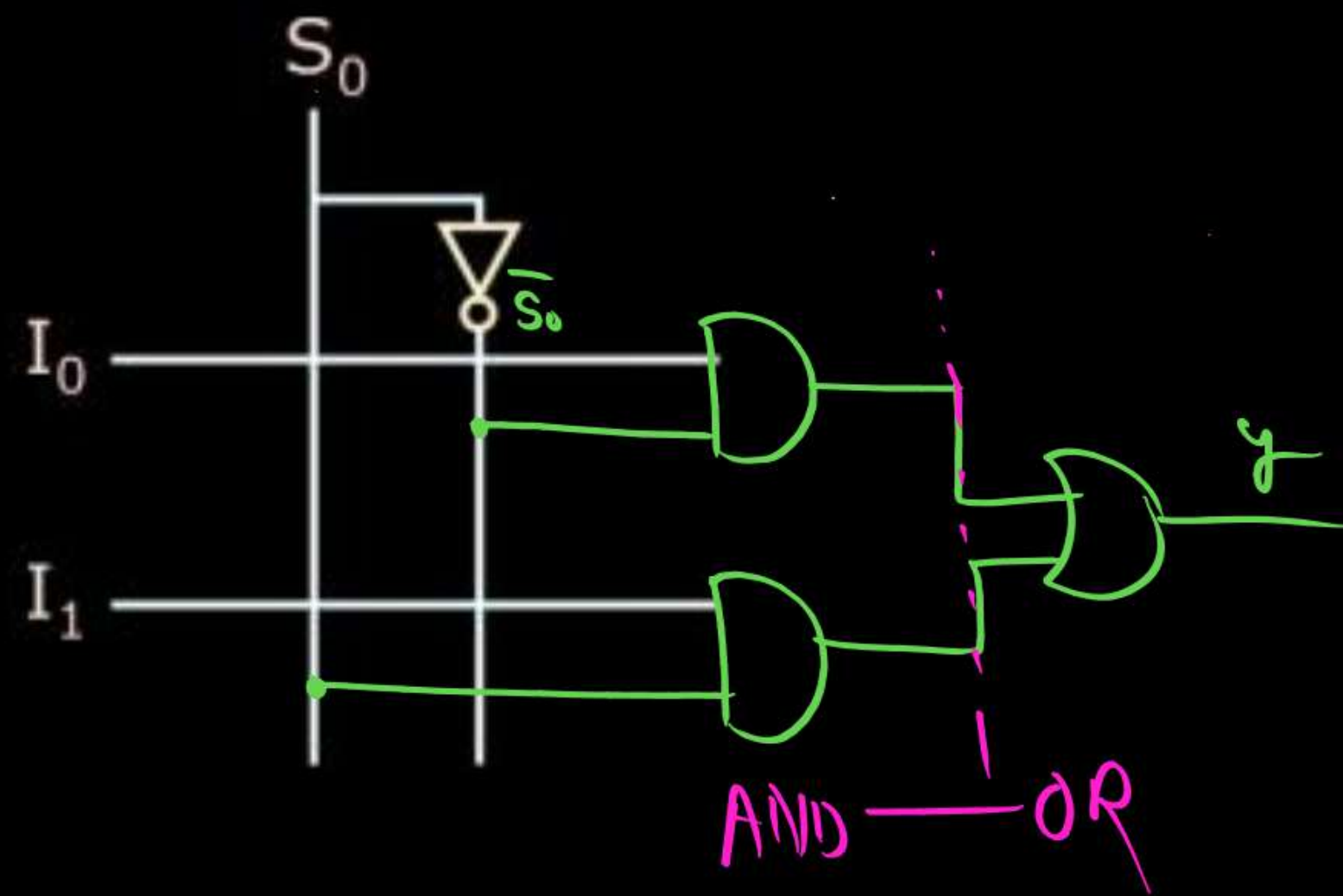


## Ex. 2. Design a 4x1 MUX?



8


Step-1. Number of input & outputs

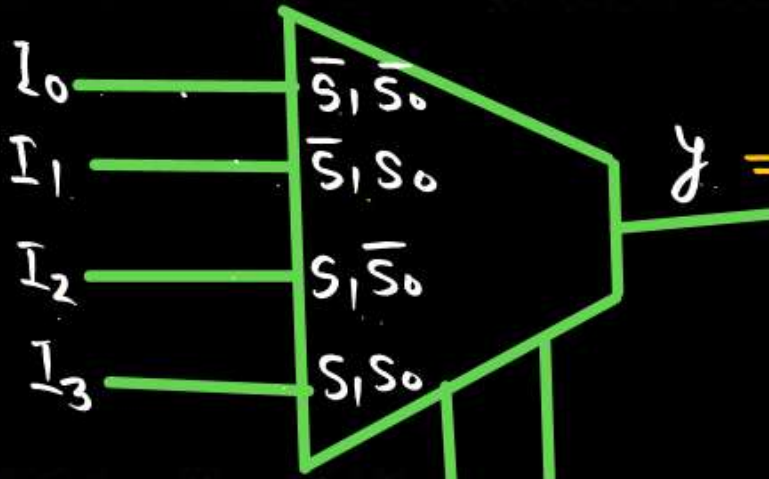

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

Step 2. Truth table.  $S_1, S_0, Y$   
M.B

$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

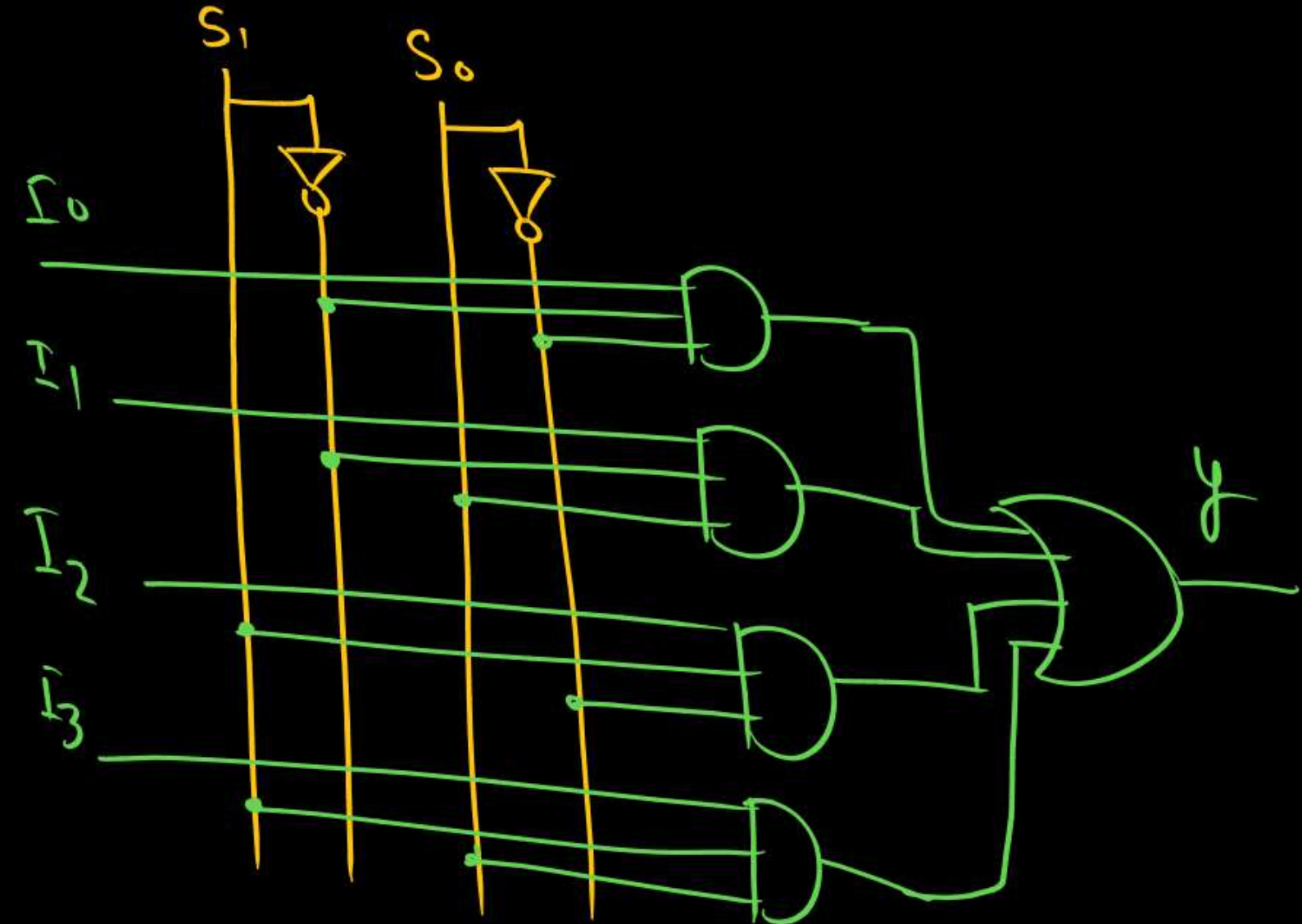





Step 3. Logical expression



Step 4. Minimization

Step 5. Hardware implementation

Design a 8x1 MUX

## TYPE -1 Designing of higher order MUX by using lower order MUX

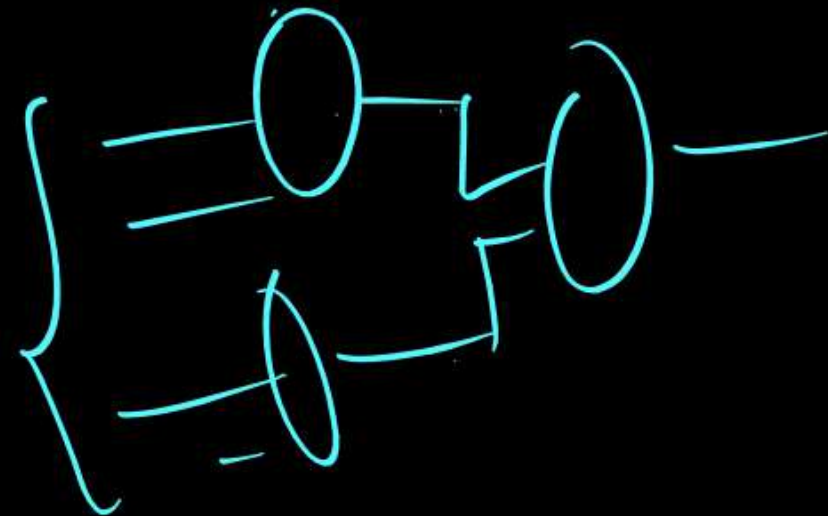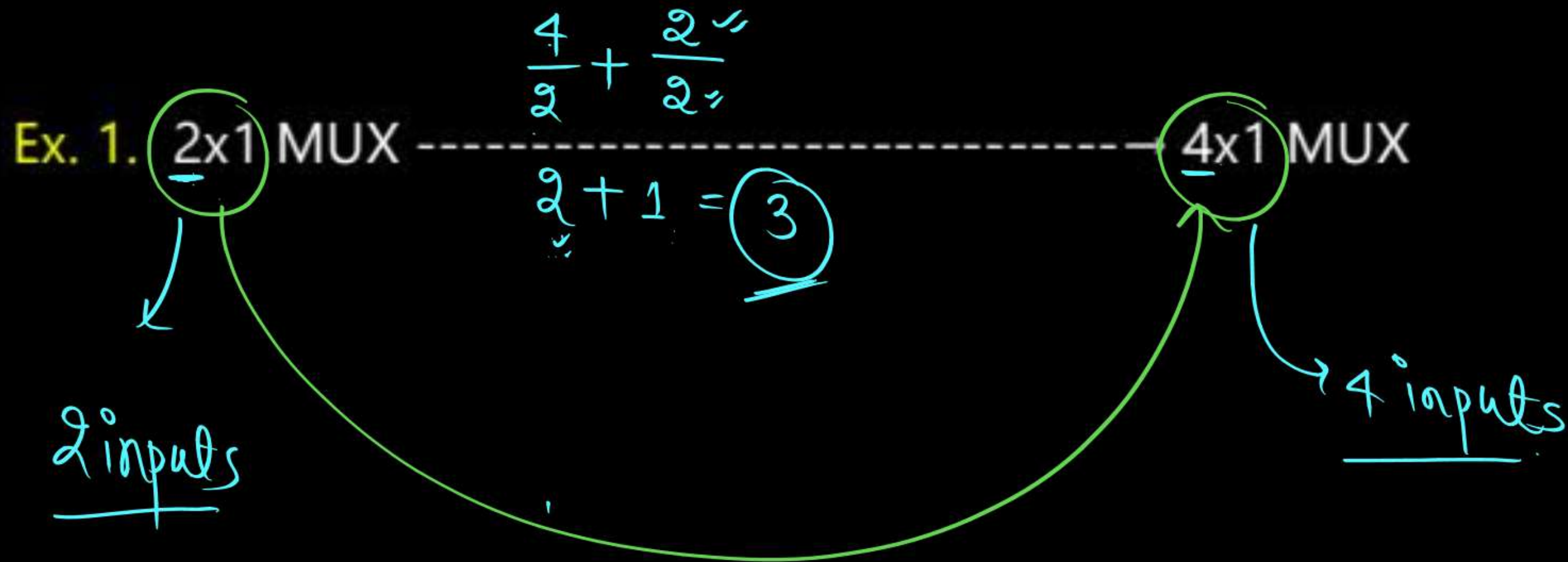

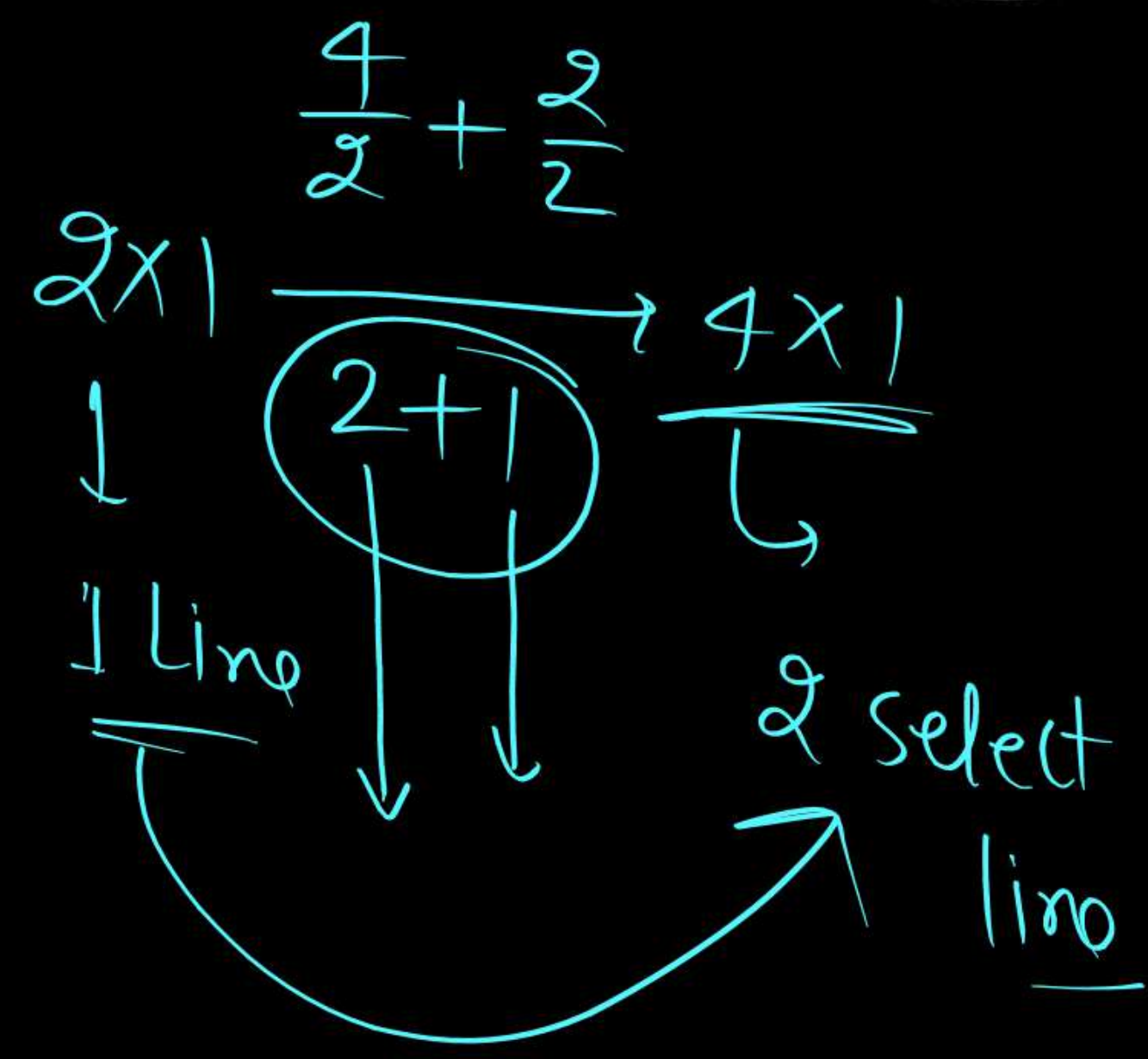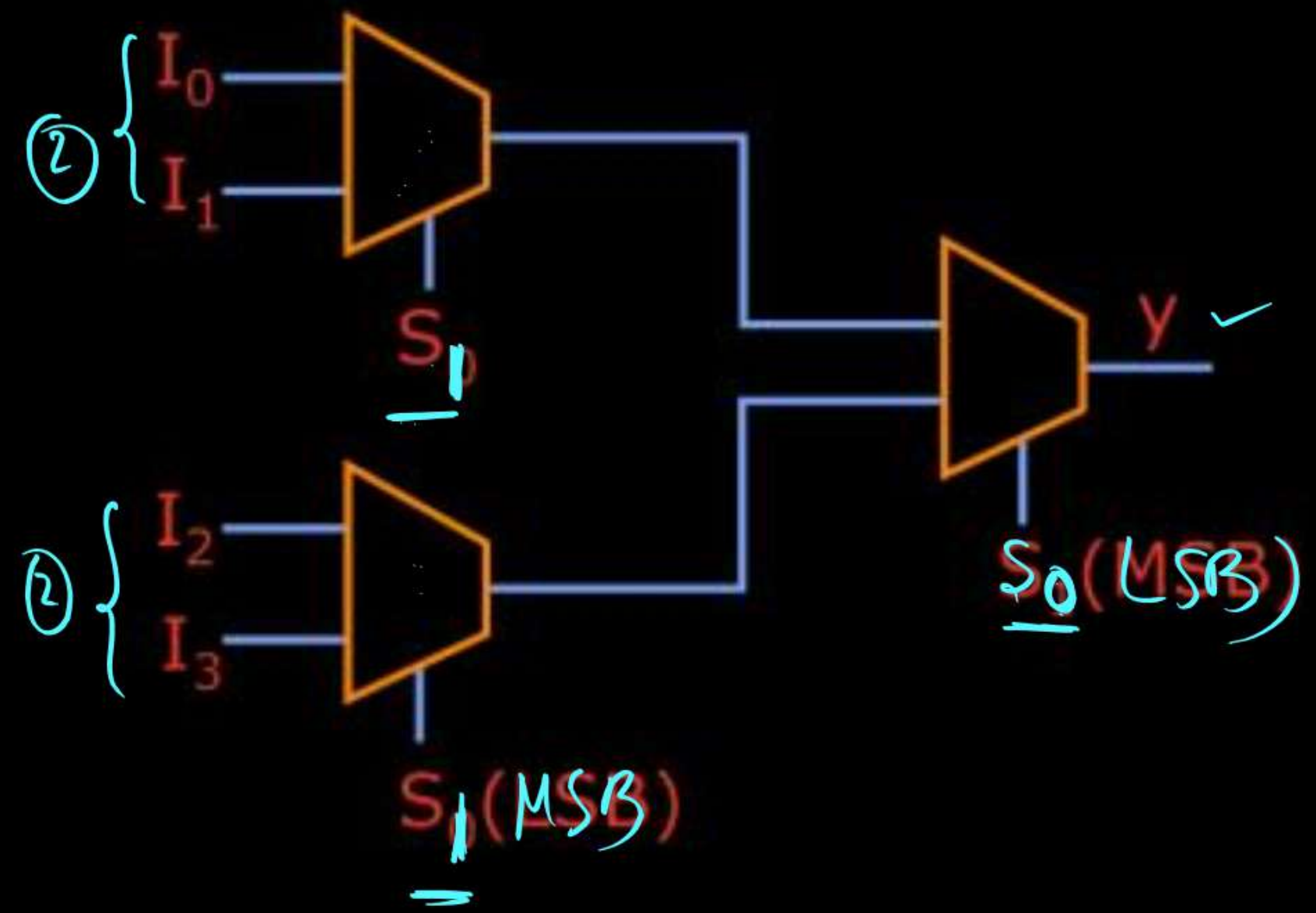



Ex. 2.  $2 \times 1$  MUX  $\xrightarrow{\frac{8}{2} + \frac{4}{2} + \frac{2}{2}}$   $8 \times 1$  MUX

$4 + 2 + 1 = 7$

Ex. 3.  $2 \times 1$  MUX  $\xrightarrow{\frac{16}{2} + \frac{8}{2} + \frac{4}{2} + \frac{2}{2}}$   $16 \times 1$  MUX

$8 + 4 + 2 + 1 = 15$

$2 \times 1$  MUX  $\xrightarrow{2^n - 1}$   $2^n \times 1$  MUX

Ex. 3. 4 x 1 MUX  $\xrightarrow{\frac{16}{4} + \frac{4}{4}}$  16 x 1 MUX


$4 + 1 = 5$

Ex. 4. 4 x 1 MUX  $\xrightarrow{\frac{8}{4} + \frac{2}{4}}$  8 x 1 MUX


$2 + 1 = 3$

$$4 \times 1 \xrightarrow{\frac{8}{4} + \frac{2}{4}} 8 \times 1 \text{ MUX}$$

$$2 + 1 = \textcircled{3} //$$

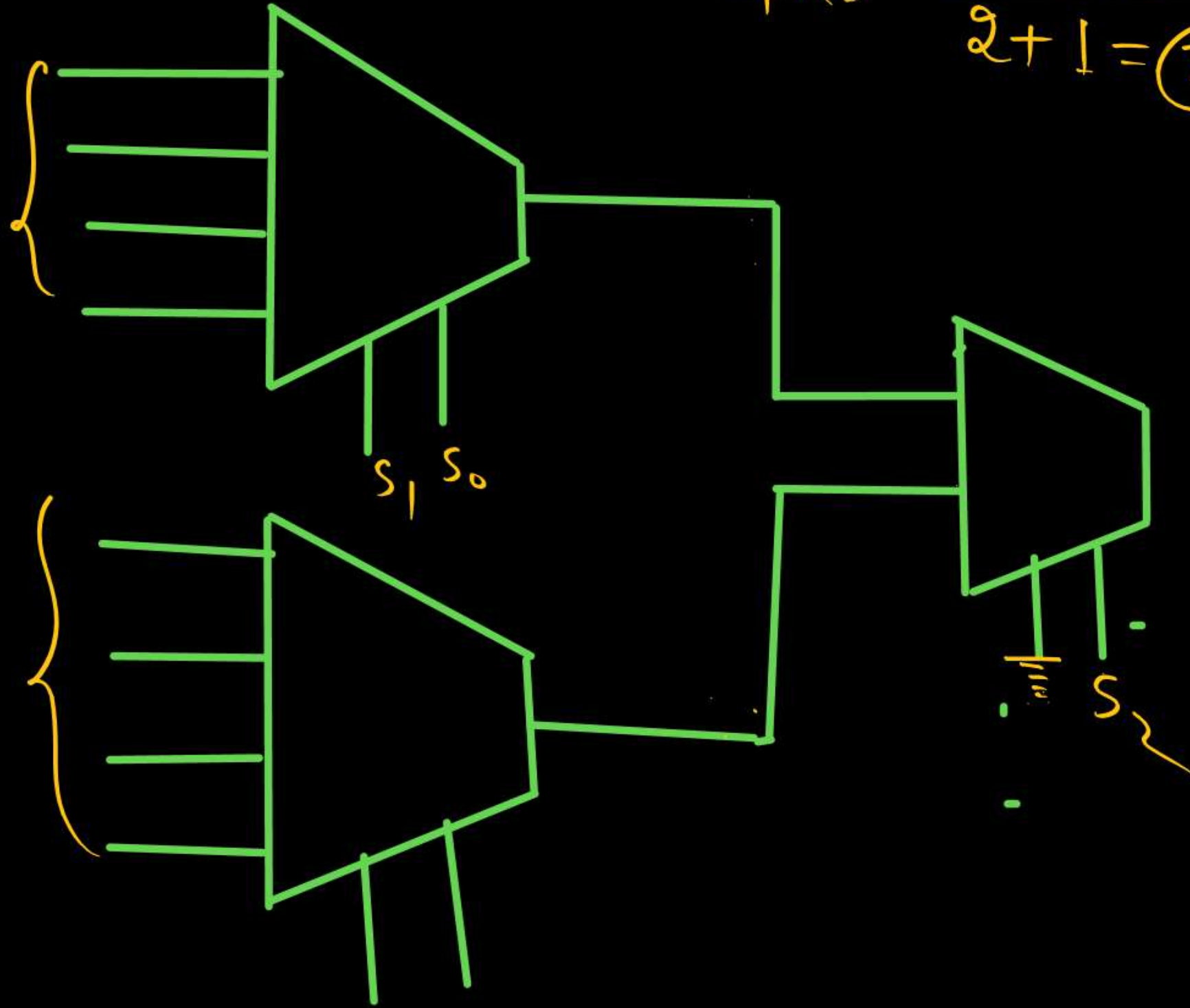



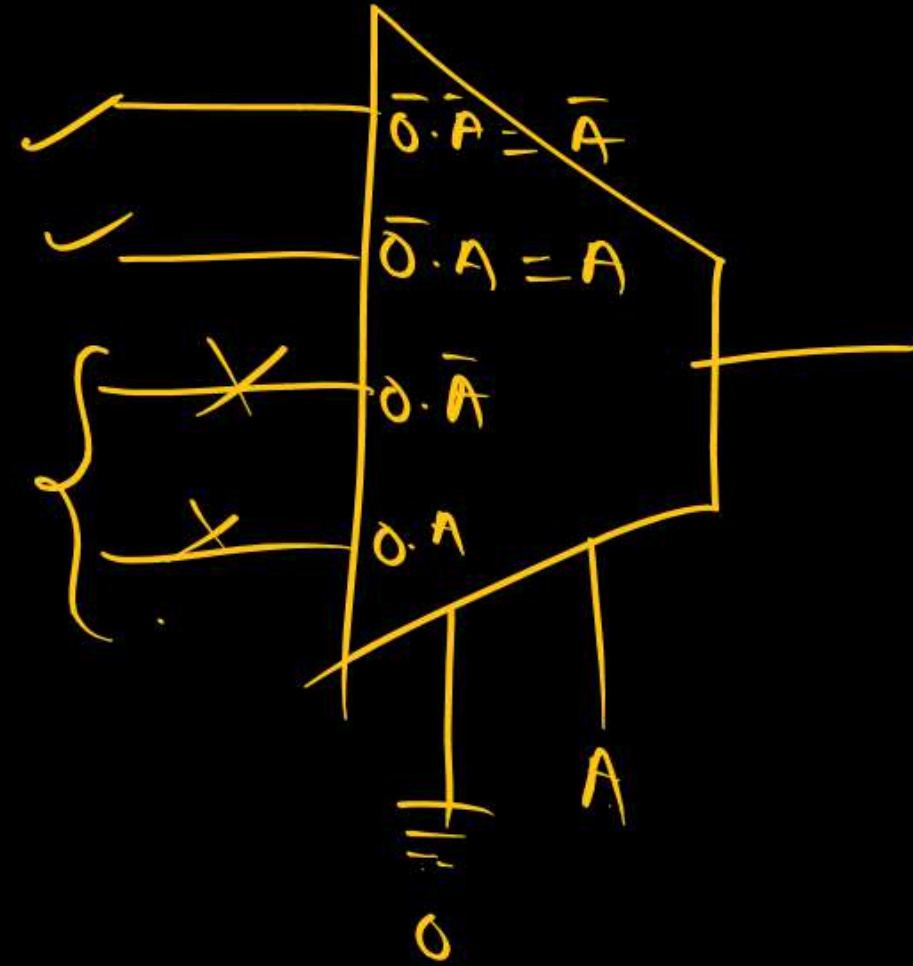


Ex. 5. 4 x 1 MUX  $\xrightarrow{\frac{64}{4} + \frac{16}{4} + \frac{4}{4}}$  64 x 1 MUX

$$16 + 4 + 1 = 21$$



# TYPE -2 MUX AS A UNIVERSAL LOGIC

## 1. Not Gate

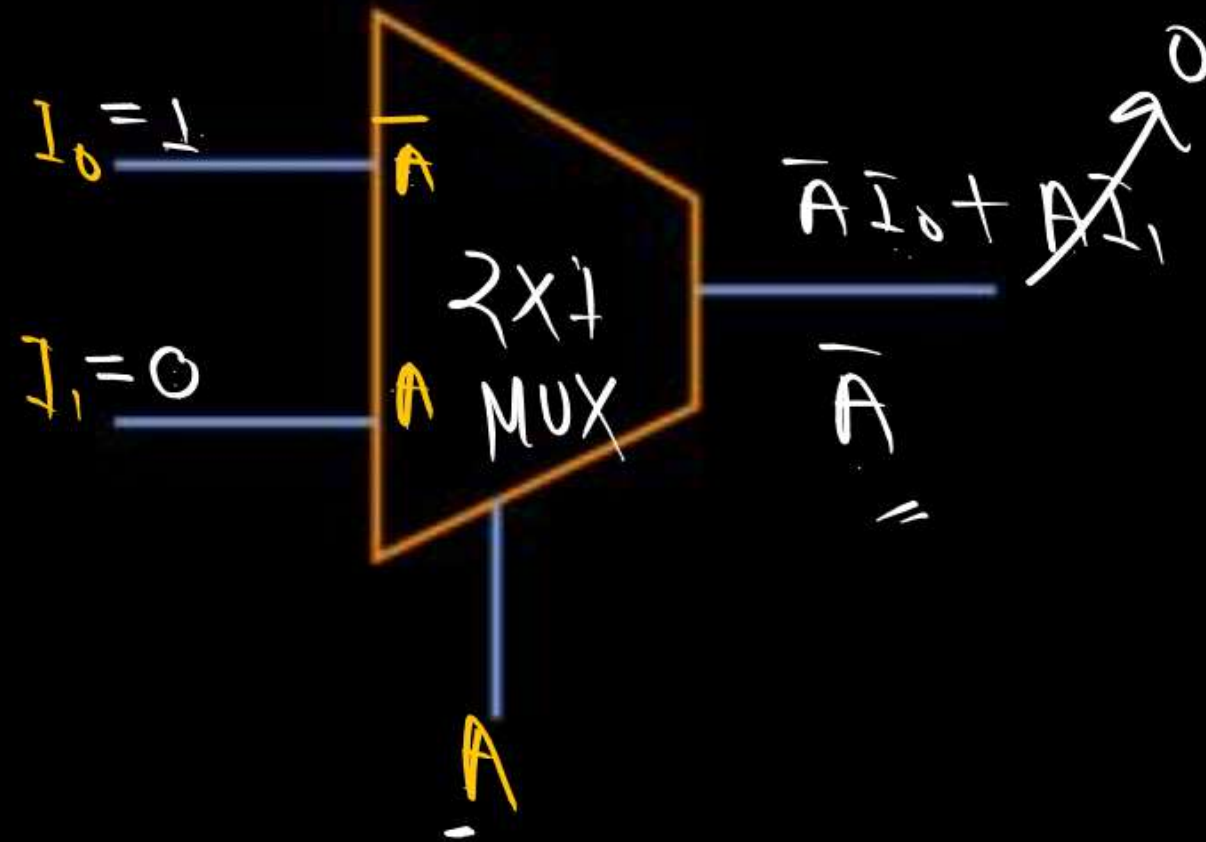




## 2. AND GATE

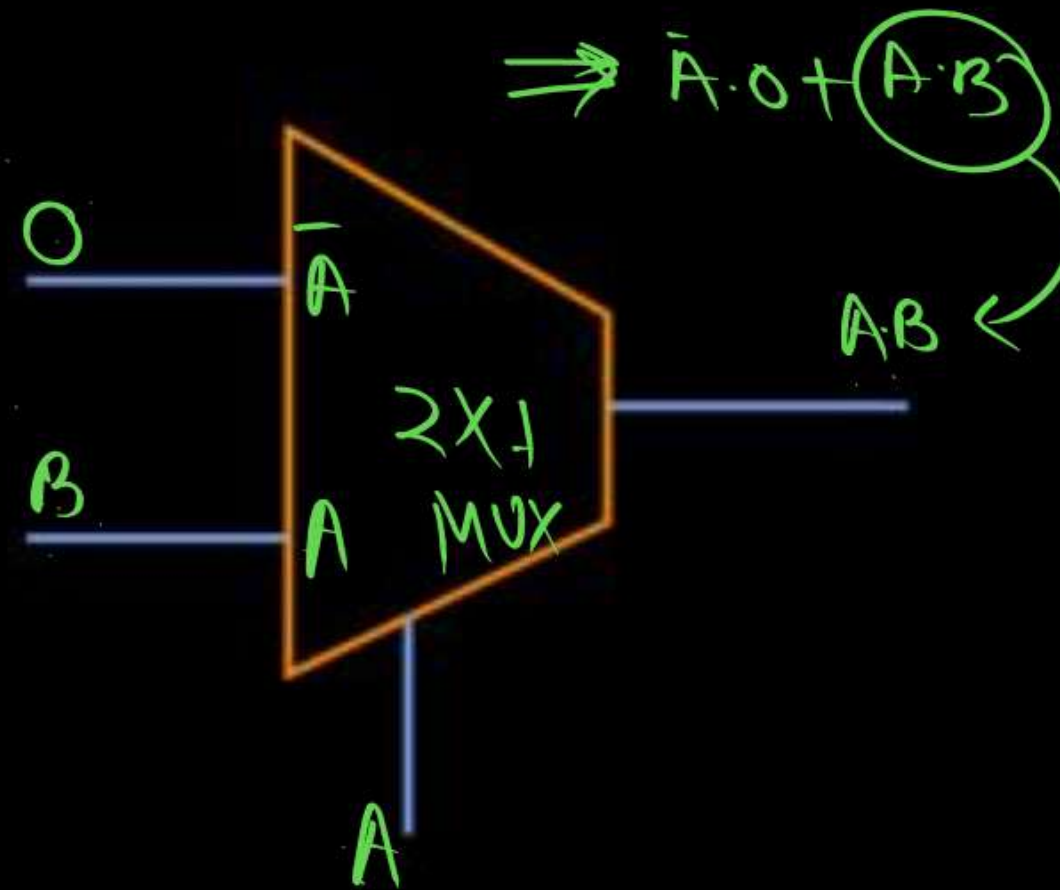
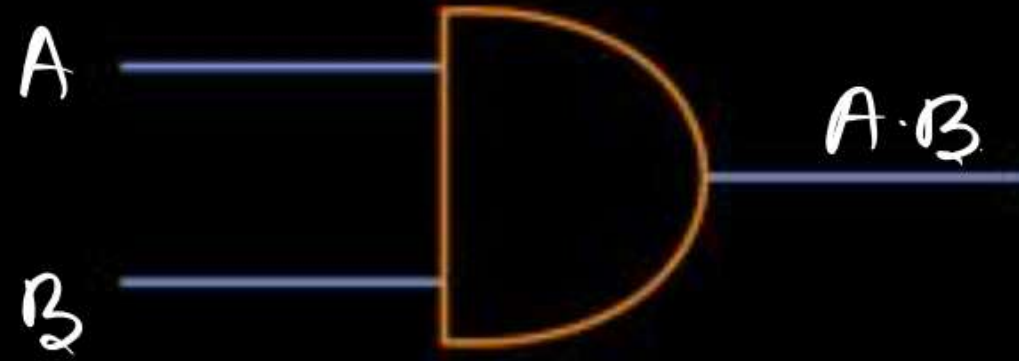


### 3. OR GATE

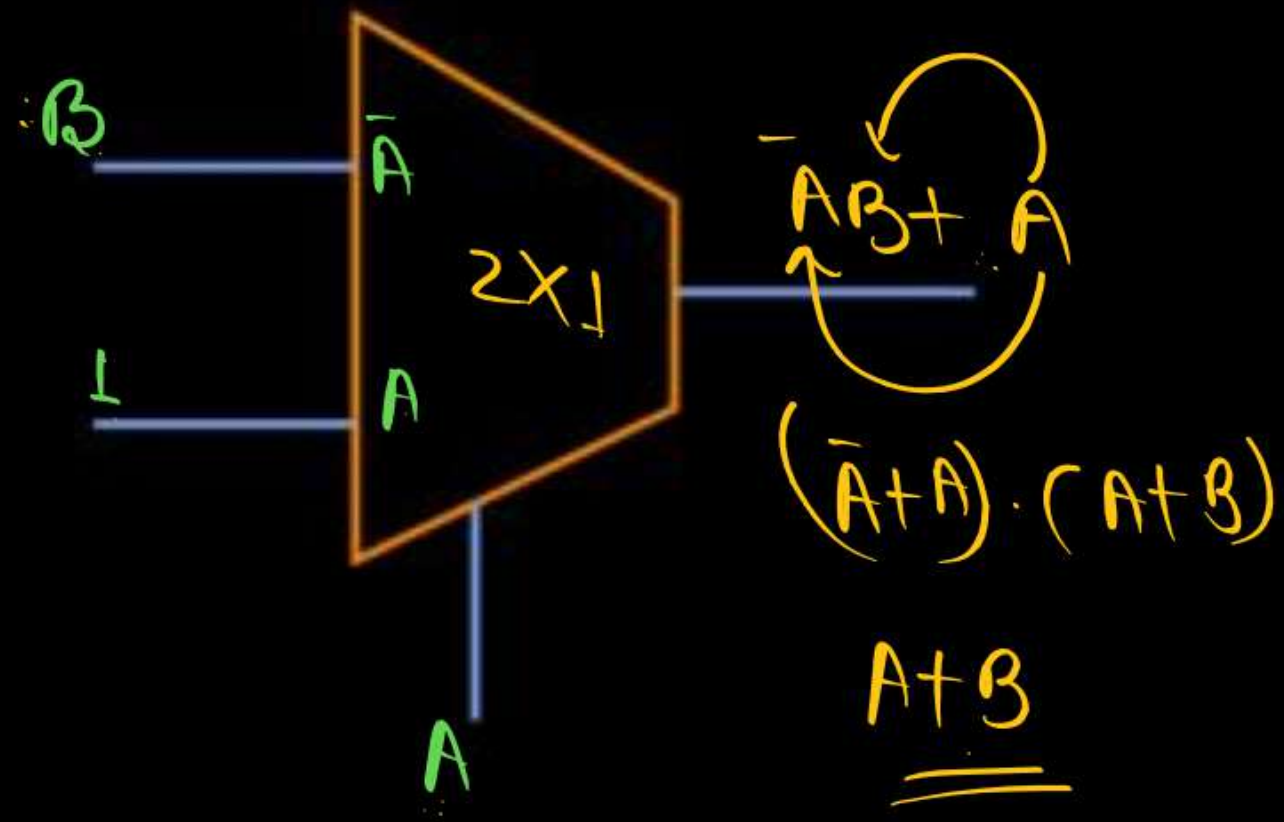


# 4. NAND GATE

2

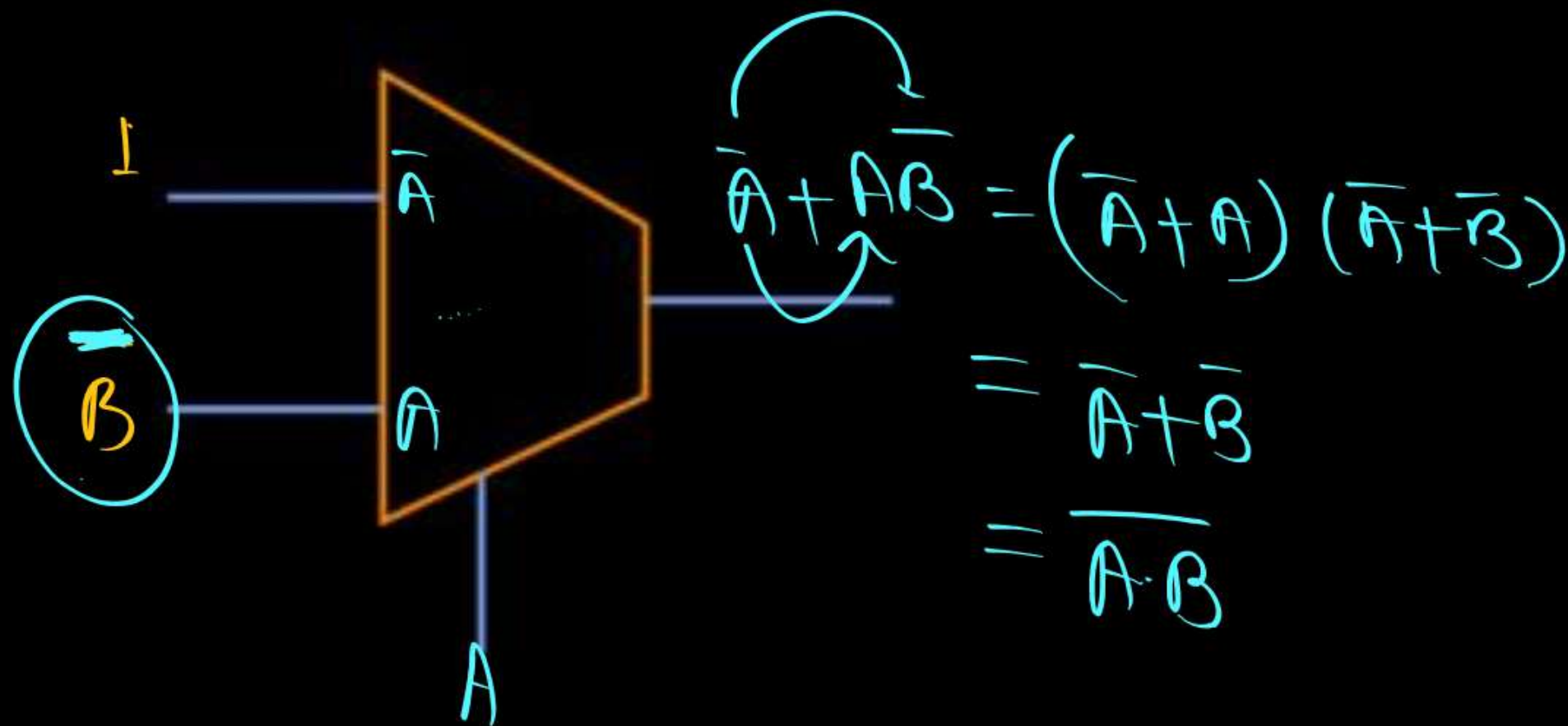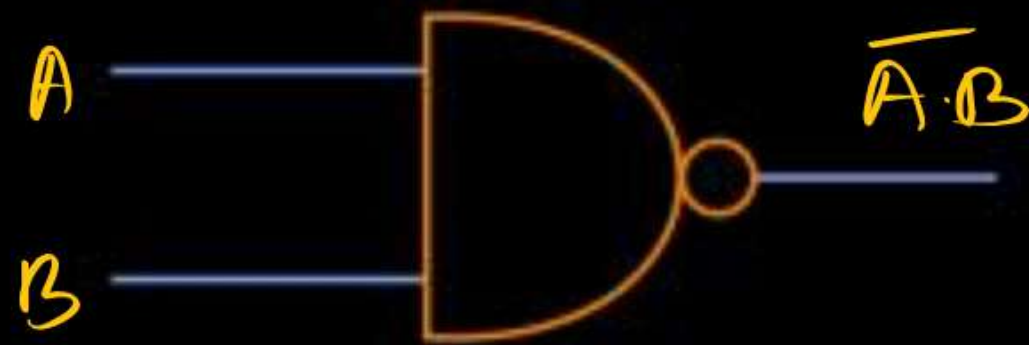




# 5. NOR GATE

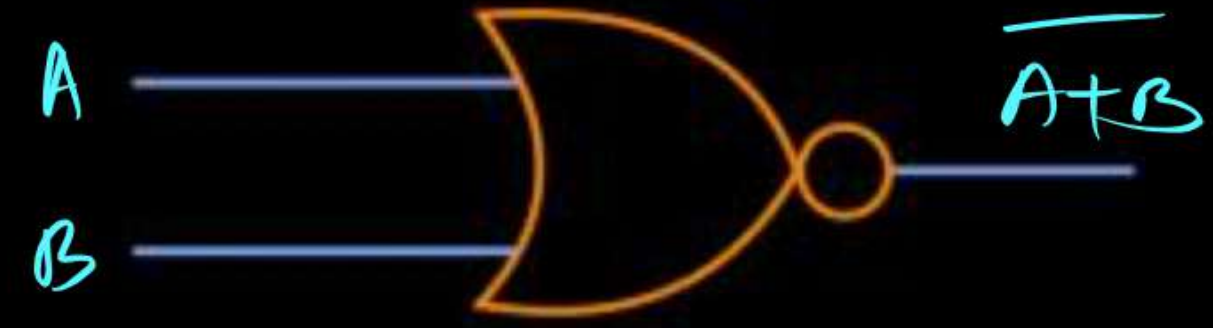


2

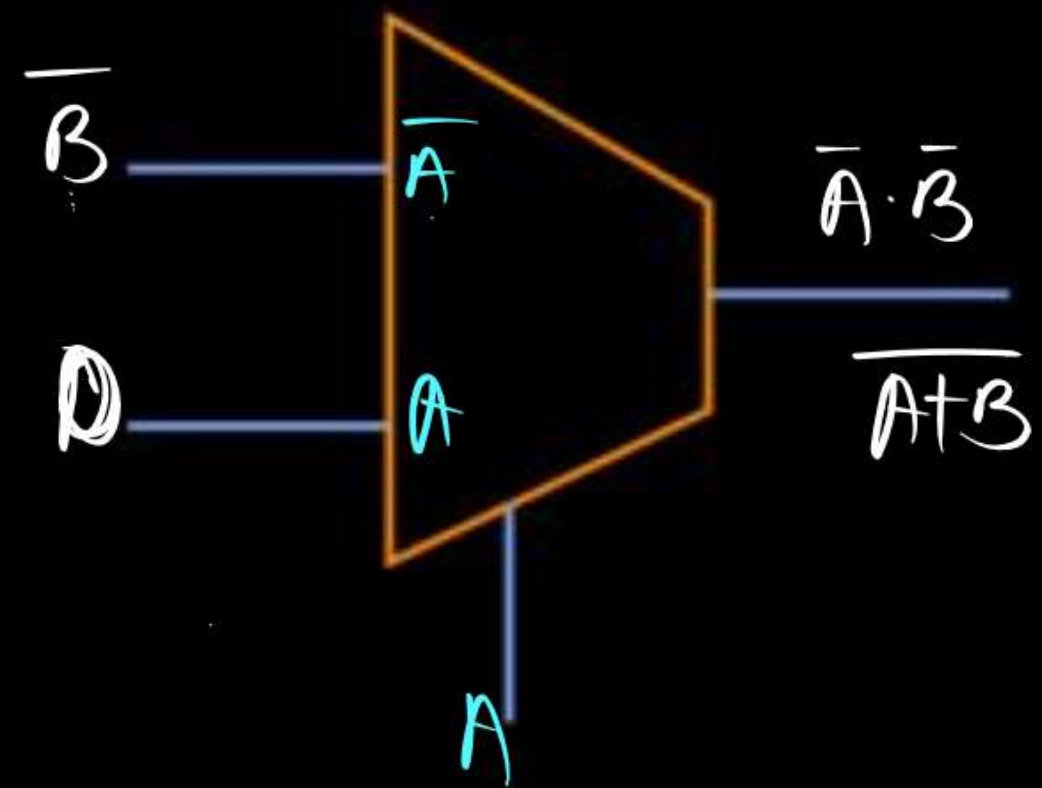

## 6. XOR GATE




2

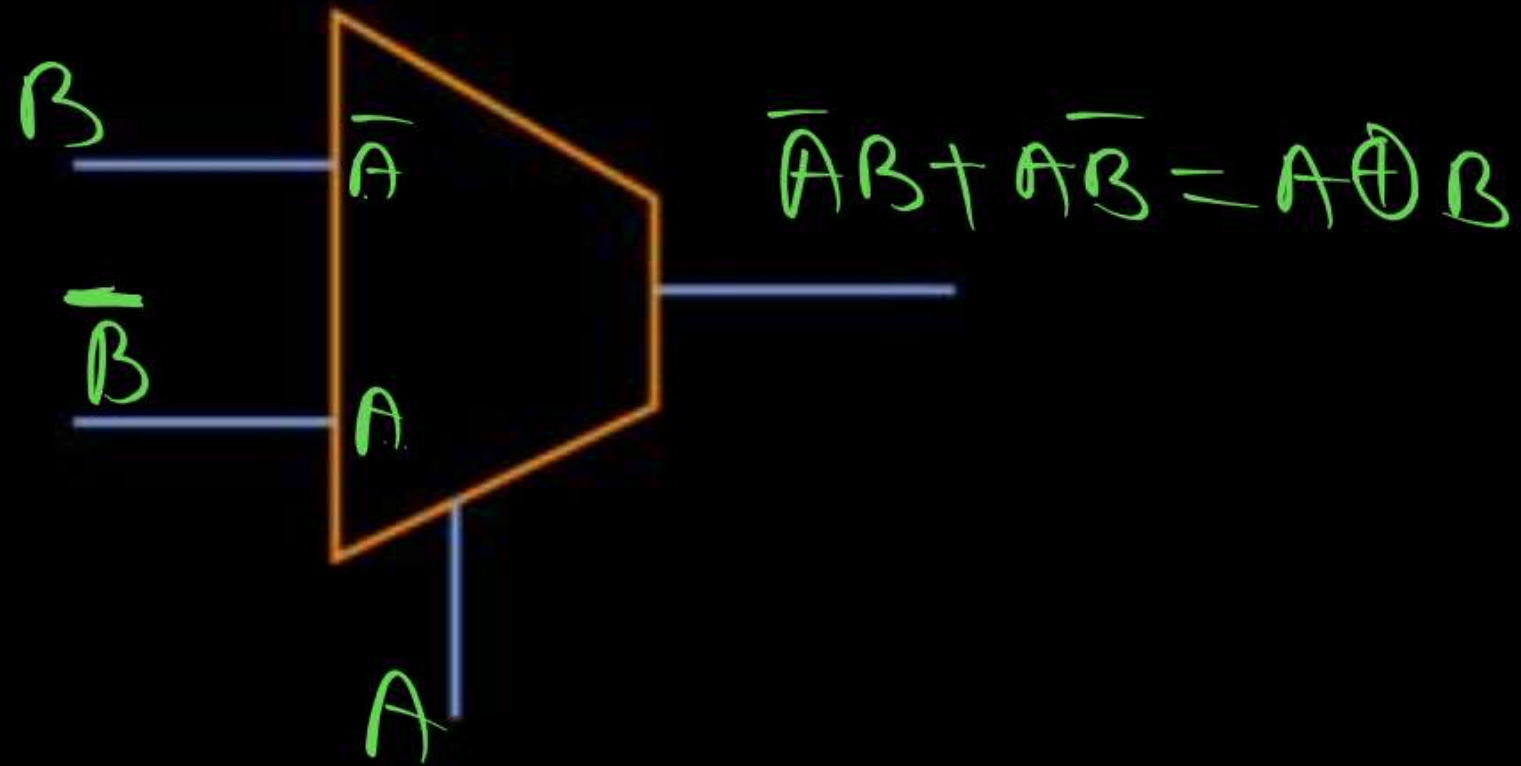

# 7. XNOR GATE

2

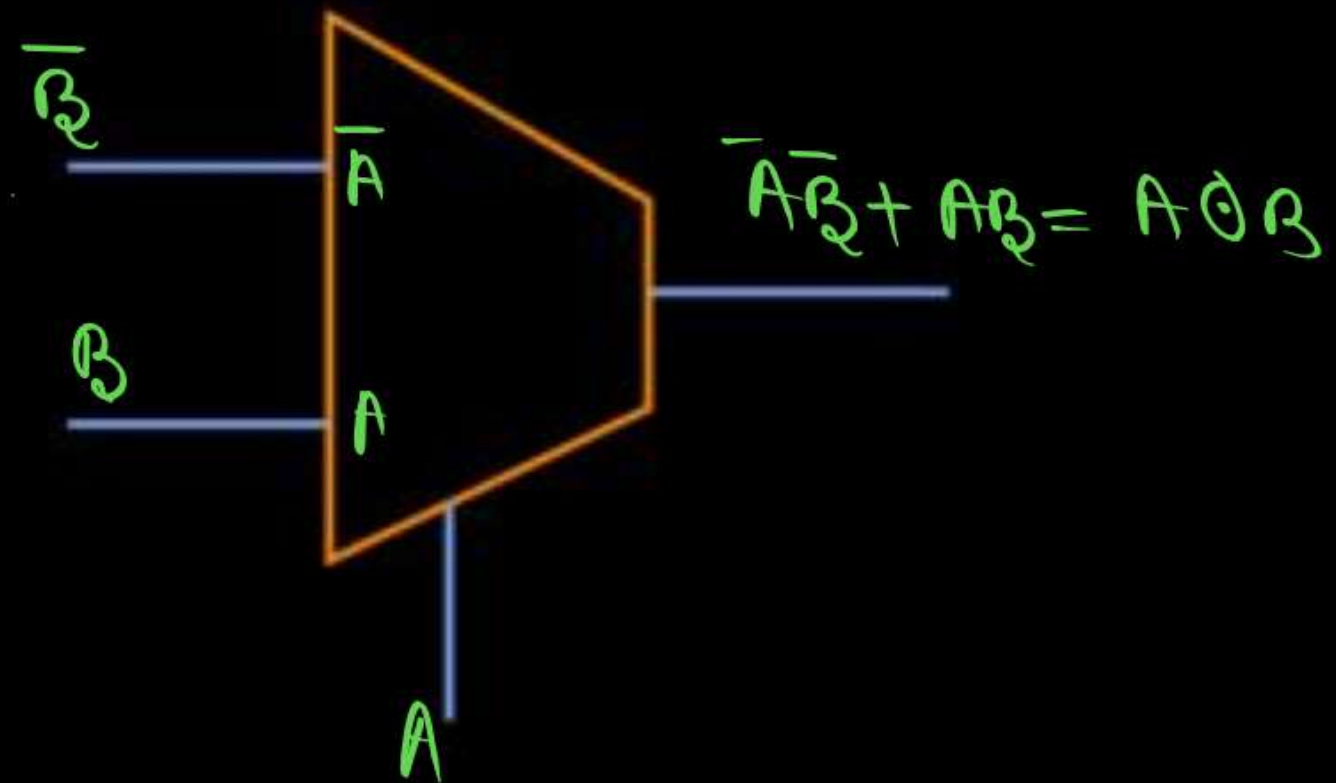




Q.



# Type-3 Minimization

Ex. 1.

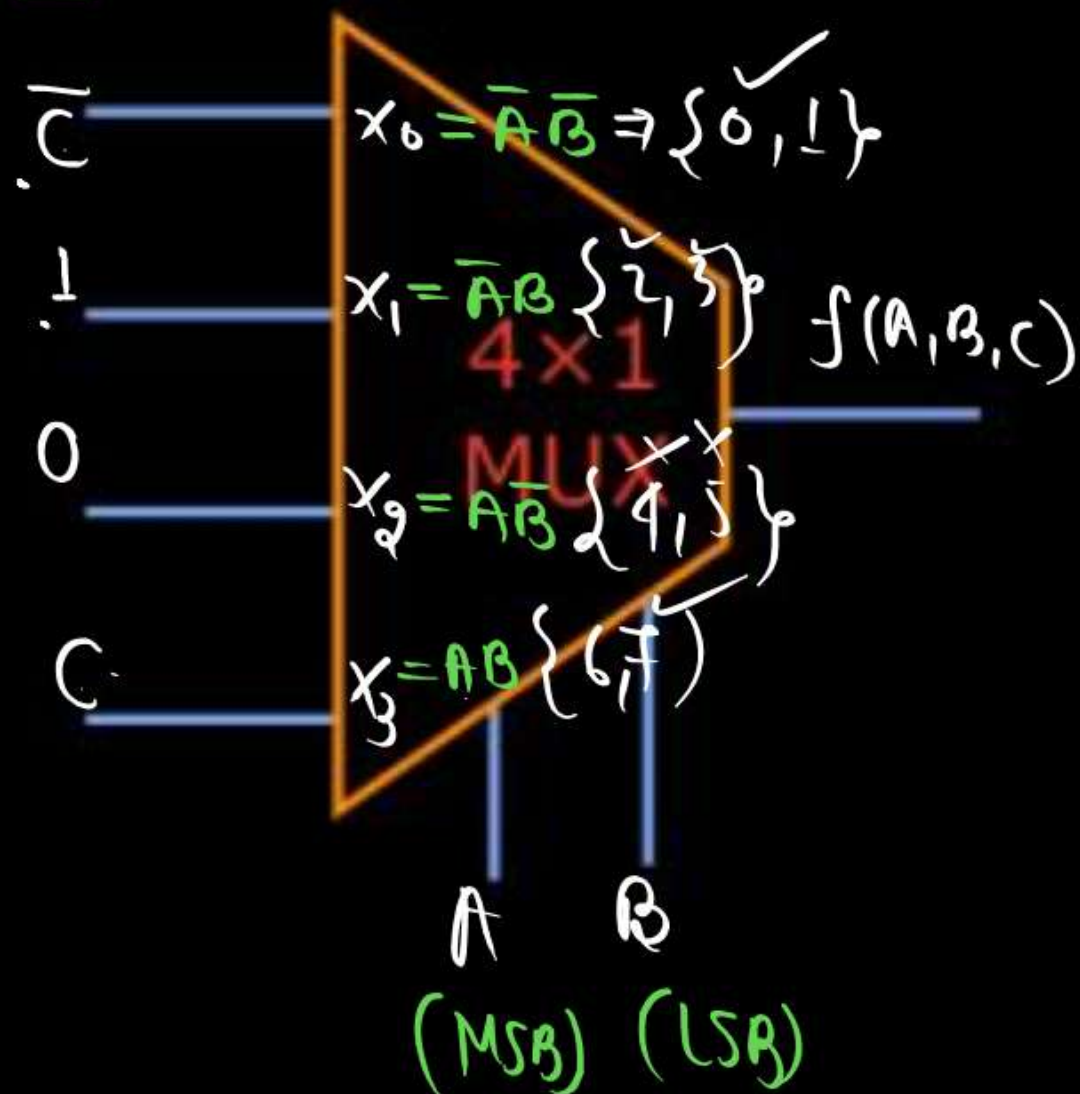


$$\begin{aligned}
 f(A, B, C) &= \bar{A}\bar{B}\bar{C} + \bar{A}B1 + A\bar{B}0 + A\cdot B\cdot C \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}B(\bar{C}+C) + A\bar{B}C \\
 &= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C \\
 &= \sum m(0, 2, 3, 7)
 \end{aligned}$$

A \ BC	00	01	11	10
0	1		1	1
1				

$$\bar{A}\bar{C} + BC \quad \text{Ans}$$


Ex

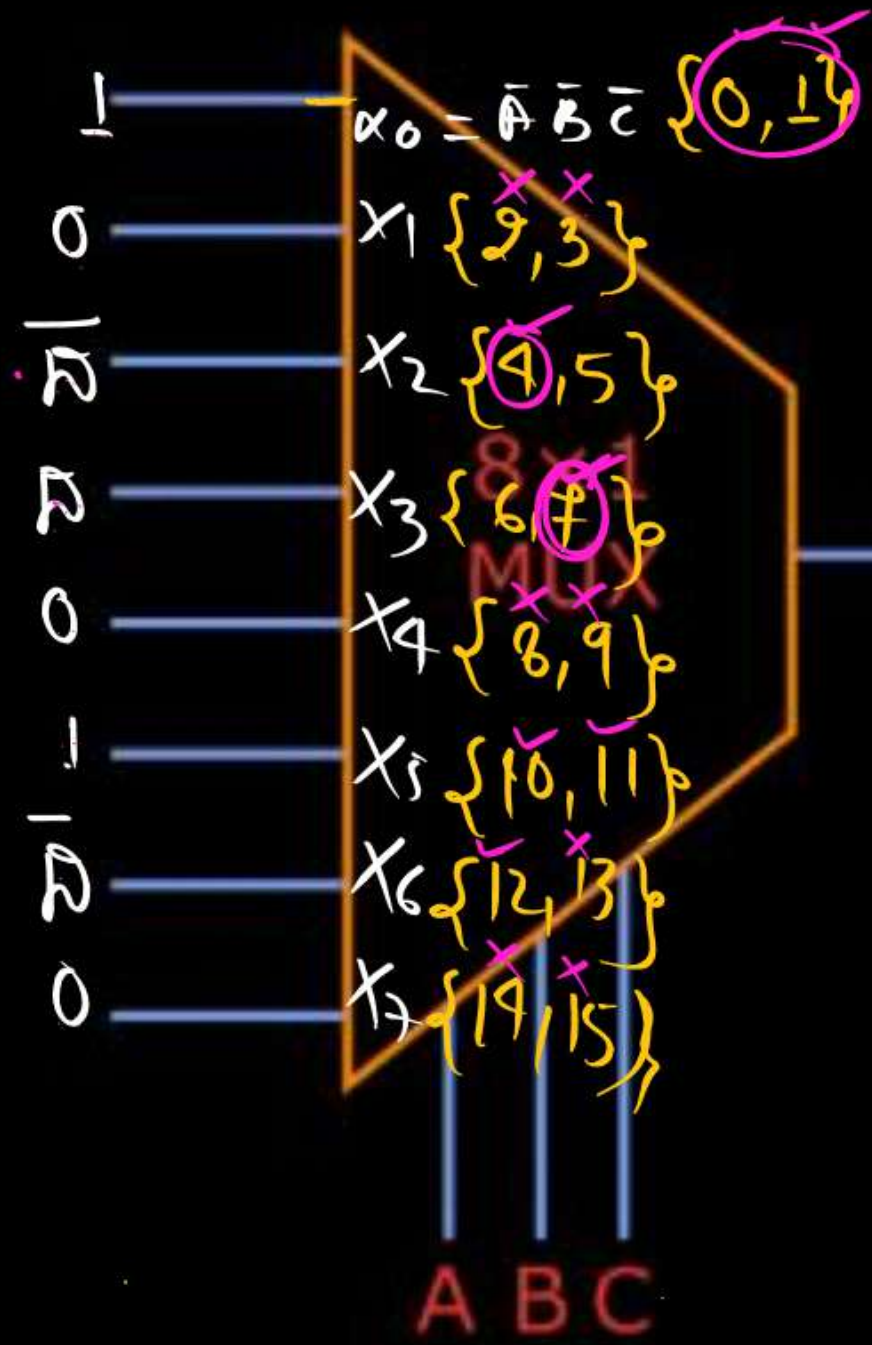


$$f(A, B, C, D) = \sum m(0, 1, 4, 7, 10, 11, 12)$$



Ex. GATE  
HW

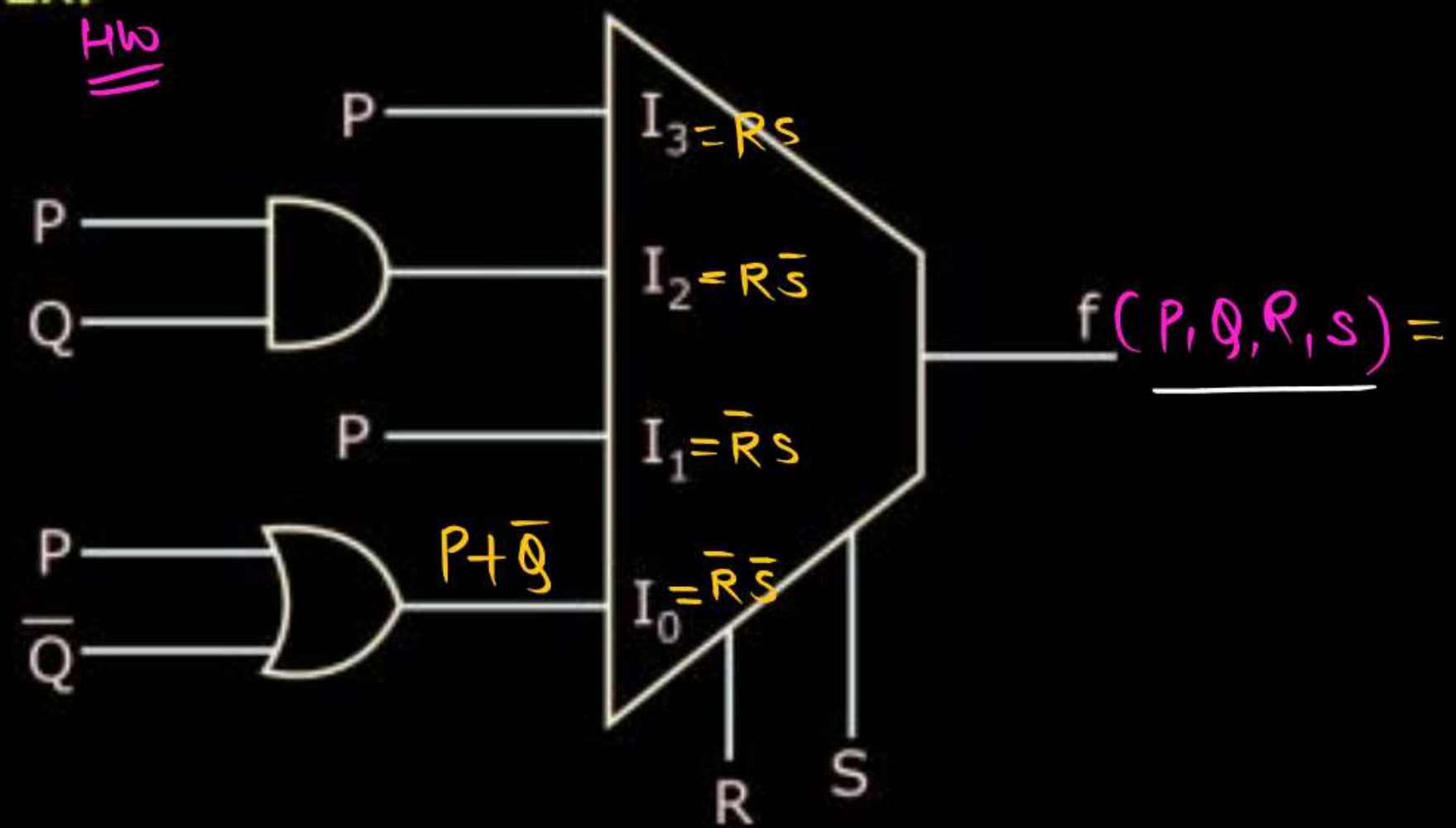

Ex.

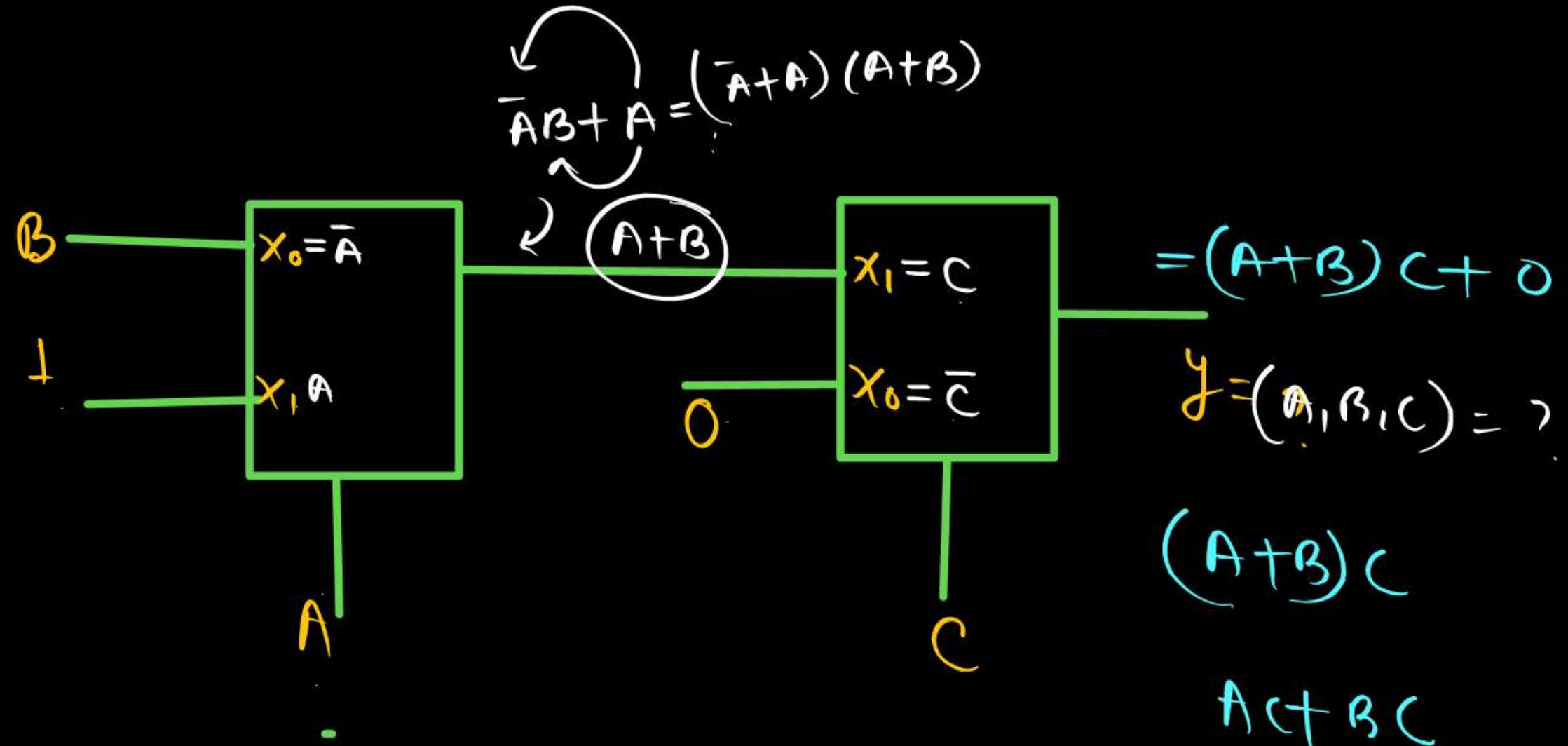


$$(A + B)C$$

$$AC + BC$$



Ans

# Type-4 Cascading of MUX

$$(A+B)C = P$$

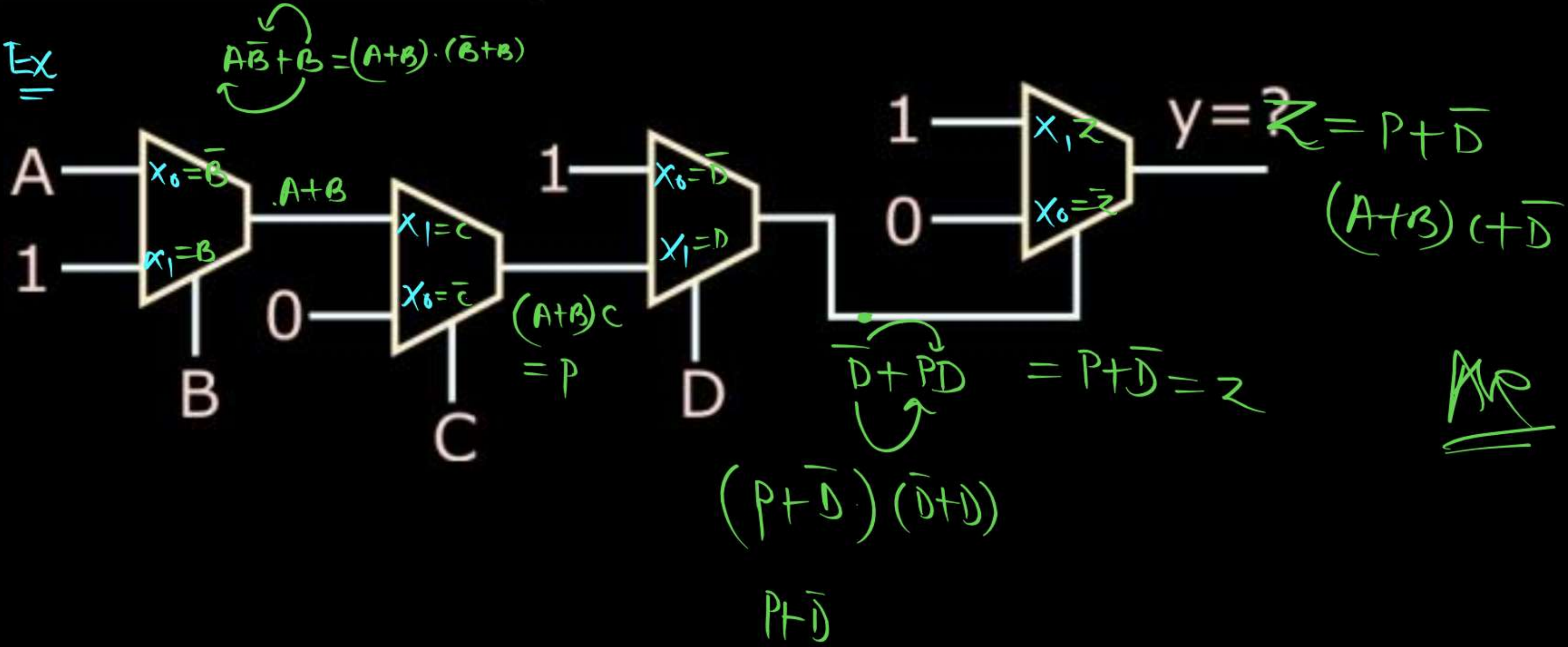




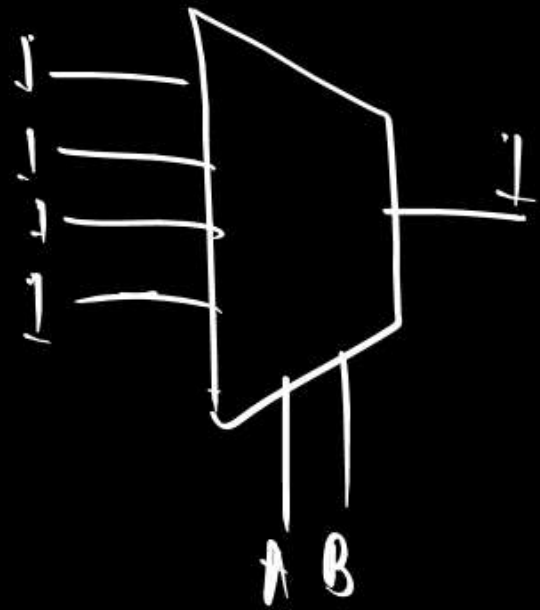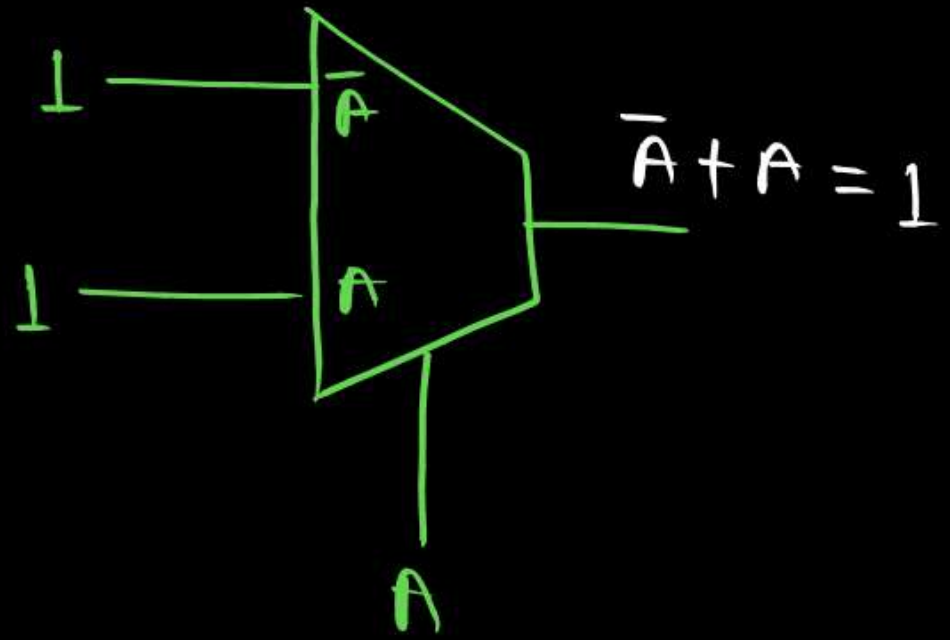

3 Sec

Ex.

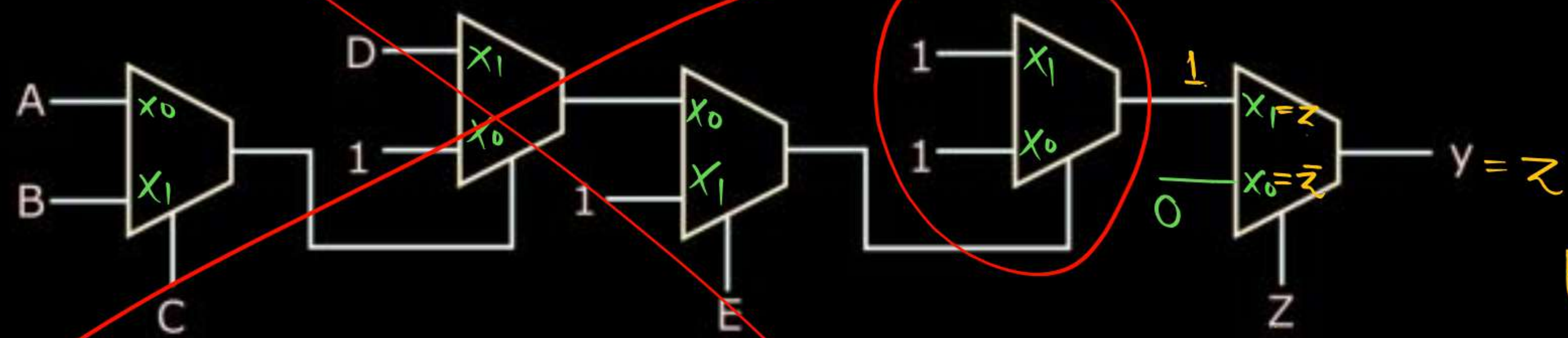

Ans

