



EC/EE/CS & IT/IN

Digital Electronics



**synchronous
Counter**





LECTURE NO. 10

Chandan Jha Sir (CJ Sir)

TOGGLE MODE OF THE FLIP FLOP

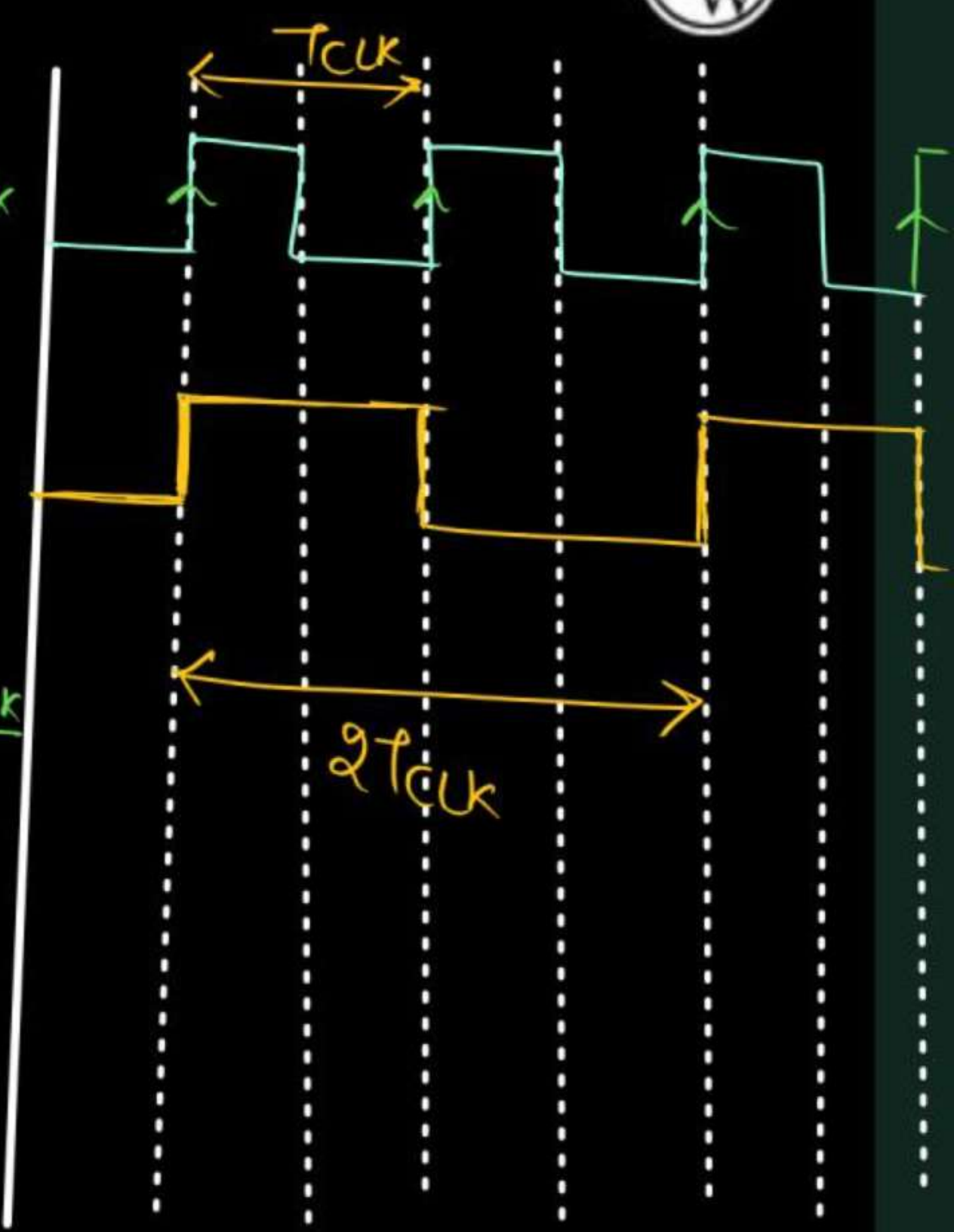
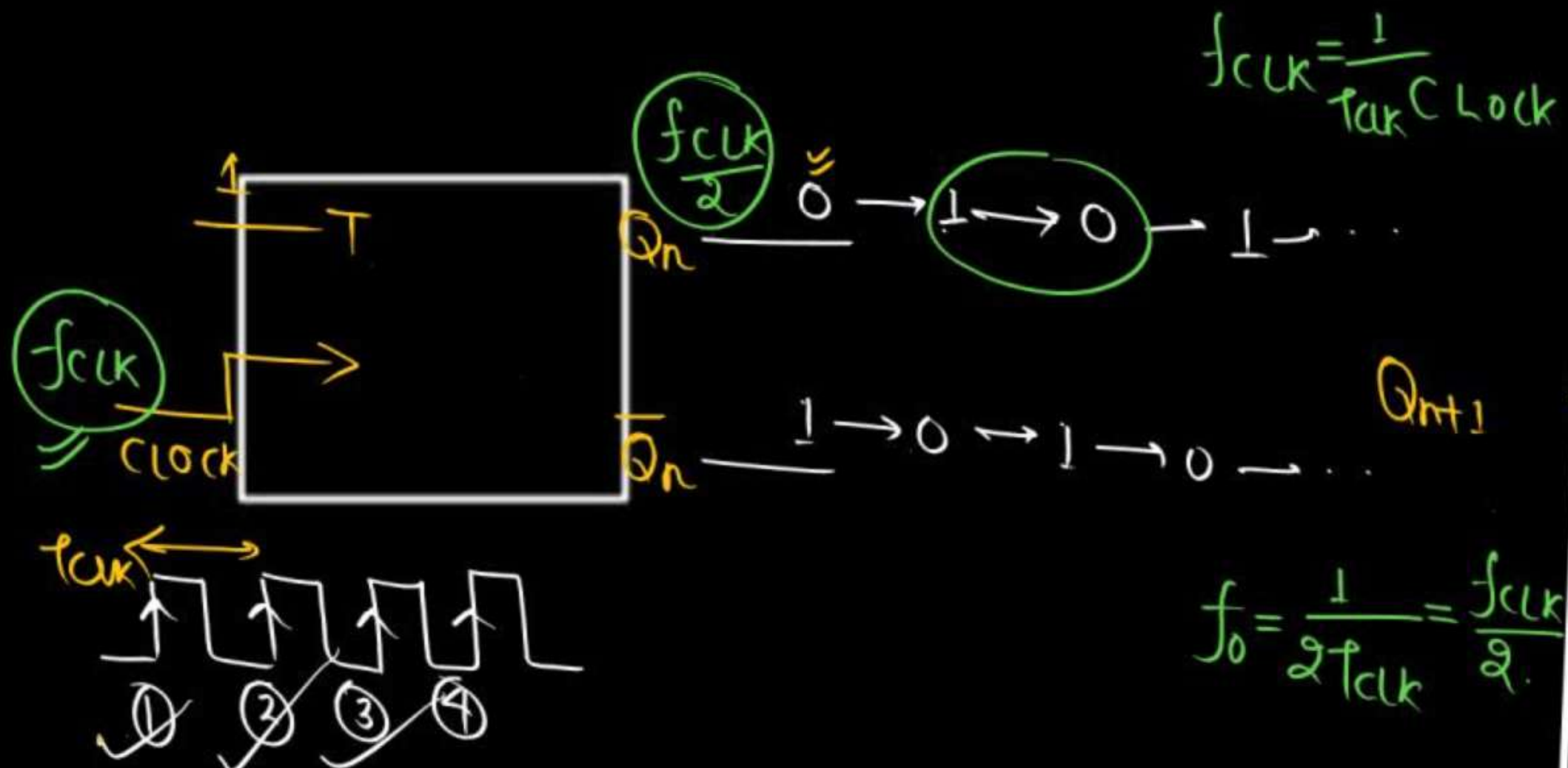


TOGGLE MODE OF THE FLIP FLOP

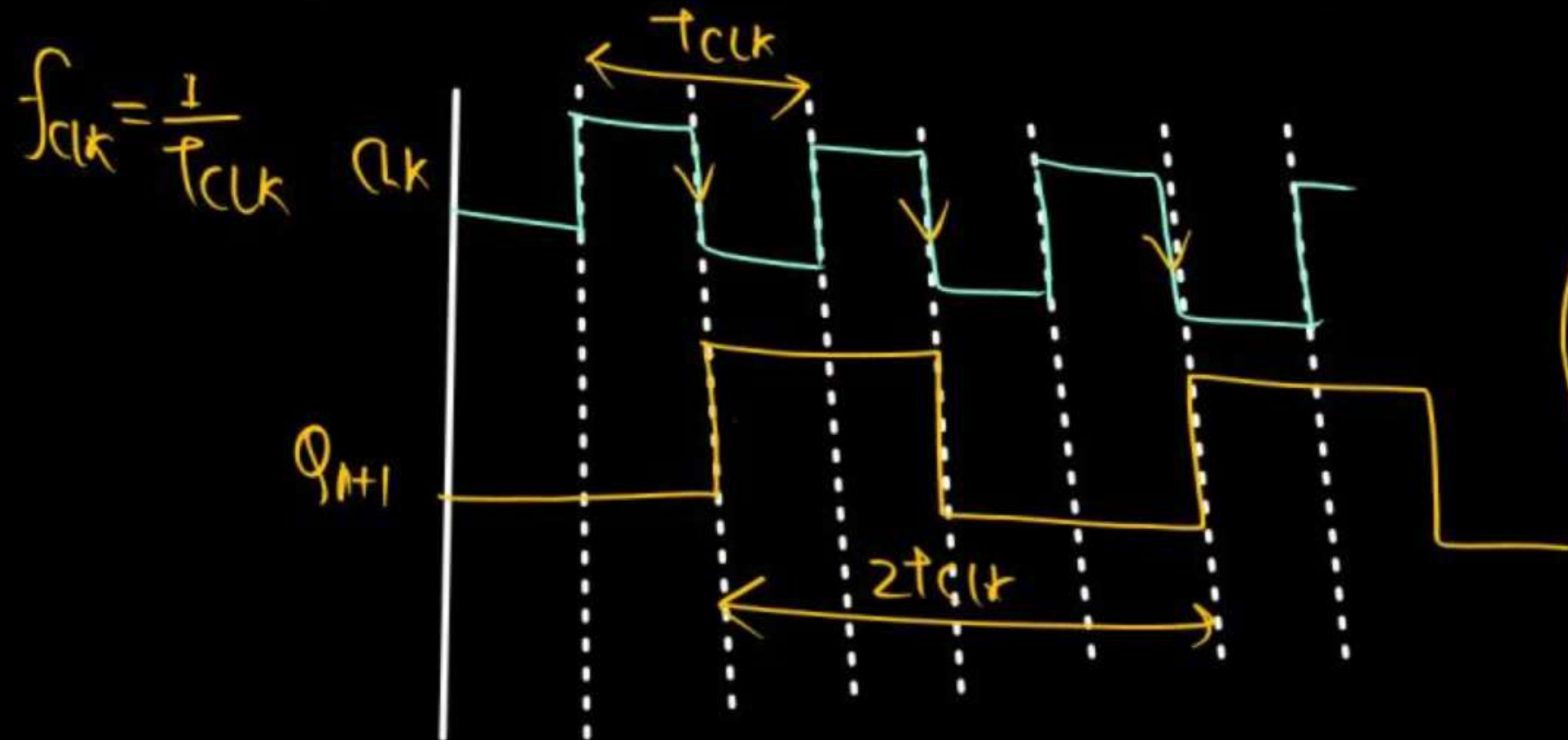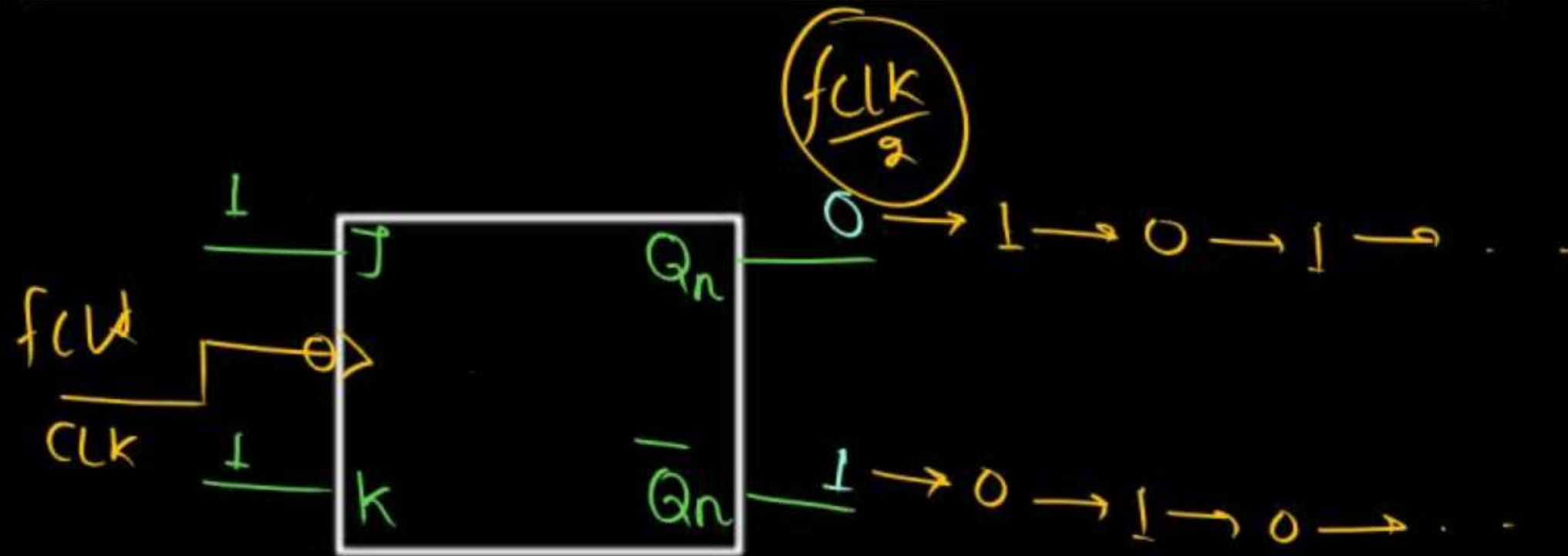


$$f_o = \frac{f_{clk}}{2}$$


TOGGLE MODE OF THE FLIP FLOP

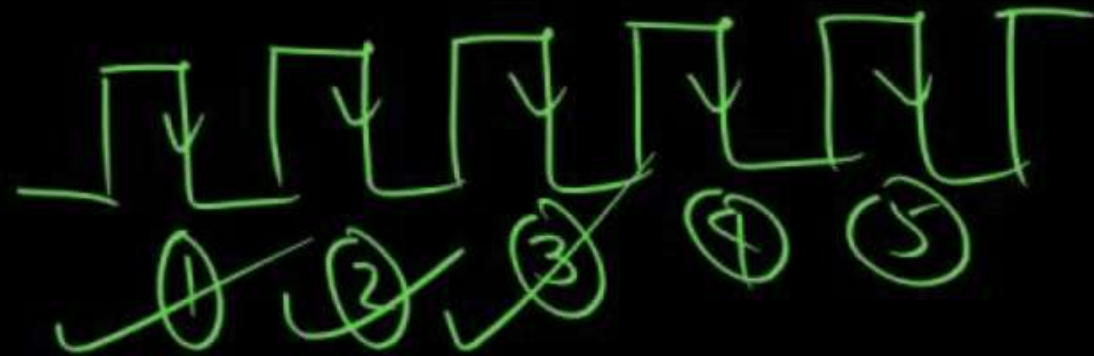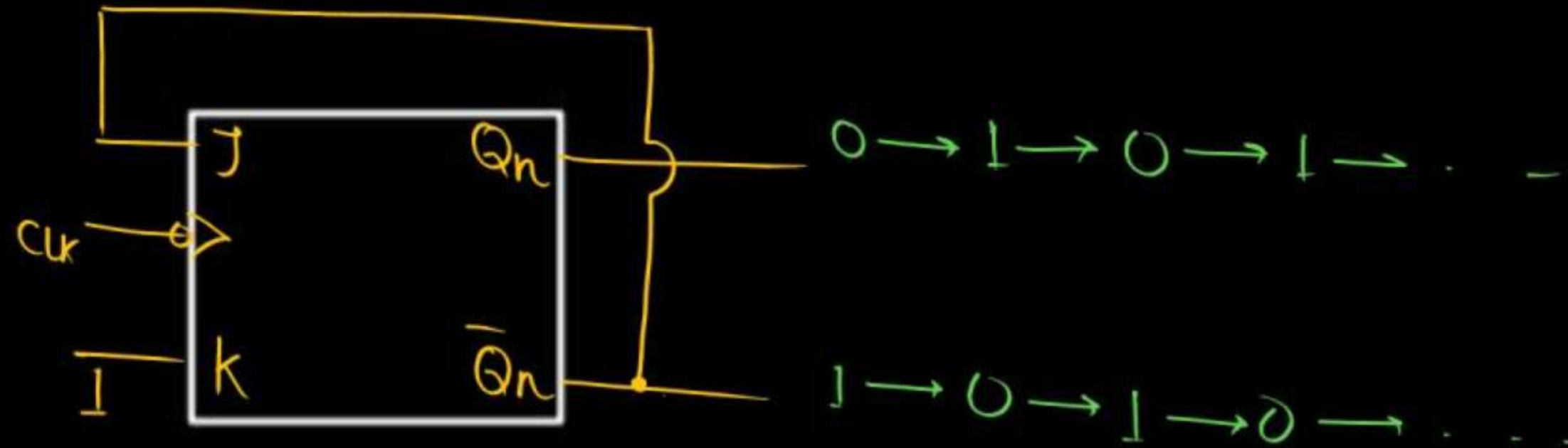


TOGGLE MODE OF THE FLIP FLOP

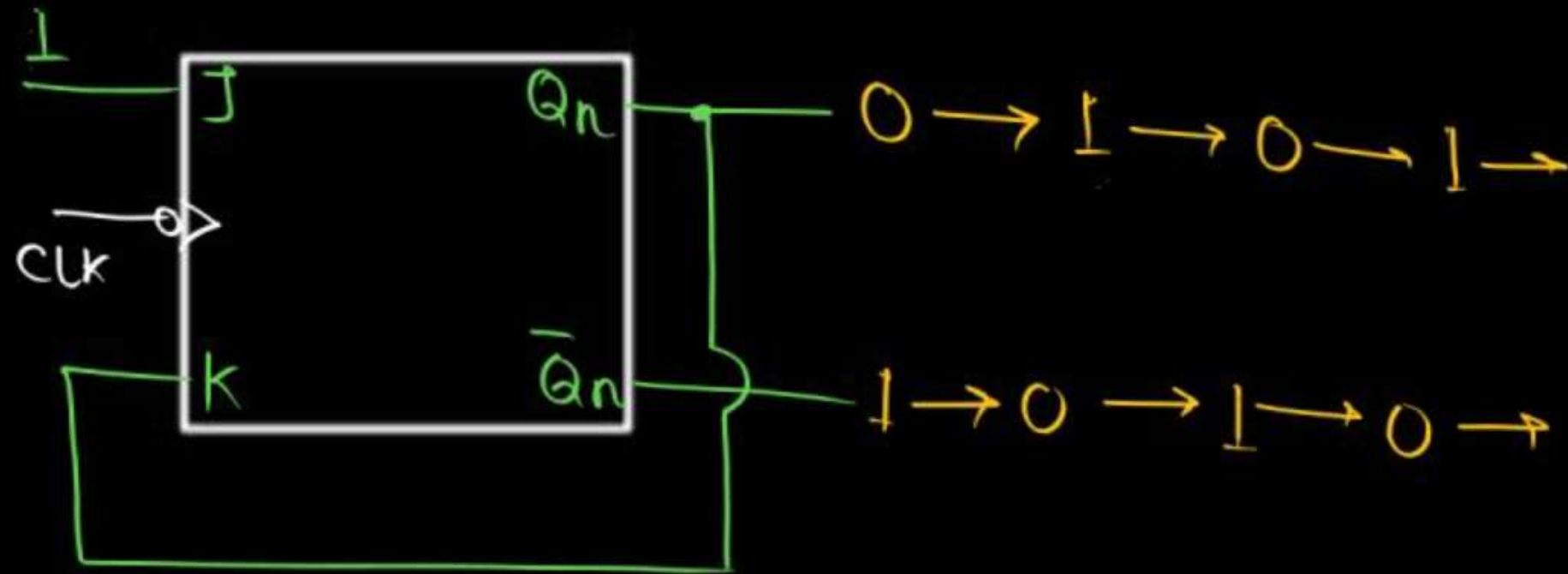


TOGGLE MODE OF THE FLIP FLOP

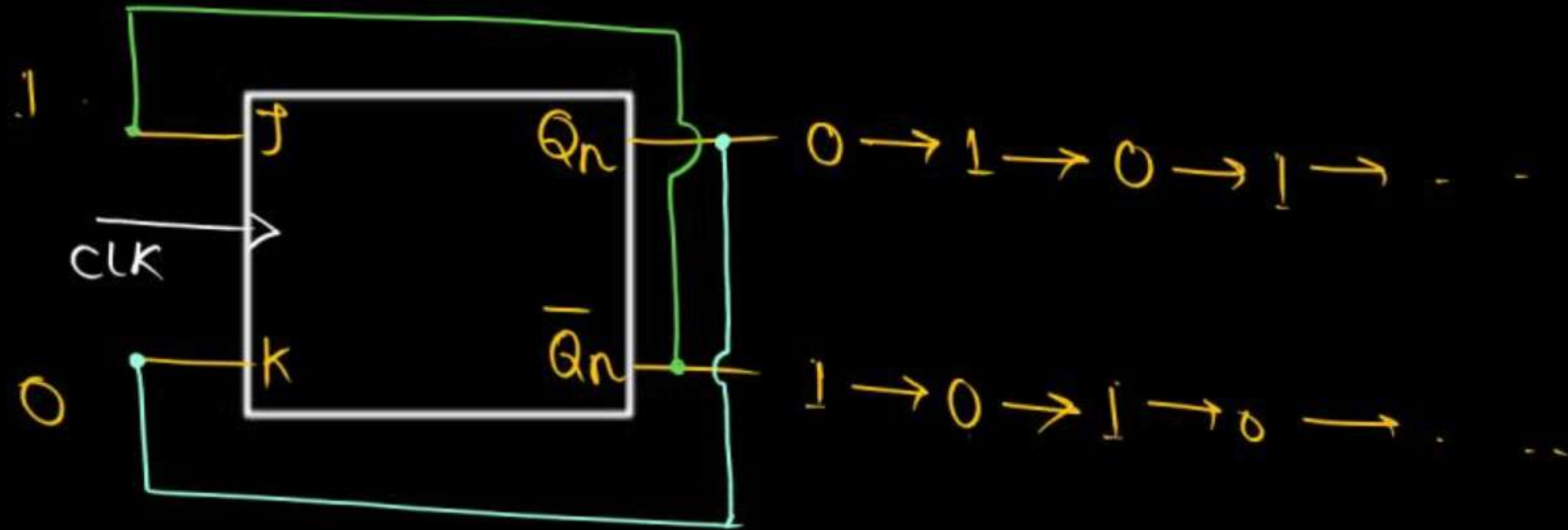

TOGGLE MODE OF THE FLIP FLOP

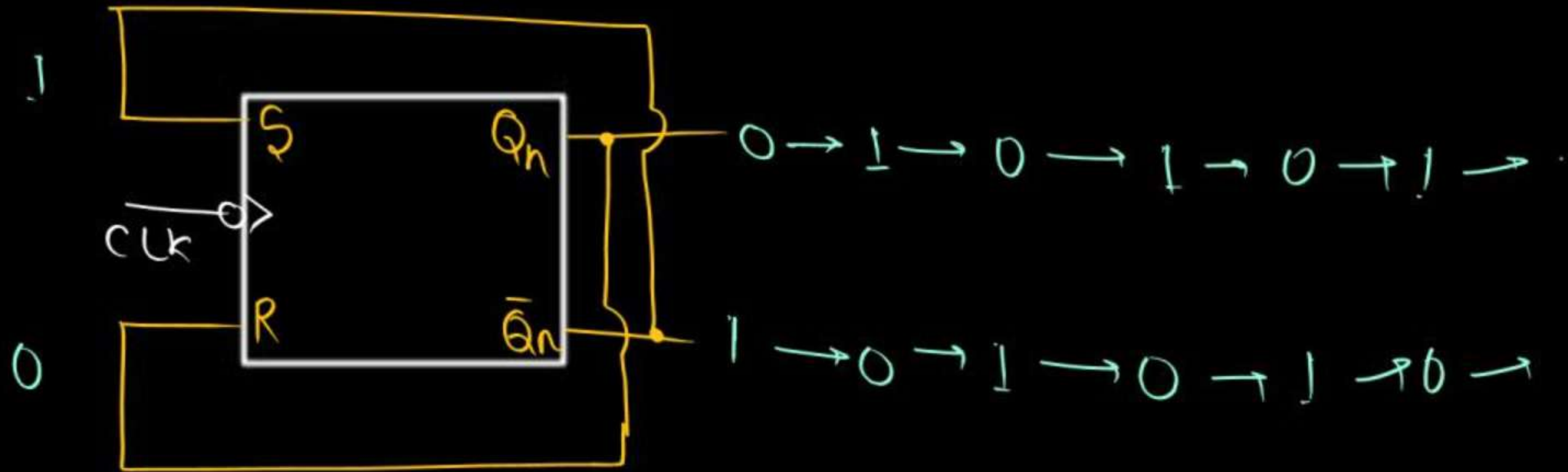

TOGGLE MODE OF THE FLIP FLOP

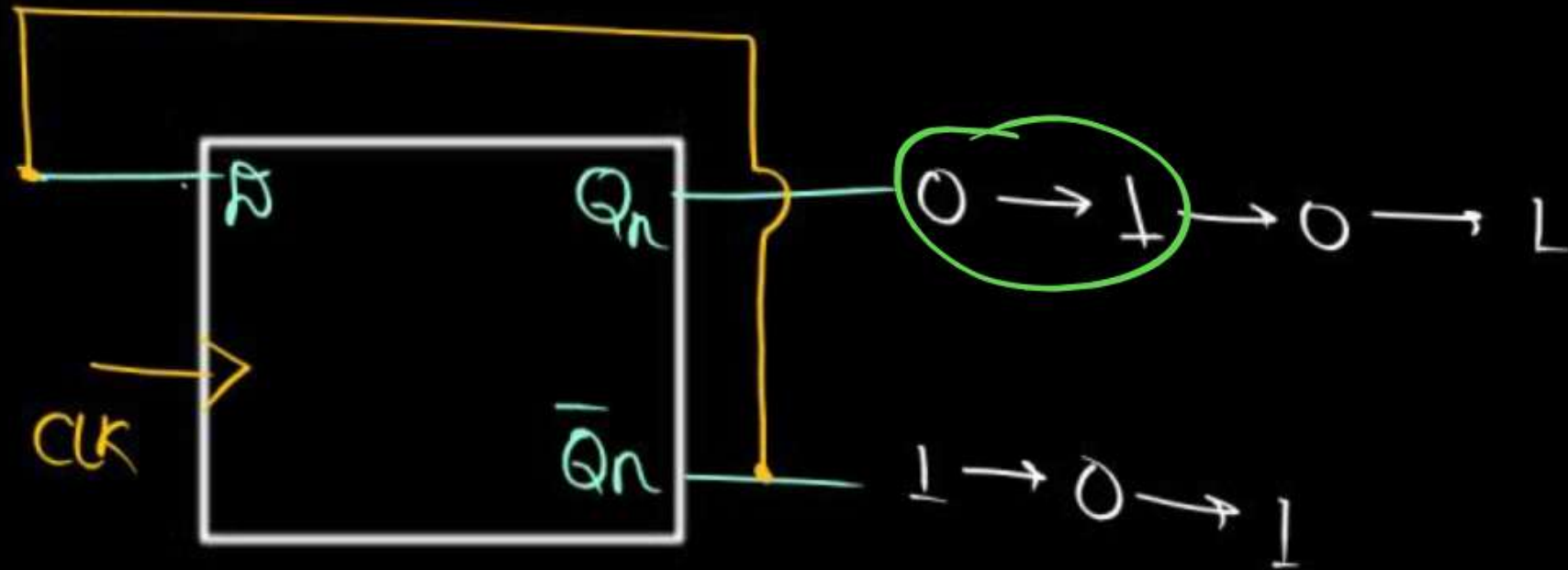

1. Counter are used to count number of clock.
2. Counters are also known as frequency divider circuit.


① Synchronous counter

② Asynchronous counter

UP	DOWN	RANDOM ✓
1	5	1
2	4	3
3	3	2
4	2	5
5	1	4

Synchronous Counters

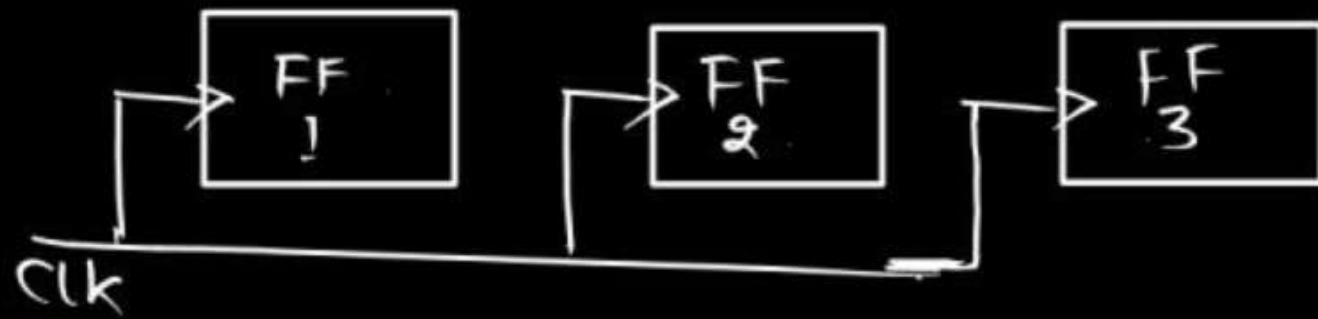1. All the flip flops are connected with same clock.



② fast

③ All type of counting are possible.

④ Ex. Ring, Johnson counter

Asynchronous Counters

1. Only one Flip Flop having External clock and the outputs of that flip flop will be clock for the next flip flop



② slow

③ Generally UP & DOWN counting are possible.

④ Ex. Ripple counter



$$\left\{ \begin{array}{cc} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{array} \right\}$$


Maximum number of states = 2^n

$n \rightarrow$ Number of FF


MOD




Number of states used by the counter.

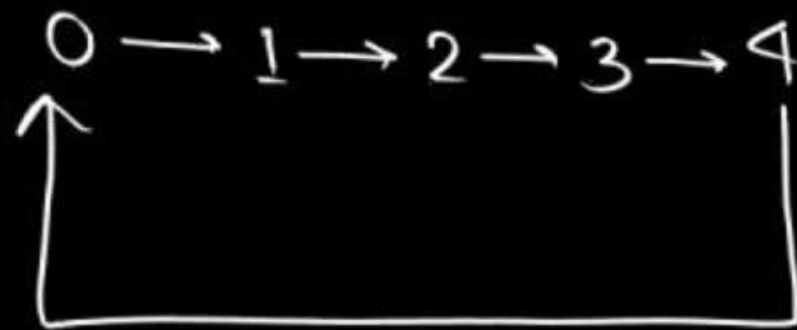

MOD=5

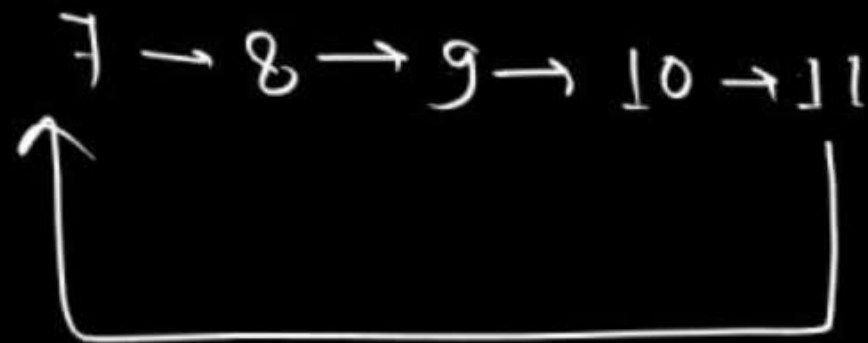

MOD=5

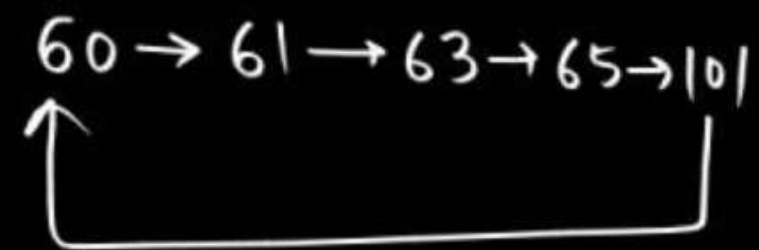

MOD=5

$$\text{MOD}(M) \leq 2^n$$

$$M \leq 2^n$$

$$n \geq \log_2 M$$

Q MOD-10 counter.

no. of FF?

$$M \leq 2^n$$

$$n \geq \log_2 M$$

$$n \geq \log_2 10$$

$$n \geq 3. \text{ something}$$

$$n \approx 4$$

₹.10
NOTE

1.

fin



$$f_{out} = \frac{f_{in}}{M} \checkmark$$

MOD (MxN)

2.

fin



$$f_{out} = \frac{f_{in}}{M \times N}$$

BCD

→ Binary coded decimal

→ Every decimal number are represented by 4 bit.

BCD

100
101
102
103
104
105
105
107
106
109

MOD-10

0 → 0000
1 → 0001
2 → 0010
3 → 0011
4 → 0100
5 → 0101
6 → 0110
7 → 0111
8 → 1000
9 → 1001

BCD

Q When MOD 5 counter is cascaded by MOD 2 counter
Then it will become.

~~(A) MOD-10 counter~~

(B) BCD counter

~~(C) Both (A) & B~~

(D) MOD 7 counter



(E) Sir, Mujhe qta to hai par mai batunga nahi.

$$5 \times 2 = \textcircled{10} \checkmark \checkmark$$

MOD


Asynchronous Counter

3 bit Ripple counter

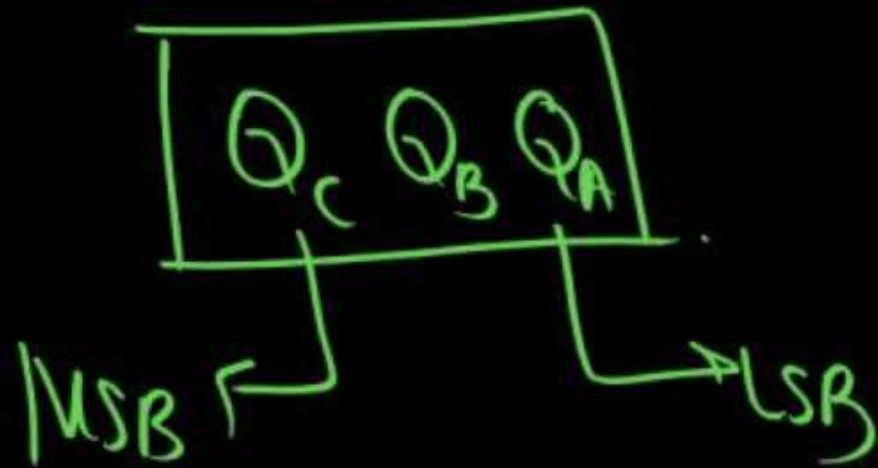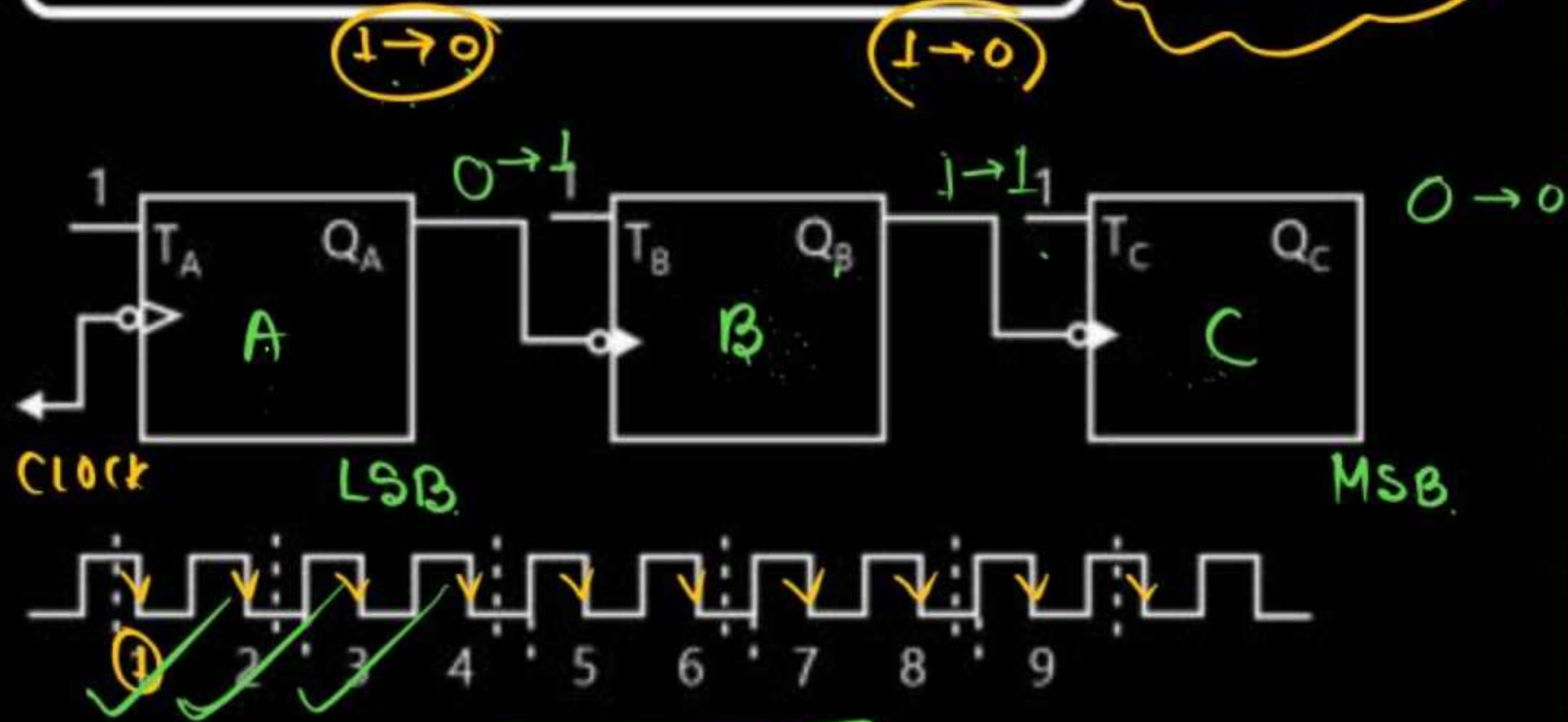


clock	Q _C	Q _B	Q _A
0	0	0	0
1	0	0	1
2	0	1	0
✓ 3	0	1	1
✓ 4	1	0	0
✓ 5	1	0	1
✓ 6	1	1	0
✓ 7	1	1	1
8	0	0	0



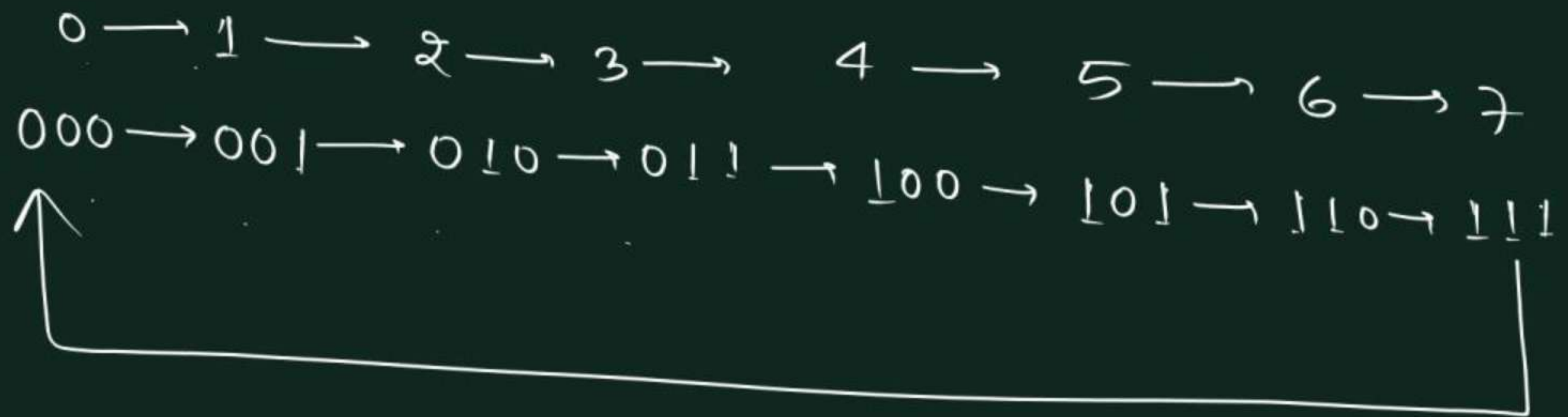

MOD-8 UP RIPPLE COUNTER


Asynchronous Counter

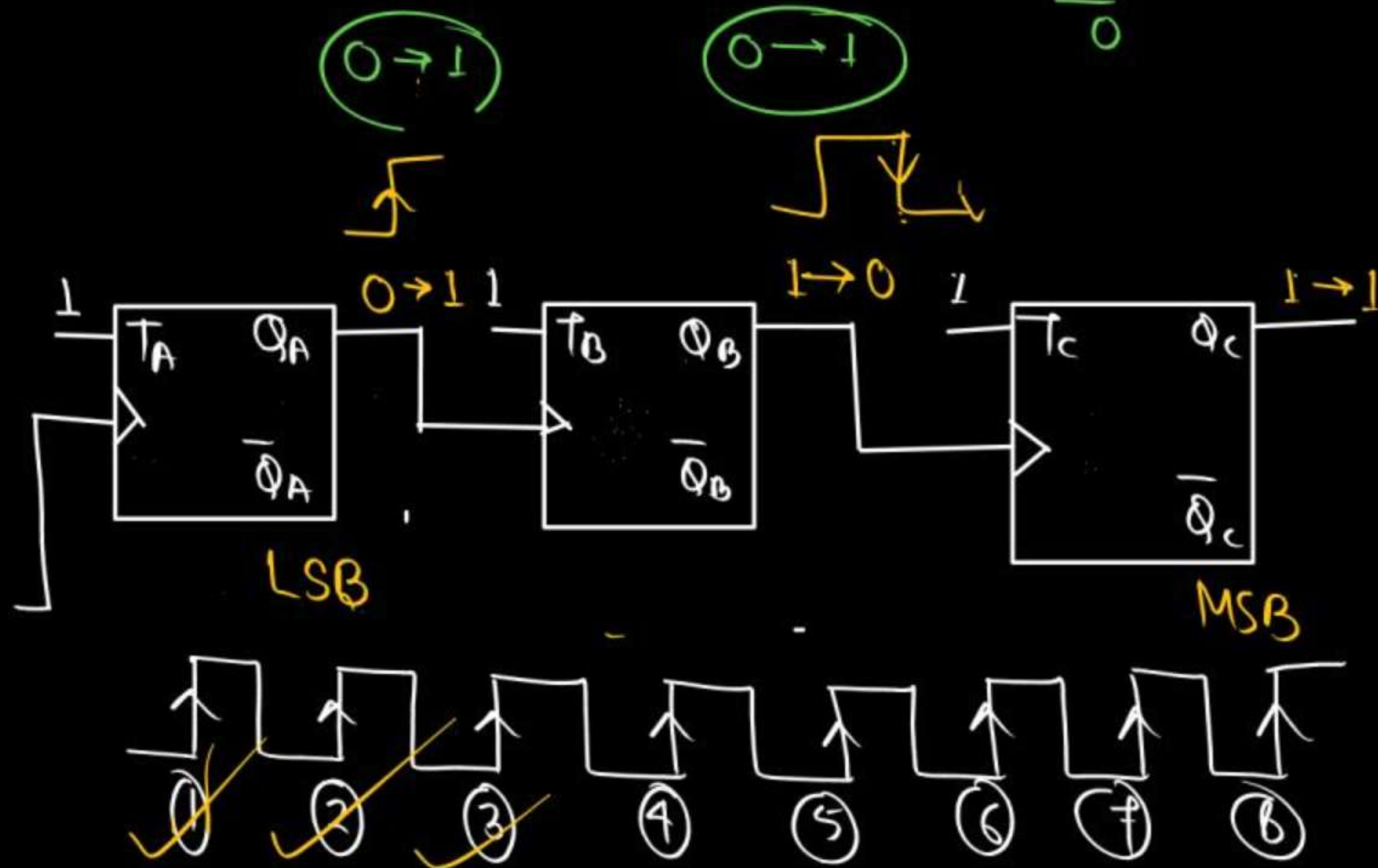

clock	Q_C	Q_B	Q_A
0	0	0	0
1	1	1	1
✓ 2	1	1	0
3	1	0	1
✓ 4	1	0	0
✓ 5	0	1	1
✓ 6	0	1	0
✓ 7	0	0	1
✓ 8	0	0	0



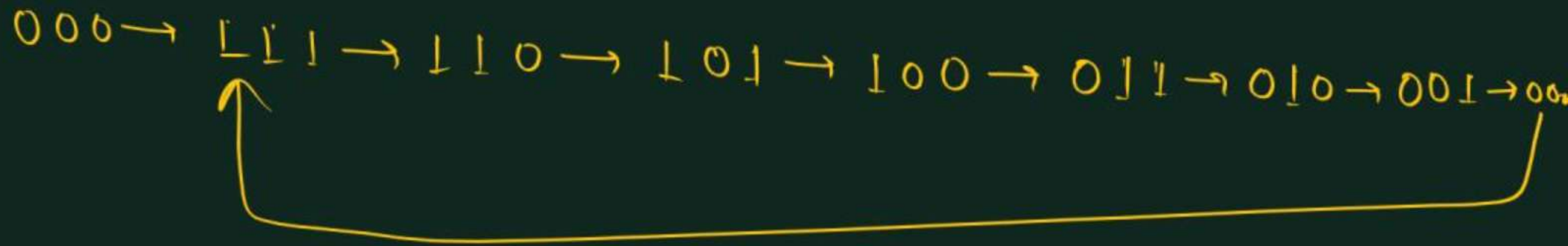000 → 111 → 110 → 101 → 100 → 011 → 010 → 001 → 000



MOD-8 DOWN RIPPLE COUNTER

Asynchronous Counter



Bubble
↓
{ 0 → -ve.
 \overline{Q} → -ve



-ve → UP
+ve → DOWN

clock	Q_C	Q_B	Q_C
0			
1			
2			
3			
4			
5			
6			
7			
8			

Asynchronous Counter



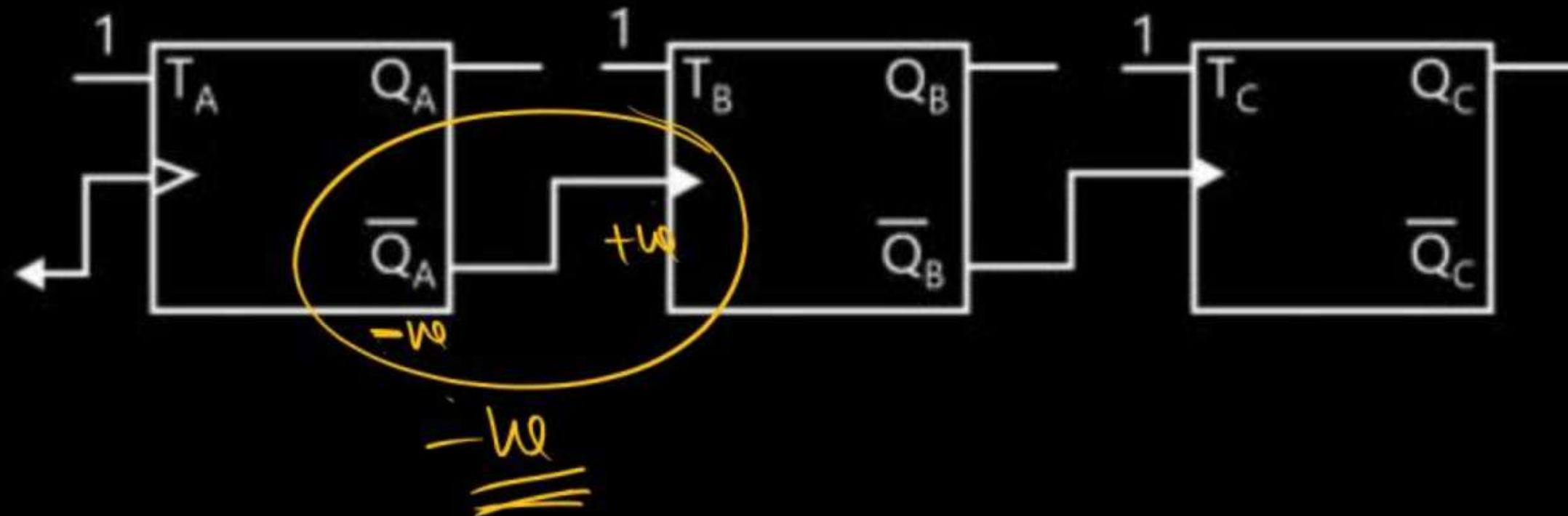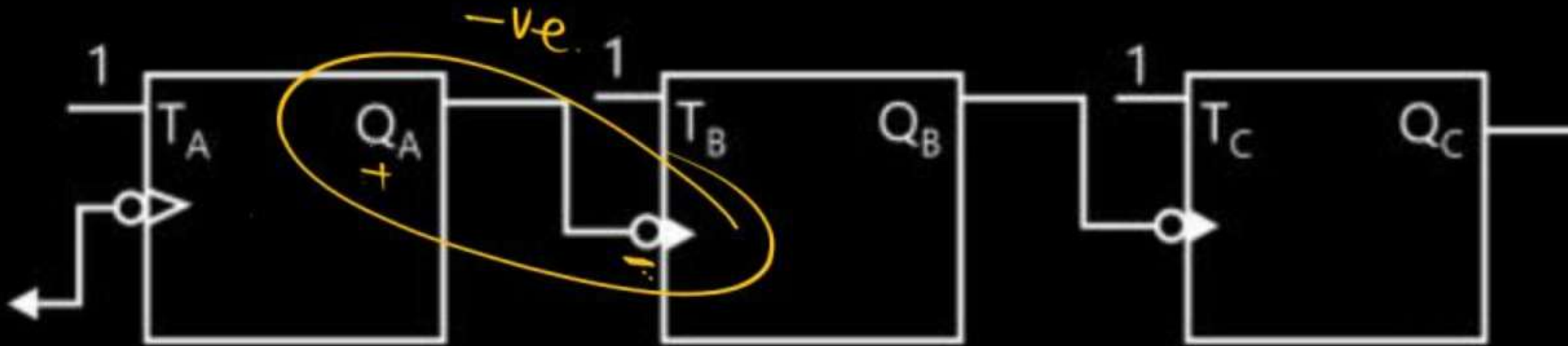
$-ve \rightarrow \underline{UP}$
 $+ve \rightarrow \underline{DOWN}$




Asynchronous Counter



$$n \rightarrow 2^n$$

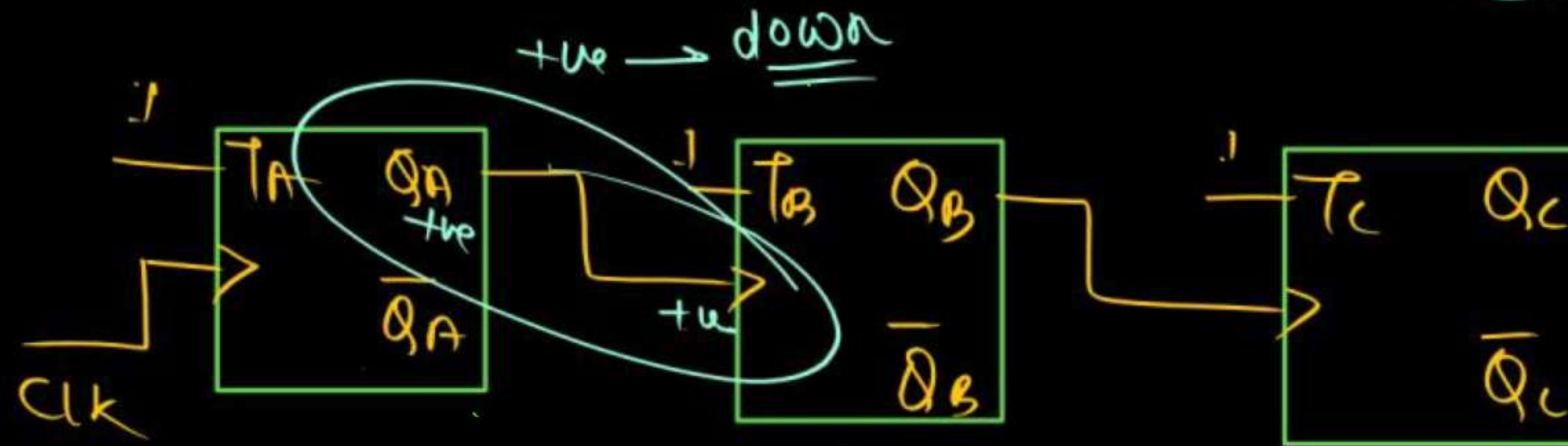


DOWN

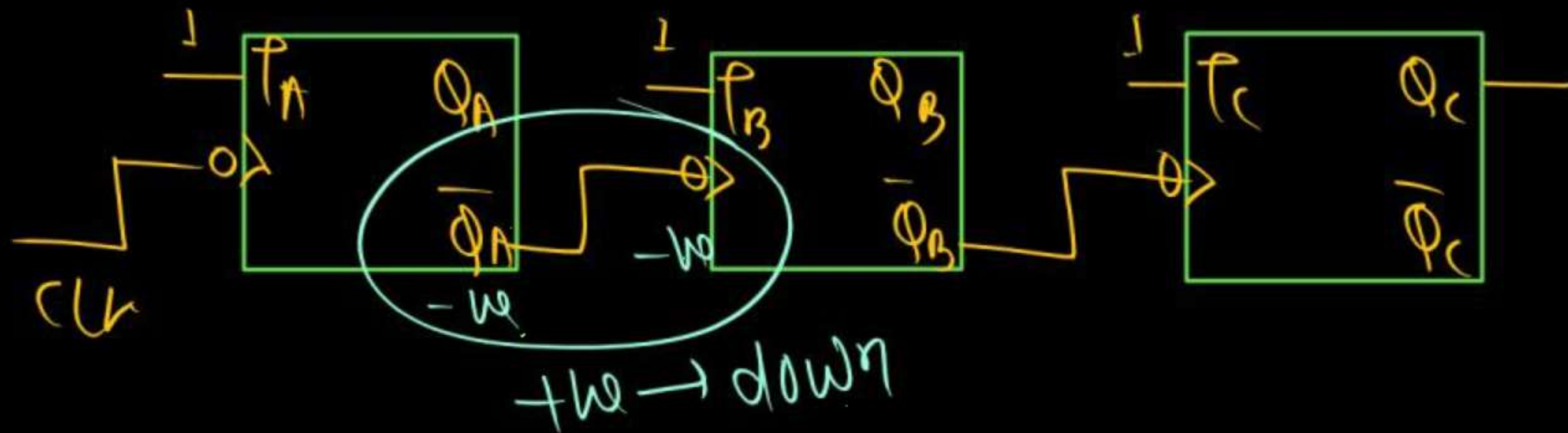

Down counter

Asynchronous Counter

$$\text{MOD} = 2^4 = 16$$

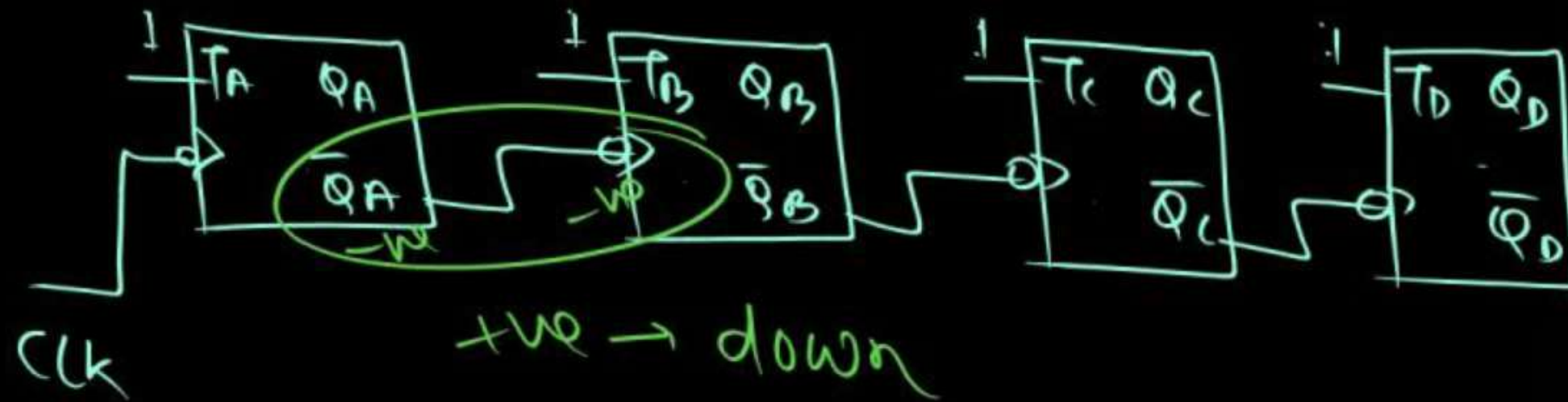

MOD 16- down Ripple counter

clock	Q_C	Q_B	Q_C	Clr
0				
1				
2				
3				
4				
5				
6				
7				
8				

Asynchronous Counter



LDL

11PM

1000

500

200

100

50

20


10

5


2

0

clock	Q _C	Q _B	Q _C	Clr
0				
1				
2				
3				
4				
5				
6				
7				
8				

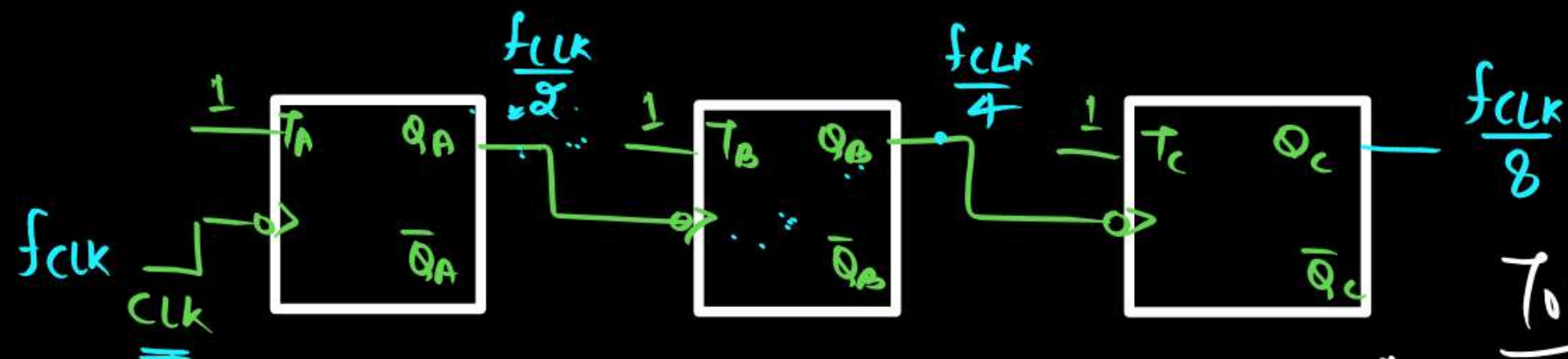



$$T = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$


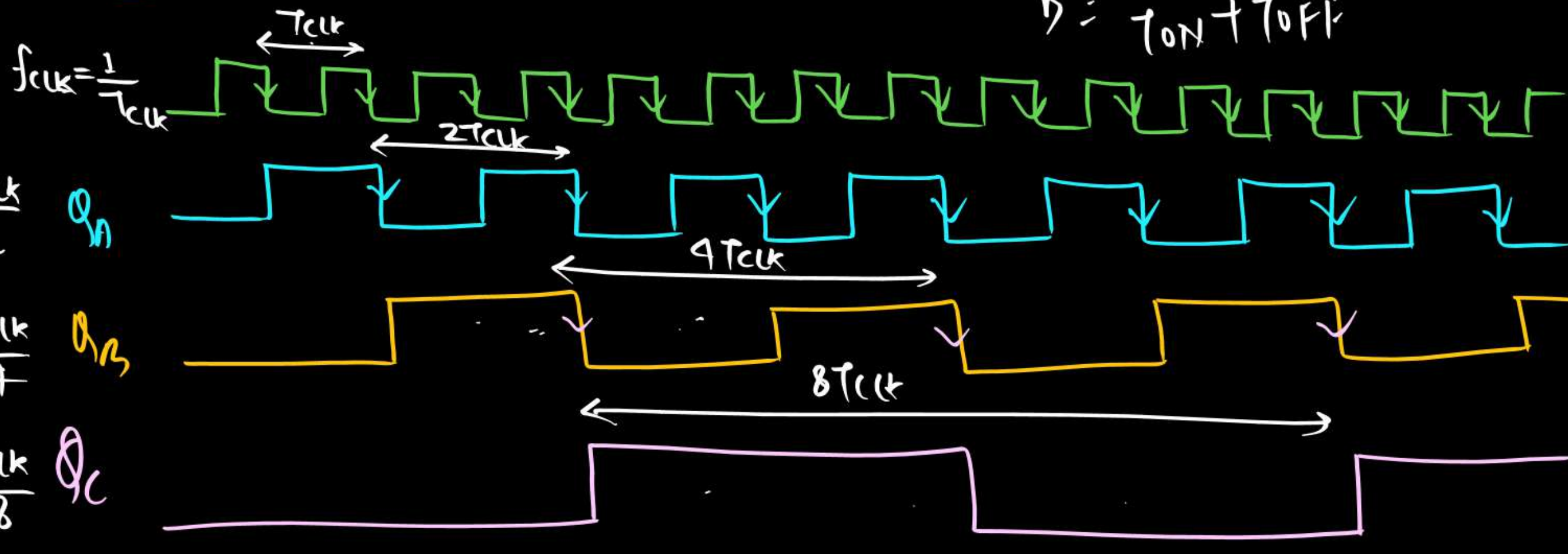


$$f_{QA} = \frac{1}{2T_{clk}} = \frac{f_{clk}}{2} \quad Q_A$$

$$f_{QB} = \frac{1}{4T_{clk}} = \frac{f_{clk}}{4} \quad Q_B$$
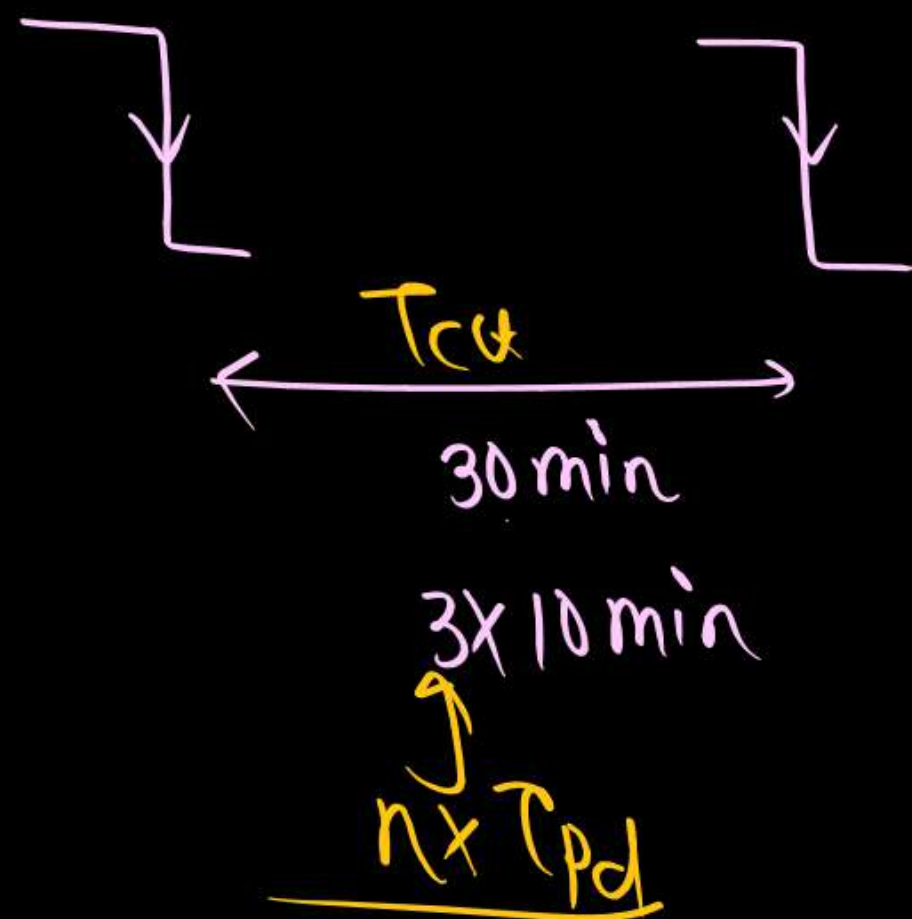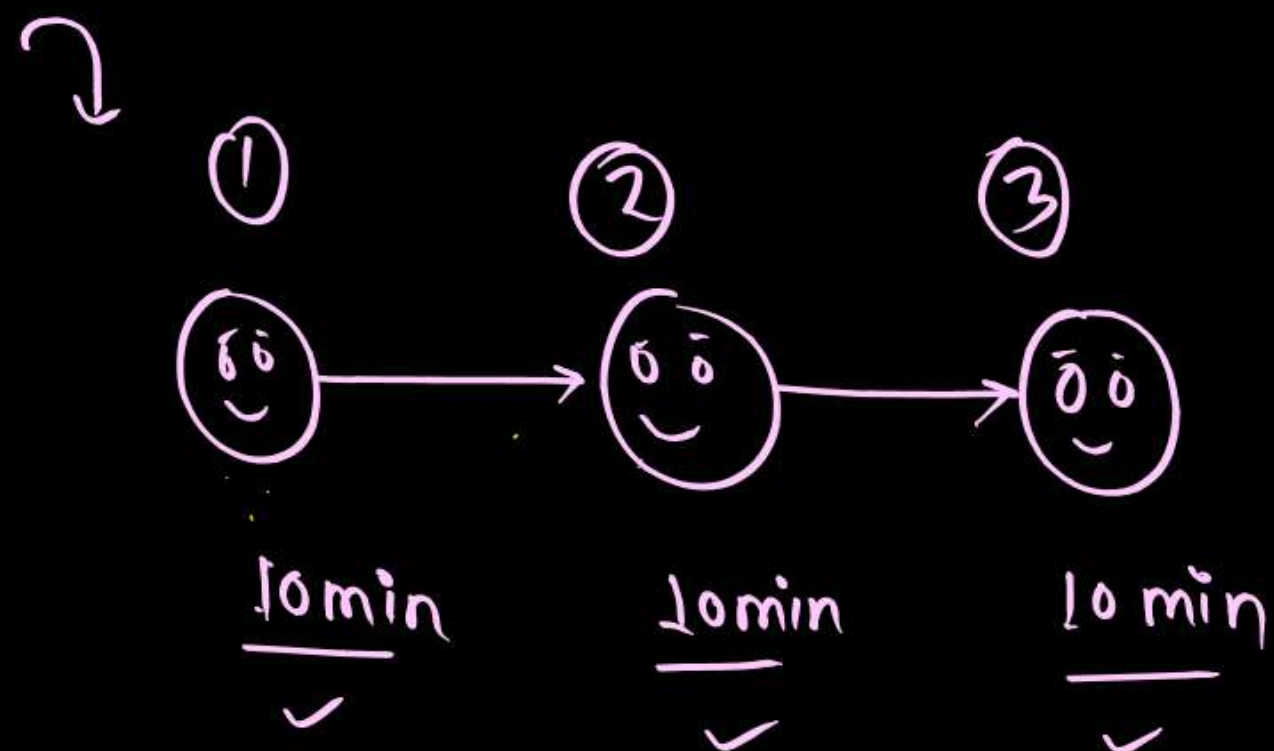
$$f_{QC} = \frac{1}{8T_{clk}} = \frac{f_{clk}}{8} \quad Q_C$$



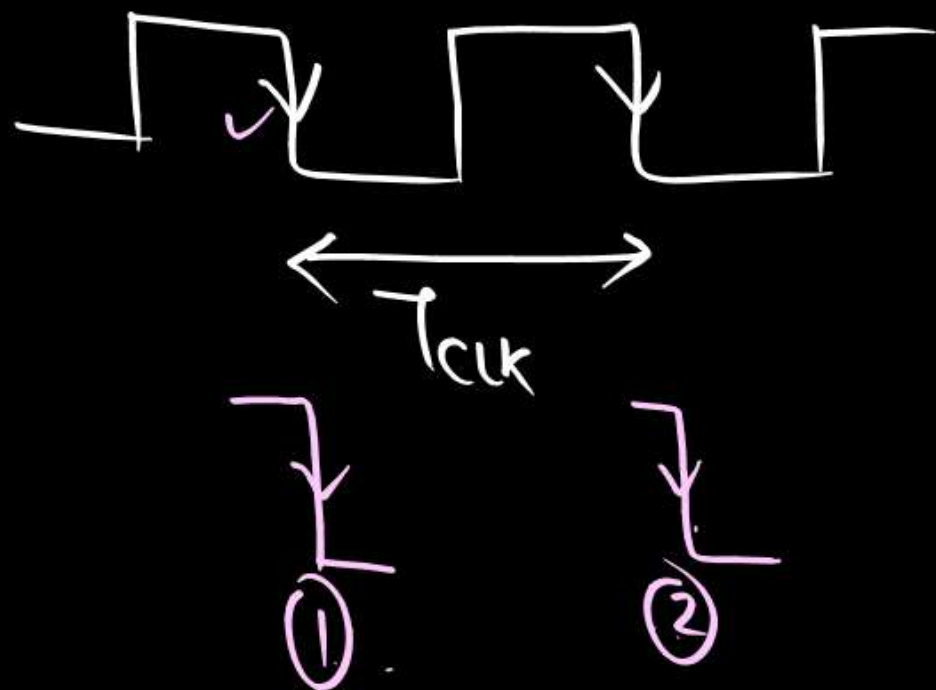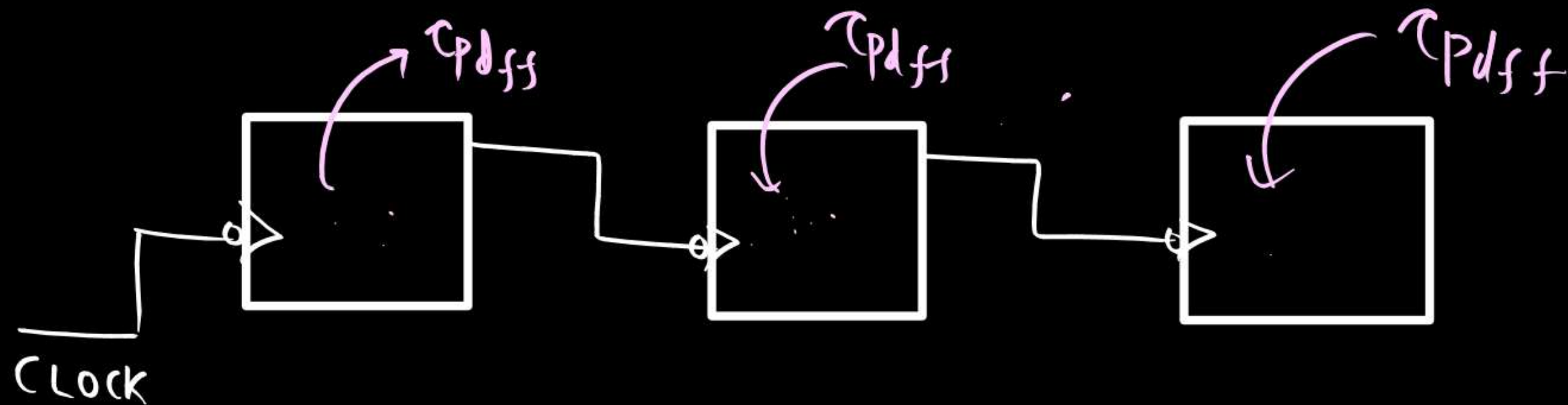

$$T_{clk} \geq 3\tau_{pdff}$$



"n" FF

$$T_{clk} \geq n \cdot \tau_{pdf}$$

$$\frac{1}{T_{clk}} \leq \frac{1}{n \cdot \tau_{pdf}}$$

$$f_{clk} \leq \frac{1}{n \cdot \tau_{pdf}}$$

$$(f_{clk})_{max} = \frac{1}{n \cdot \tau_{pdf}}$$

$T_{clk} \geq \text{Sum of Delay of all the FF}$



Q (Asynchronous)
In BCD counter. Delay of FF is 10 ns.

all FF are identical.

Find the clock frequency for stable operation?

$$\begin{aligned} f_{clk} &\leq \frac{1}{n \cdot \tau_{pdf}} \\ &\leq \frac{1}{4 \times 10 \times 10^{-9}} \text{ Hz} \\ &\leq \frac{10^9}{4 \times 10} \text{ Hz} \\ &\leq \frac{1000 \times 10^6}{4 \times 10} \text{ Hz} \end{aligned}$$

$$(f_{clk})_{\max} = 25 \text{ MHz}$$


$$\text{MOD} = 10$$

$$M \leq 2^n$$


$$n \geq \log_2 M$$

$$n \approx 4$$

Reset (clr)

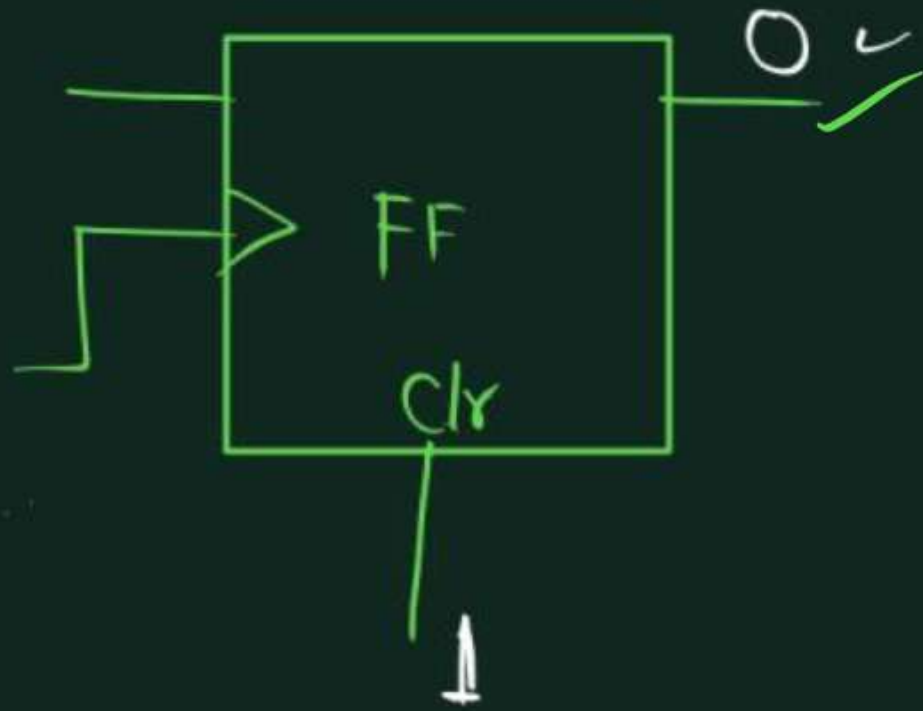


Preset

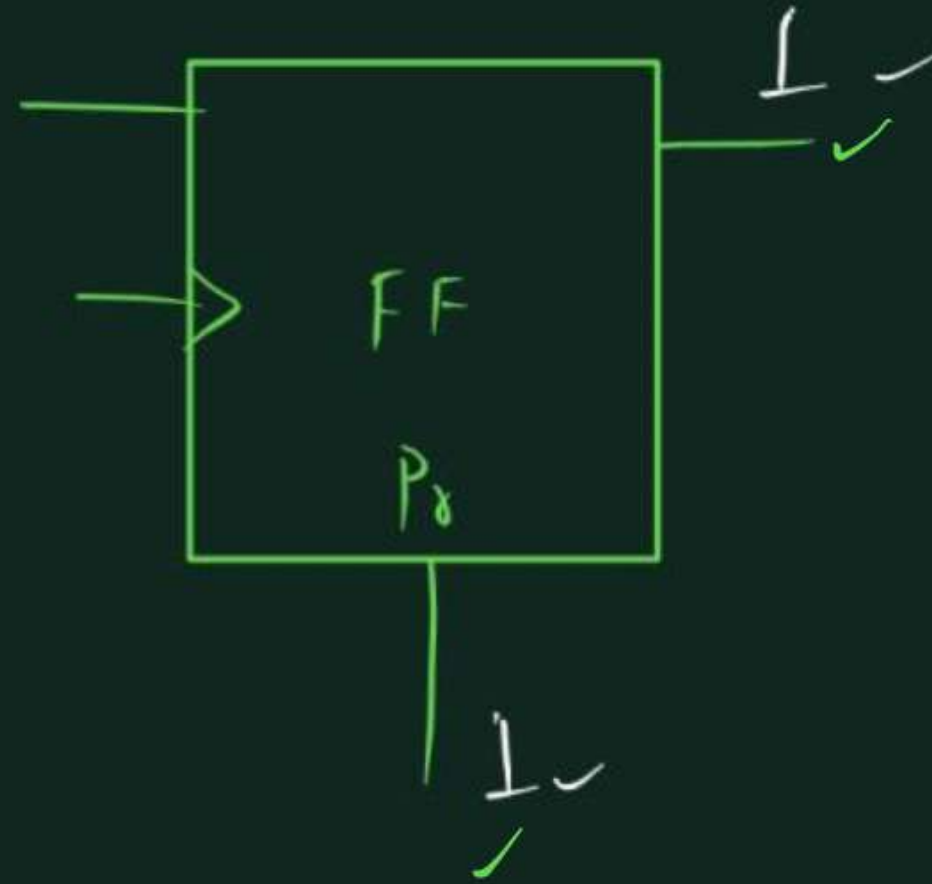

Asynchronous Counter

MOD-5 UP COUNTER

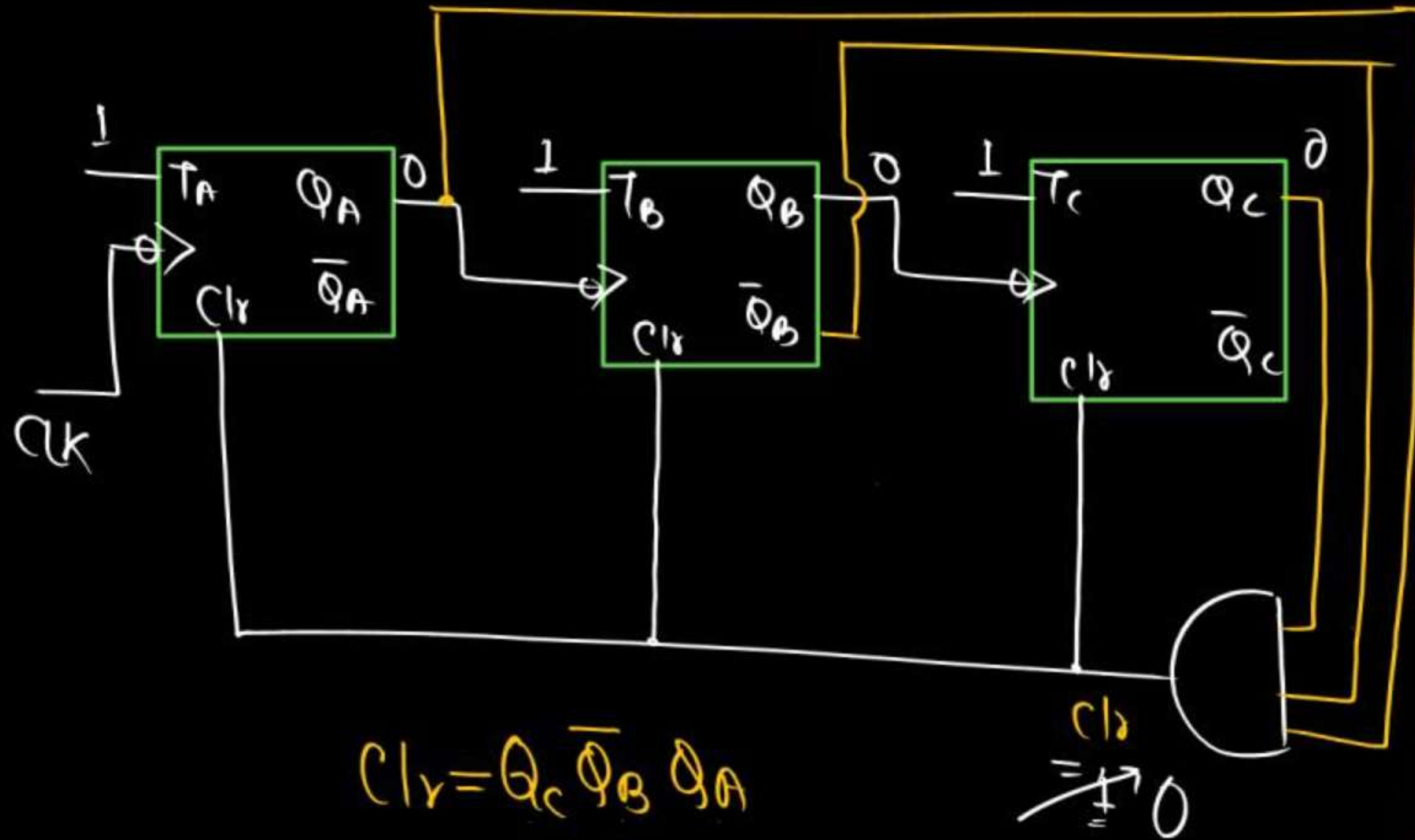


$$C1_r = Q_c \overline{Q_B} Q_A$$

UP) $Clr = Q_1 \cdot \bar{Q}_3 \cdot Q_2$
 101 → 5 MOD



clock	Q_C	Q_B	Q_A	$Clr = Q_C \bar{Q}_B Q_A$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1 0	0 1	1 0	1 0
6	0	0	1	0
7	0	1	0	0
8	0	1	1	0

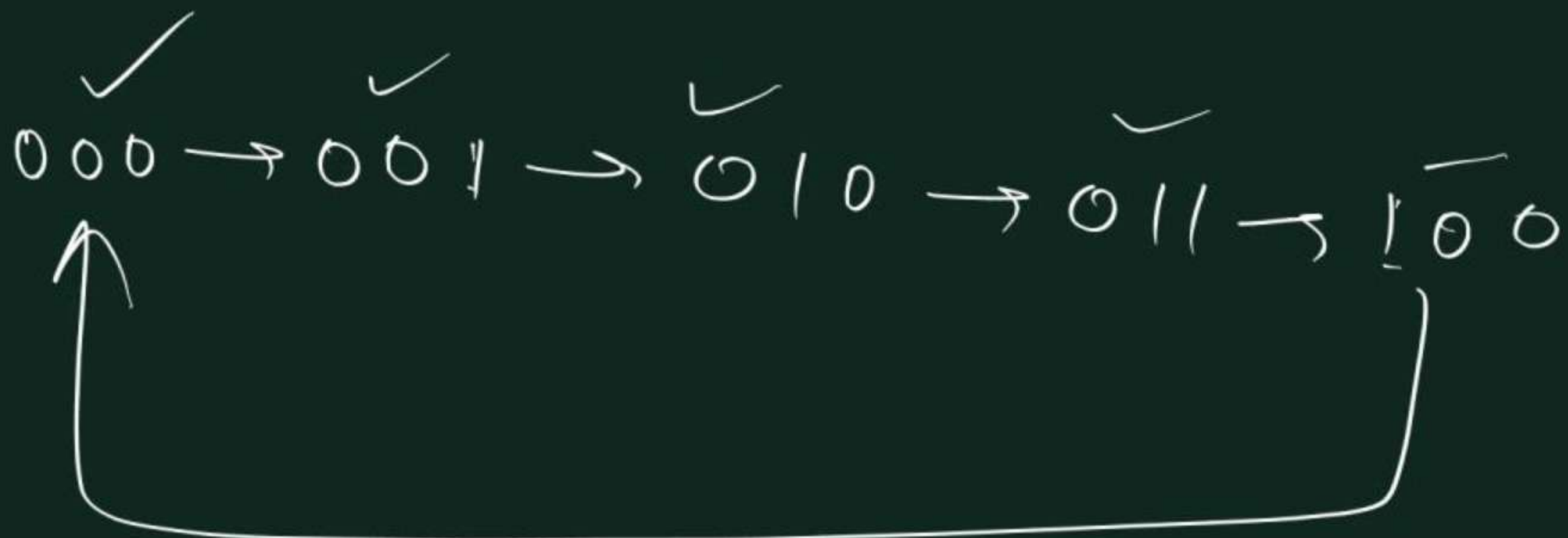

$\text{MOD} = 5$

जीत की खातिर बस जूनून चाहिए,
जिसमें उबाल हो ऐसा खून चाहिए,
ये आसमान भी आ जाएगा ज़मीन पर,
बस इरादों में जीत की गूँज चाहिए।

Asynchronous Counter




clock	Q_C	Q_B	Q_C	Clr
0				
1				
2				
3				
4				
5				
6				
7				
8				



$1010 \rightarrow 10 \rightarrow \underline{MOD}$

SHANDAR ♡

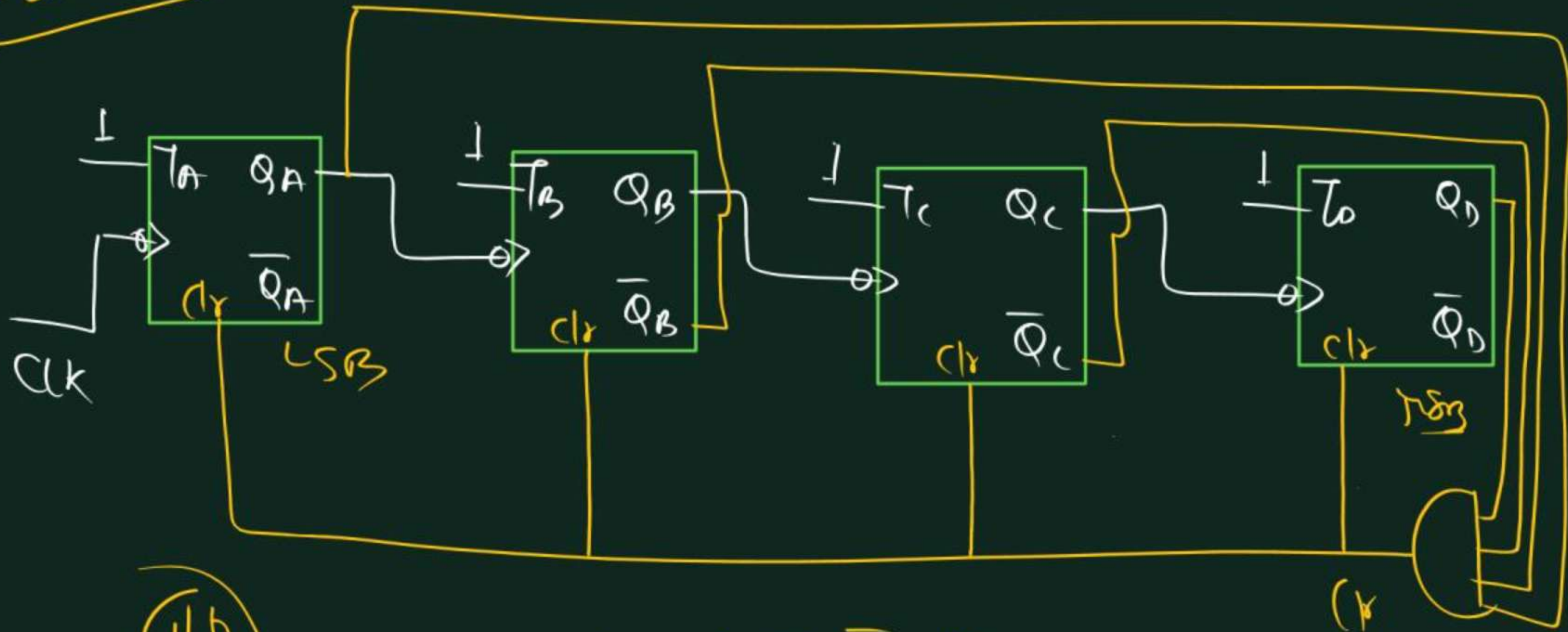

VP

$$Clr = Q_D \bar{Q}_C \bar{Q}_B Q_A$$

1 0 0 1 → 9

MOD-9 UP
Ripple counter


Asynchronous Counter



$Q_b Q_c Q_d Q_n$

Q Design a BCD counter

Clr =

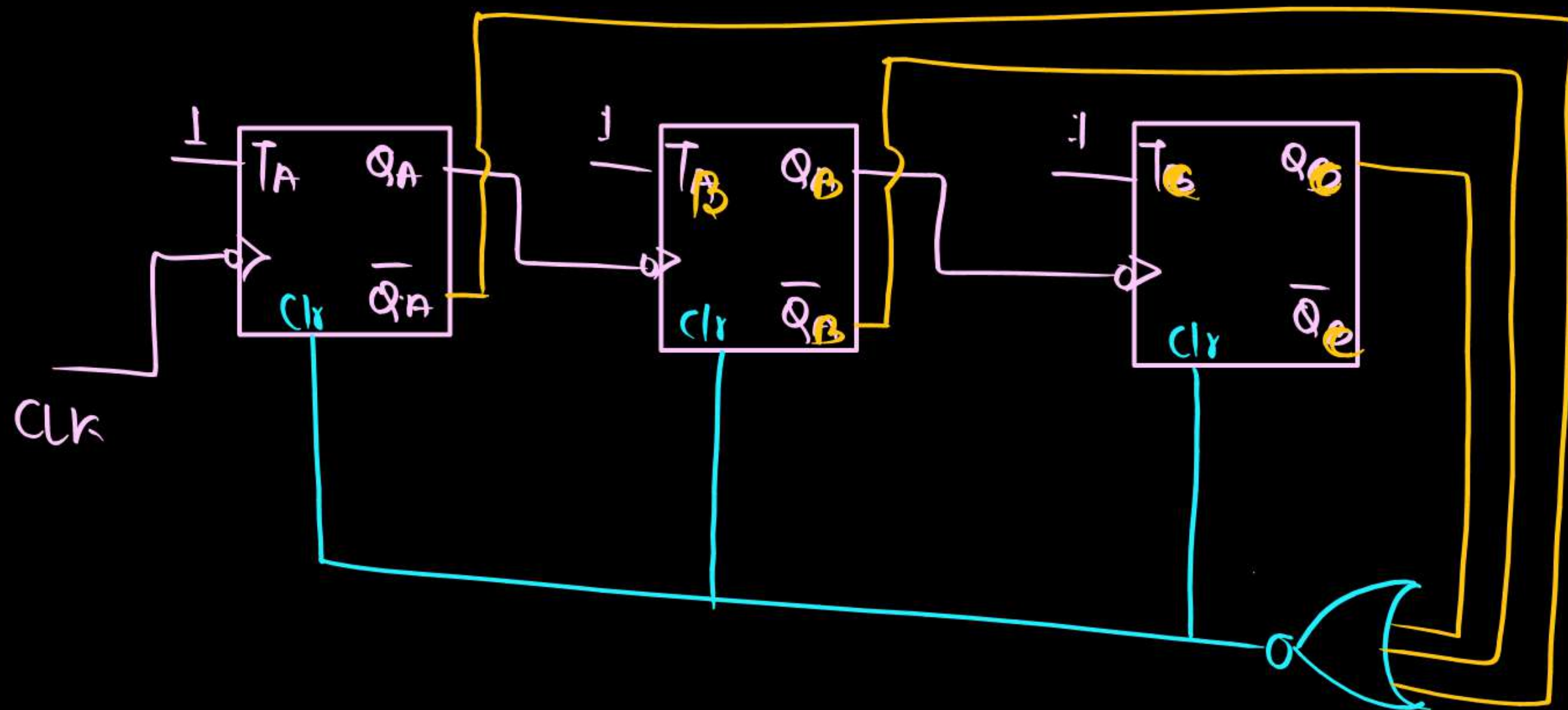

$$\text{clr} = \overline{Q_C + \overline{Q_B} + \overline{Q_A}}$$

$$\text{clr} = \overline{Q_C} \cdot Q_B \cdot Q_A$$

0 1 1 \rightarrow MOD-3

Full-UP=DOWN

$8-5=(3)$

$$C/r = Q_C \bar{Q}_B Q_A$$

101


Synchronous counter.



① Ring counter.

② Johnson counter.

RING COUNTER :->

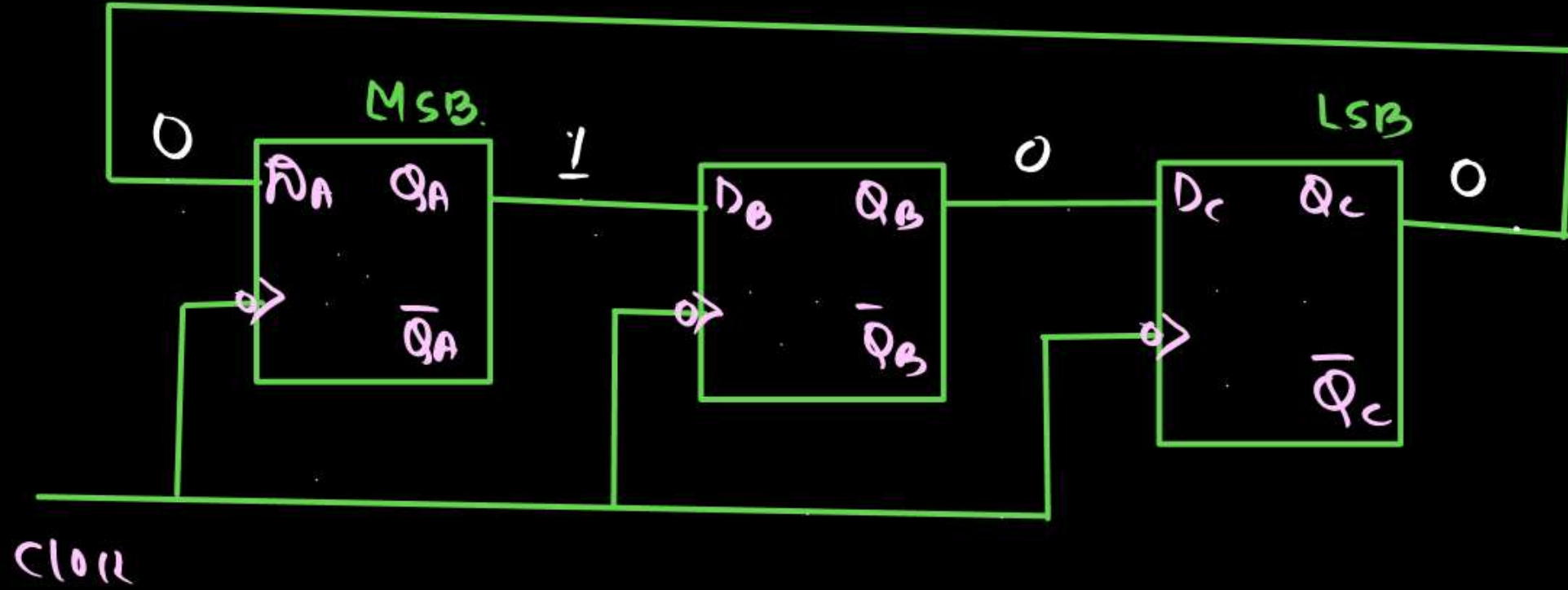

Clock	Q _A	Q _B	Q _C
0	0	0	0
1	1	0	0
2	0	1	0
3	0	0	1
4	1	0	0

100
010
001

MOD=3



$$\left\{ \begin{array}{cccc} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{array} \right\} \text{Mod } (4)$$




N bit Ring counter.

MOD = N.




Symbolic Representation:

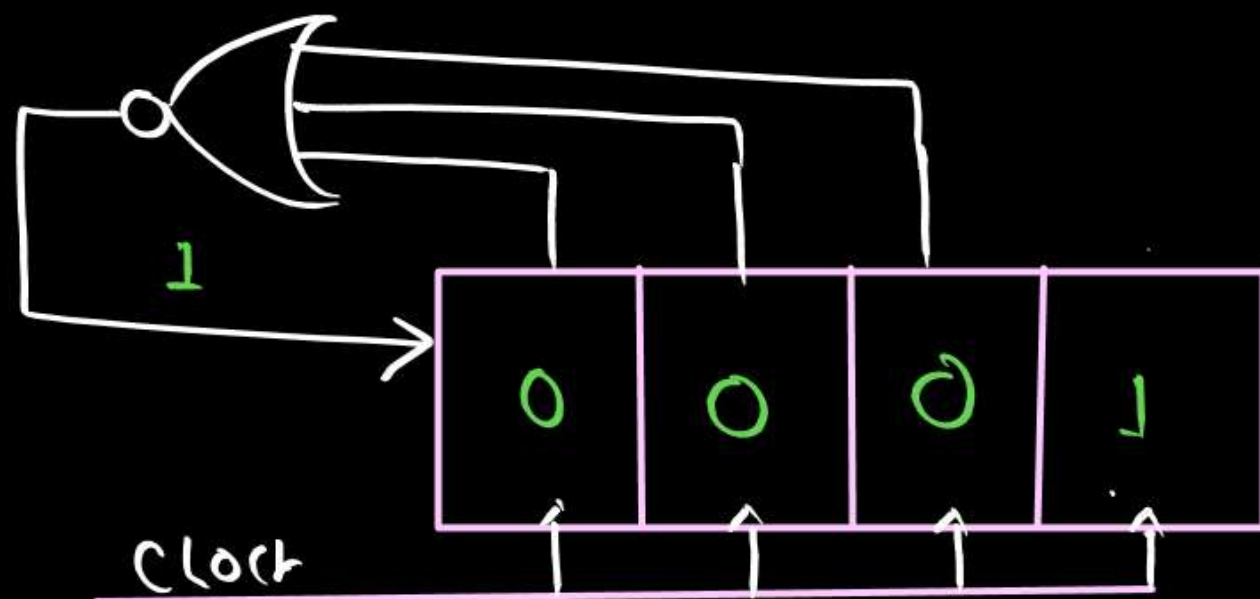

0000 → 1000 → 0100 → 0010 → 0001

Clock	Q _A	Q _B	Q _C	Q _D
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0

Self starting Ring counter.

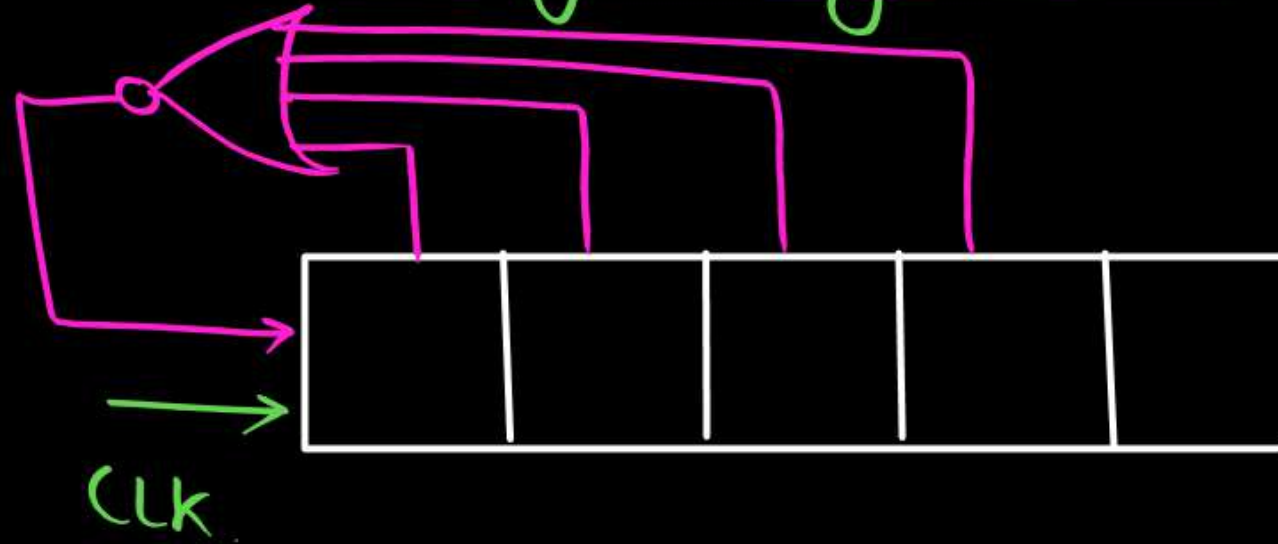




Johnson counter

↳ Twisted Ring counter

↳ Creeping counter

↳ Mobies counter

↳ Walking counter

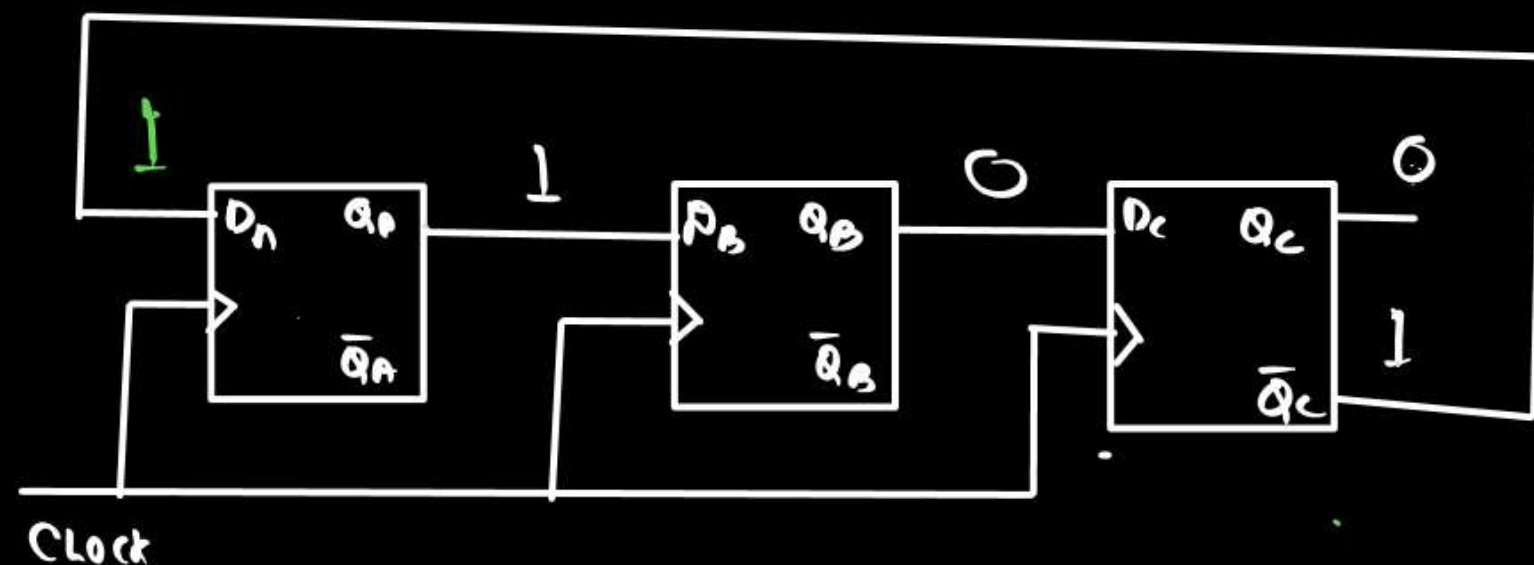

Clock	Q_A	Q_B	Q_C
0	0	0	0
1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1
6	0	0	0
7	1	0	0

$$\left\{ \begin{array}{ccc} 0 & 0 & 0 \\ 1 & 0 & 0 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \end{array} \right\} \text{MOD } 8$$



4 bit Johnson counter

N'bit Johnson counter


8 MOD {


0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1

Used state = MOD = $2N$



Symbolic Representation

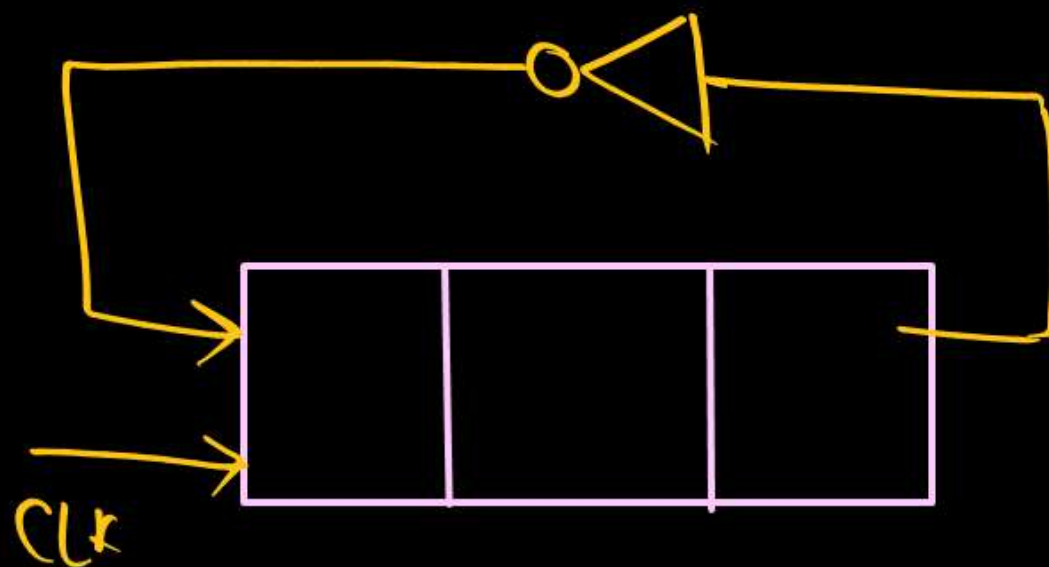

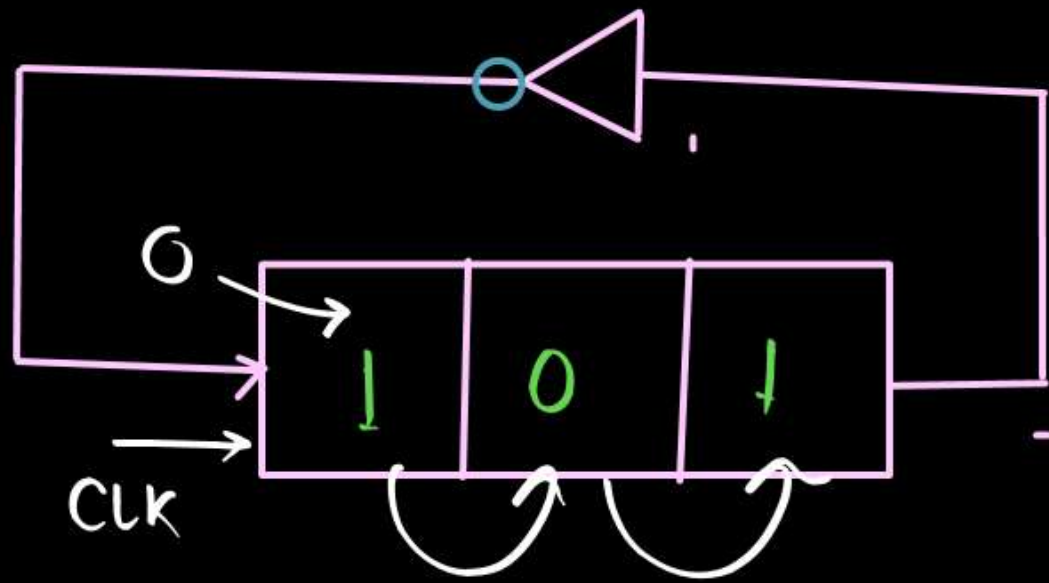


LOCKOUT PROBLEM

Clock	Q ₁	Q ₂	Q ₃
0	0	1	0
1	1	0	1
2	0	1	0
3	1	0	1
4	0	1	0

Lock
into unused
state

	000
	001
Unused →	010
	011
	100
Unused →	101
	110
	111

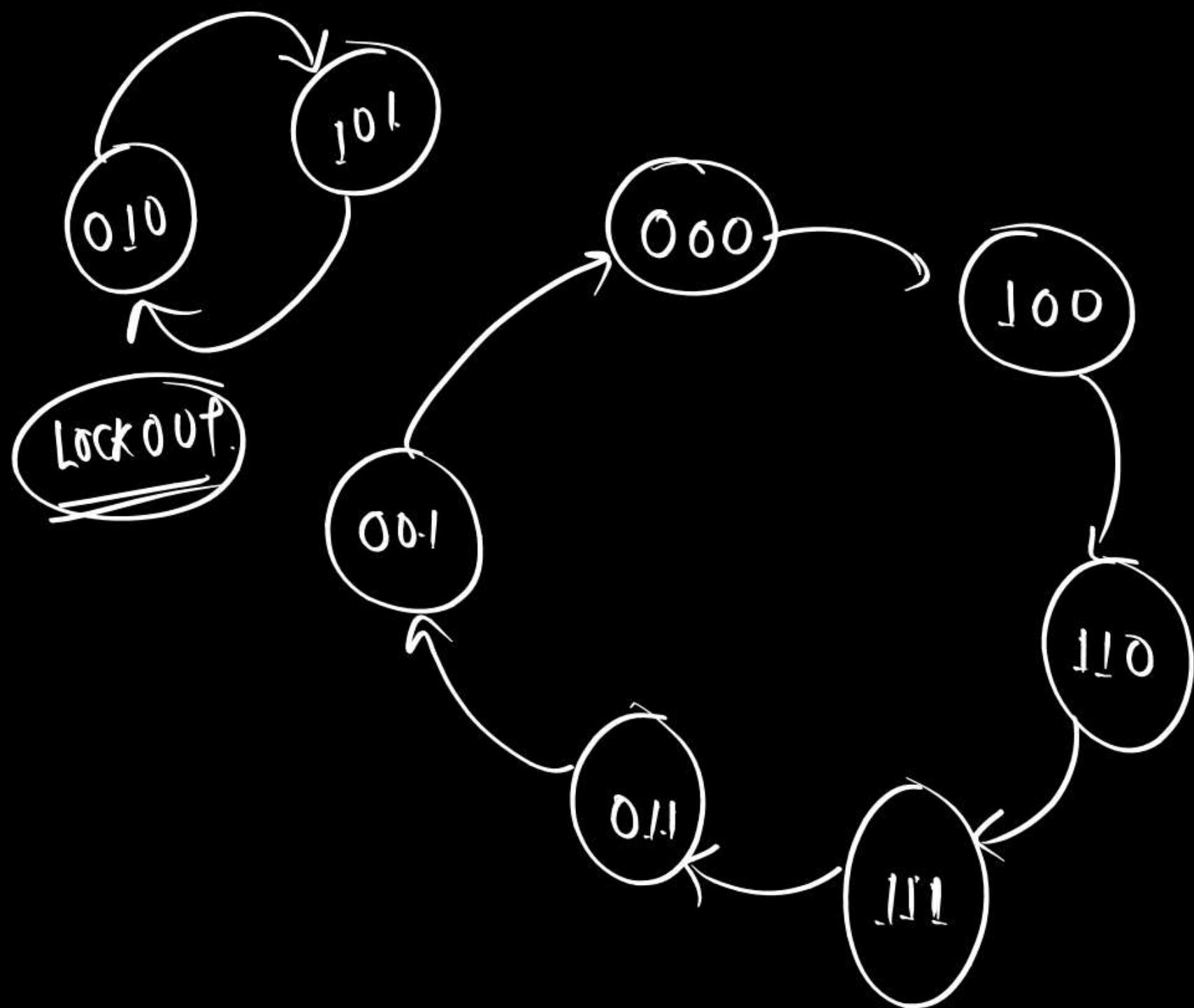



Synchronous Counter Design.

Step 1 : Write the present and Next State.

Step 2. Write the excitation table of Flip-Flop.

Step 3. Write the Logical expression

Step 4. Minimization

Step 5 → Hardware Implementation.



Q Design a synchronous counter by using T-FF which count

$\{ \overset{Q_1 Q_0}{00} \rightarrow 01 \rightarrow 10 \rightarrow 11 \}$

Step 1

Step 2

Q_1	Q_0	Q_1^+	Q_0^+	T_1	T_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

Step 3.
Step 4.]

$$T_1 = \bar{Q}_1 Q_0 + Q_1 Q_0$$

$$T_1 = Q_0 (\bar{Q}_1 + Q_1)$$

$$\boxed{T_1 = Q_0}$$


$$\boxed{T_0 = 1}$$



Step 5:

$$T_1 = Q_0$$


$$T_0 = !$$

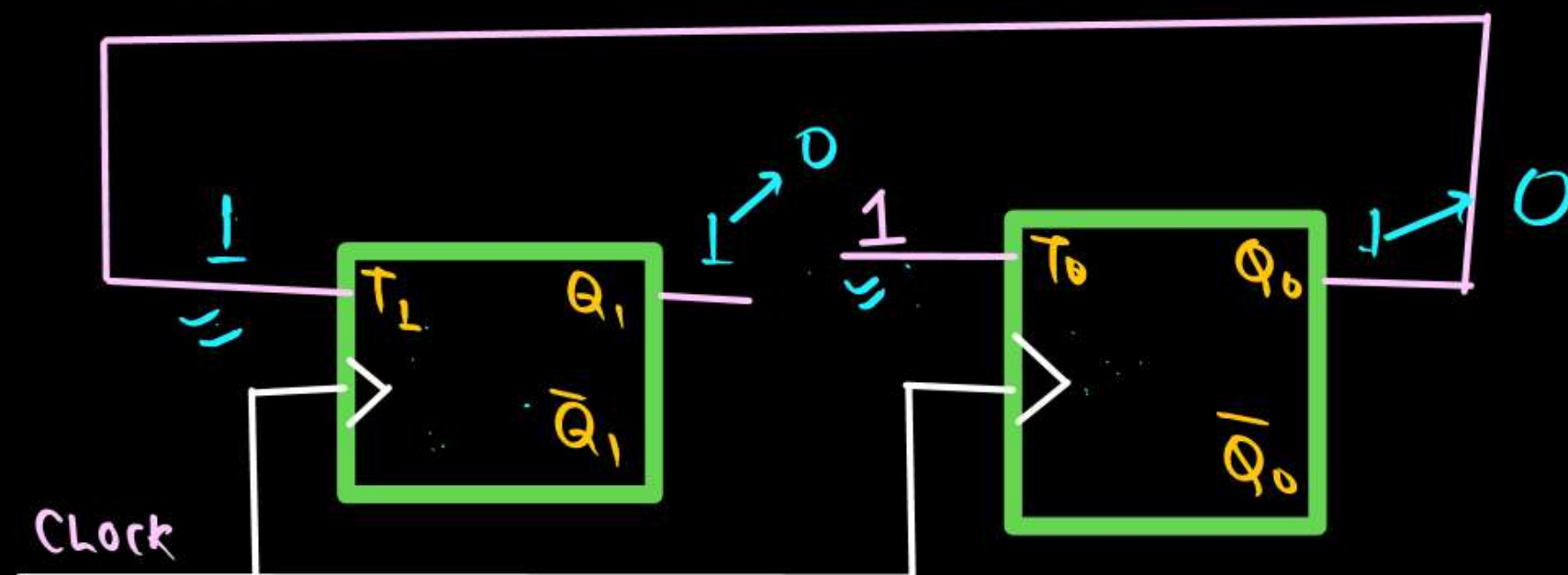

Clock	Q_1	Q_0
0	0	0
1	0	1
2	1	0
3	1	1
4	0	0

ЧАМКА

Q. Which type of counter is shown below?

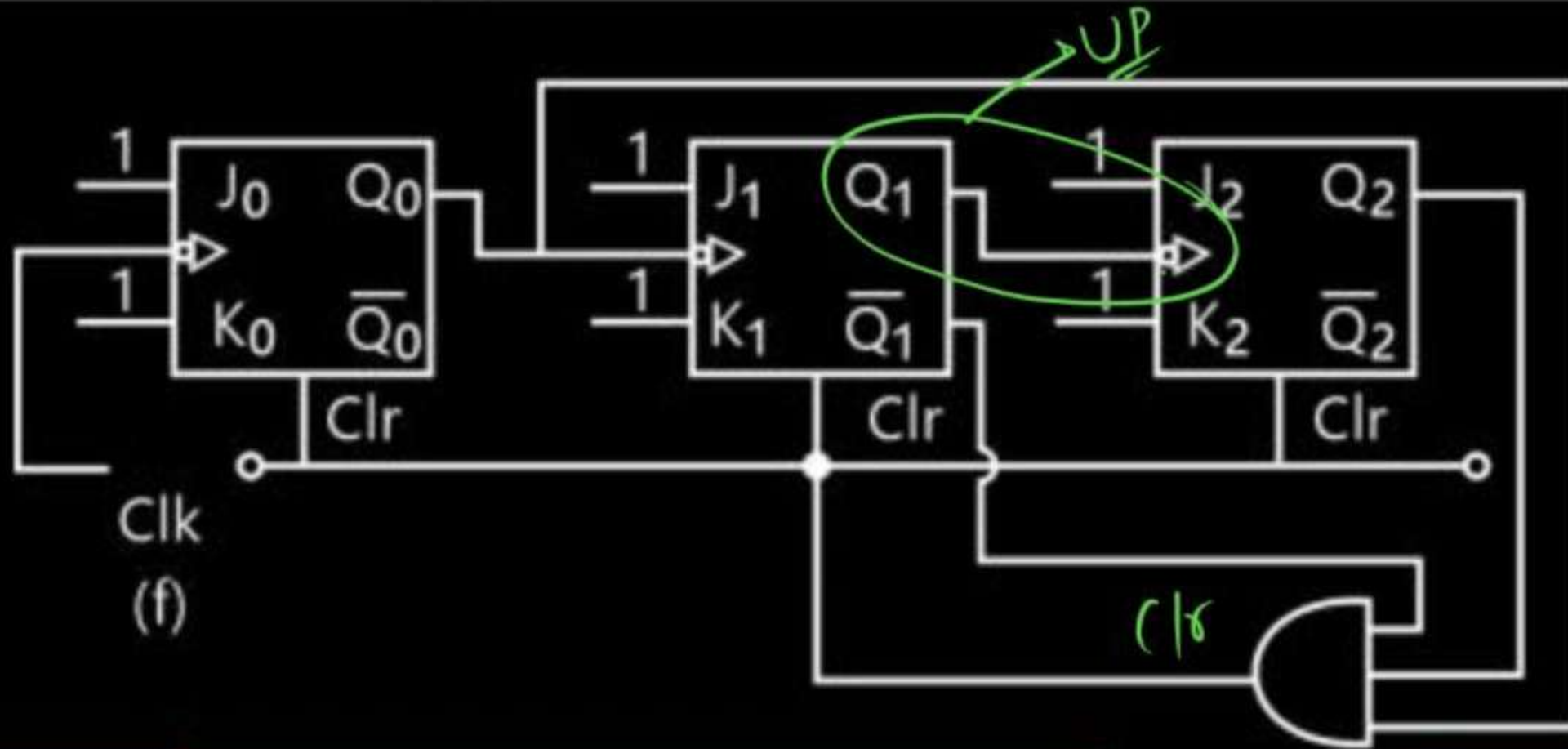

A

mod 5 down counter

B

mod 5 up counter

C


mod 6 up counter

D

mod 6 down counter

Q. Consider the following counter

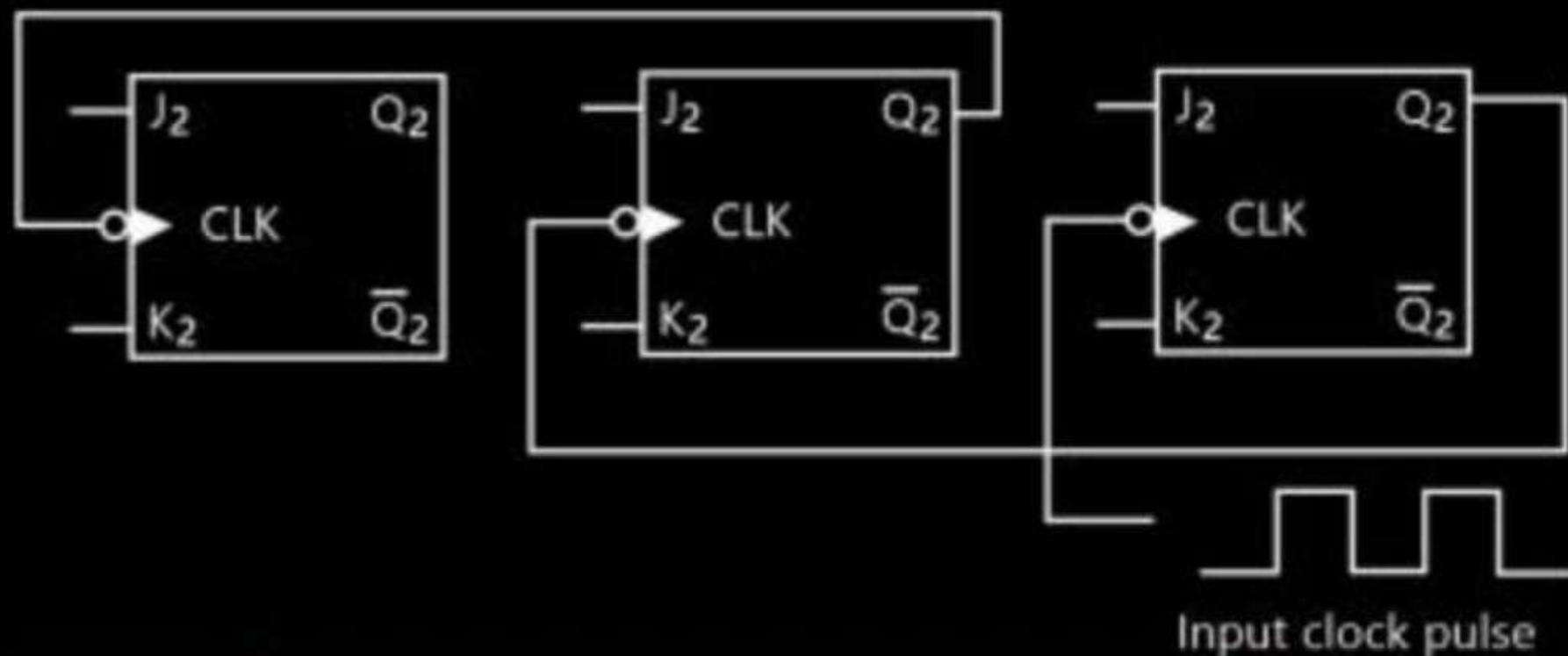If counter starts at 000, what will be the count after 13 clock pulses?



HPW

Comment

A

100

B

101

C

110

D

111

सपने उनके सच होते हैं,
जिनके सपनों में जान होती है,
पंखों से कुछ नहीं होता,
होंसलों से उड़ान होती है।

