



EC/EE/CS/IN

Digital Electronics

LOGIC GATE
NOR,
XOR,XNOR
GATE

LECTURE NO. 2



Chandan Jha Sir (CJ Sir)


रख हौसला वो मंजर
भी आयेगा,
प्यासे के पास चल के
समन्दर भी आयेगा,
थक करन बैठ ऐ
मंजिल के मुसाफिर,
मंजिल भी मिलेगी....
और मिलने का मज़ा
भी आयेगा।

ABOUT ME

- Cleared Gate **Multiple times with double Digit Rank**
(AIR 23, AIR 26)
- Qualified **ISRO Exam**
- Mentored **More than 1 Lakh+** Students (Offline & Online)
- More than **250+** Motivational Seminar in various Engineering College including NITs & Some of IITs



Chandan Jha

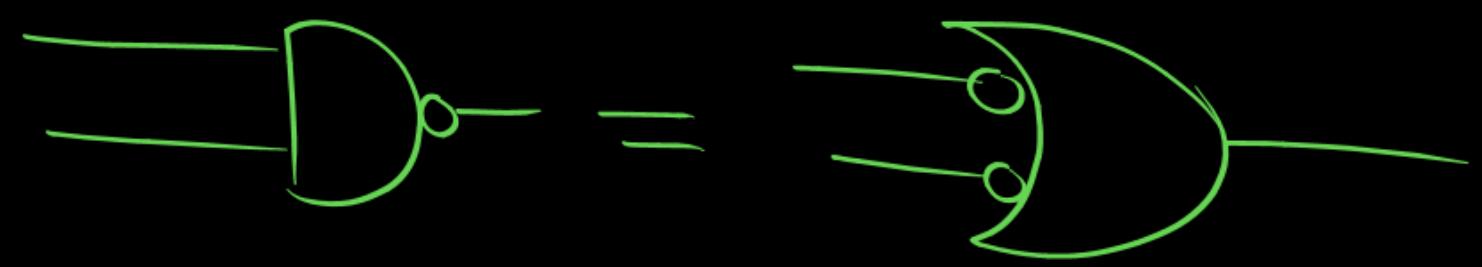

NAND = Bubbled OR


Q.1 Find the minimum number of two input NAND required to implement the function given below:

$$f = AB + CD$$

AOI

AND-OR-Inverter

③

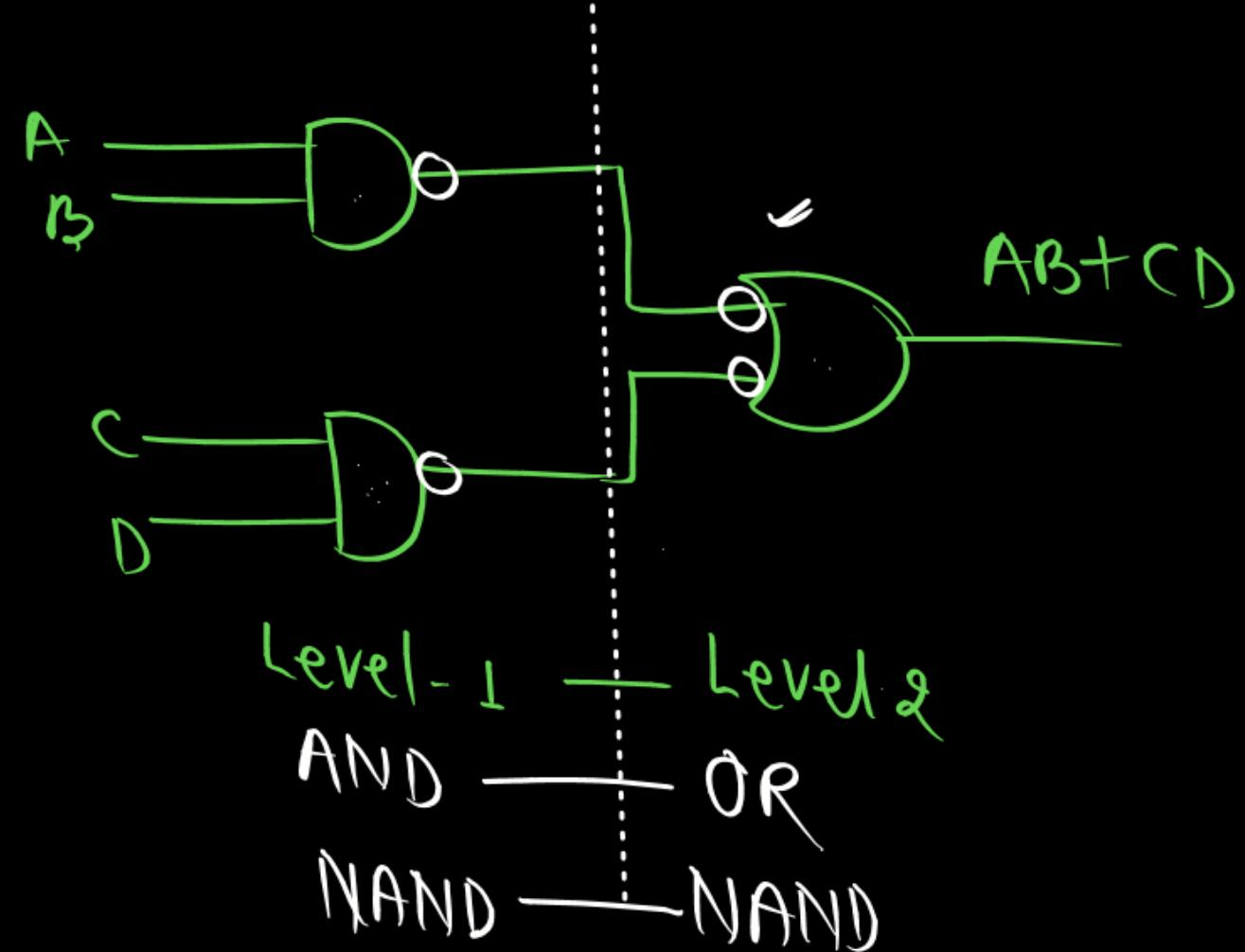③ NAND ✓

Function

T

NAND

SOP

Sum of Product

POS

Product of Sum


NOR

SOP


$$f = \underline{AB} + \underline{CD}$$

SOP

Ex. $f = (A+B) \cdot (C+D)$

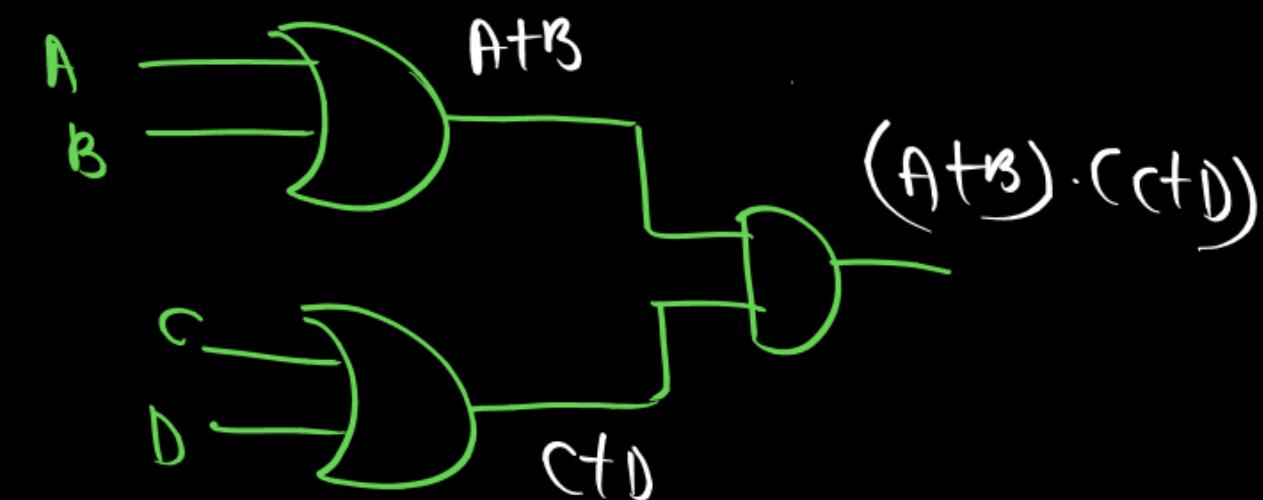


Case(3)

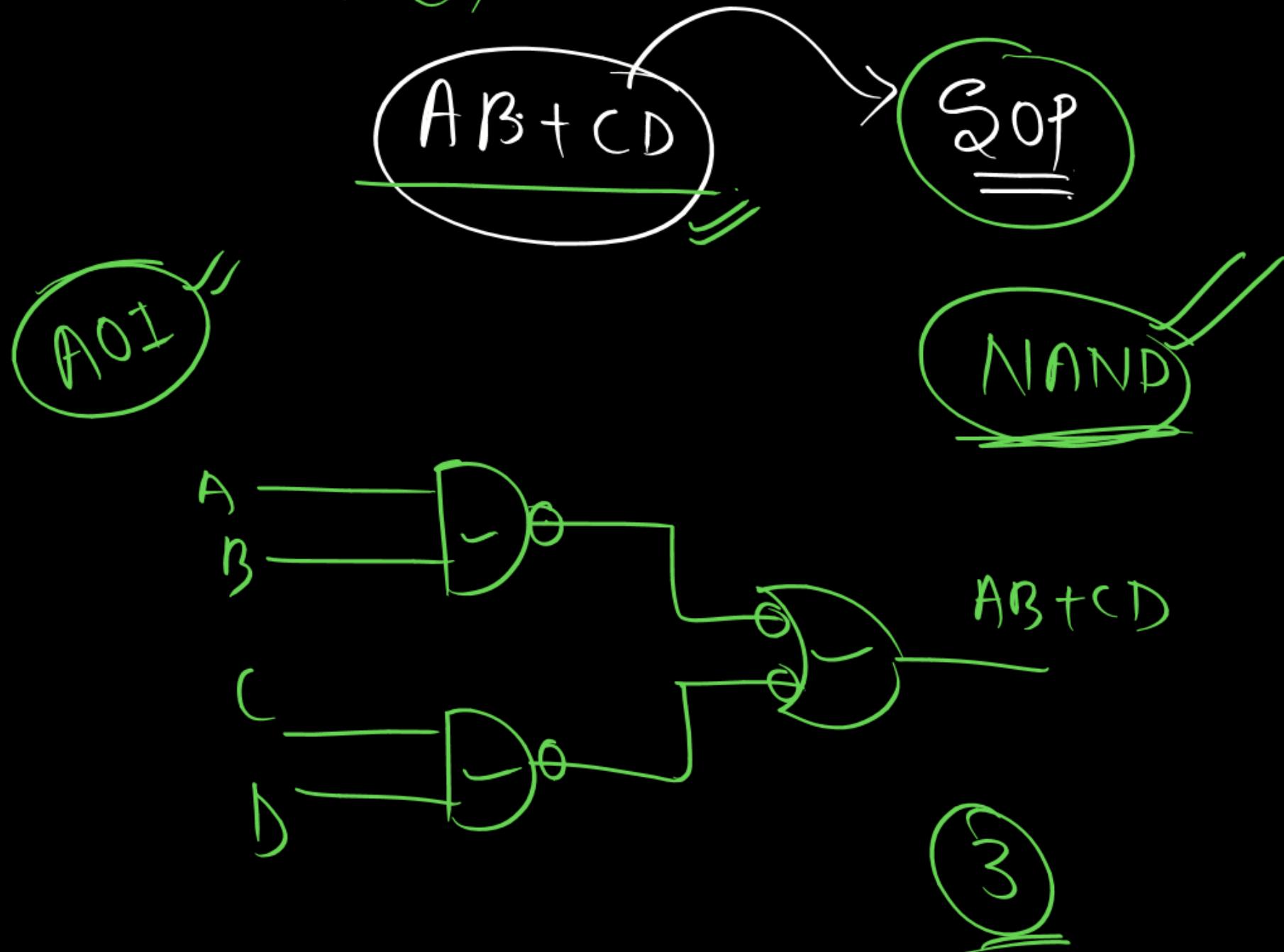


AND-OR
NAND-NAND

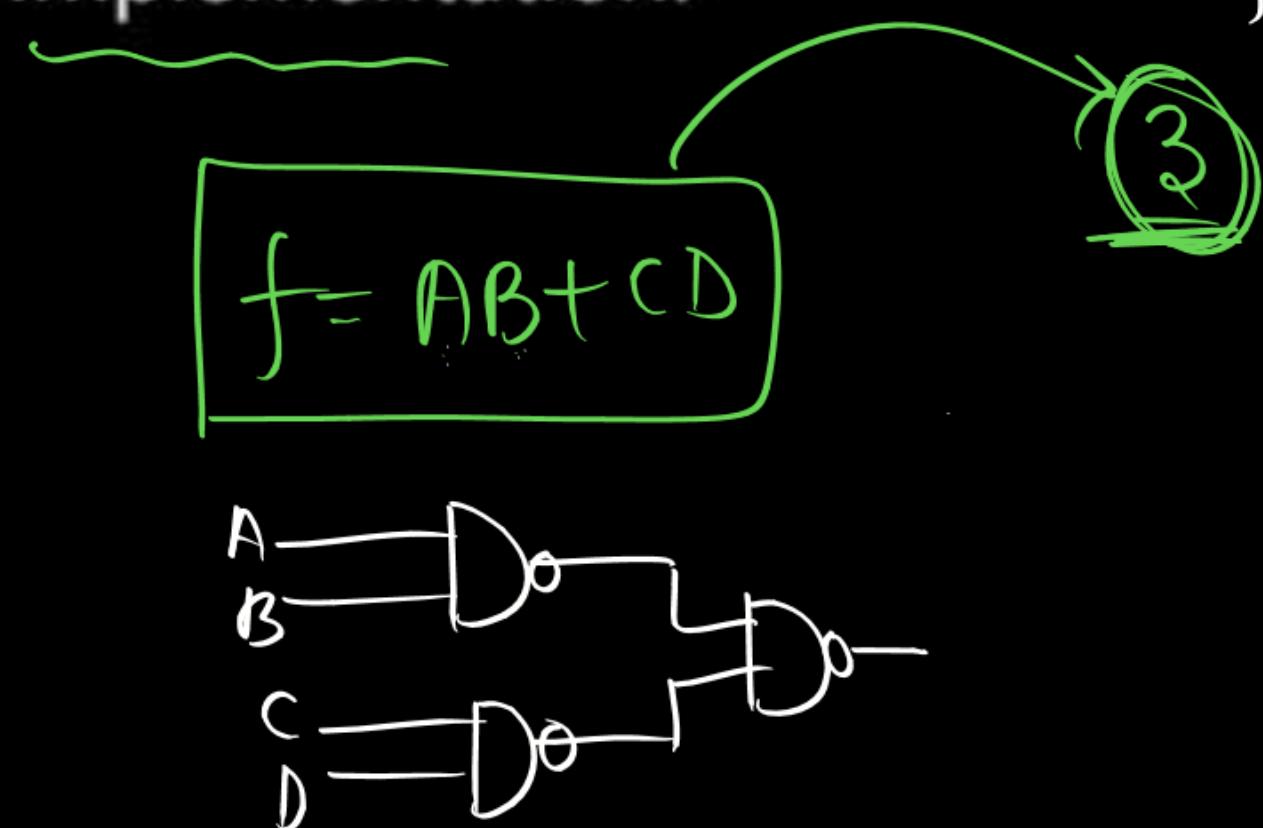When ever minimum number of two input NAND Gates are asked
write the Function in SOP Form & implement it by using
AOI(AND-OR-INVERTER) which is a two level AND-OR
Implementation which is exactly equal to NAND - NAND
Implementation.



$$f = A \cdot A + B \cdot B$$
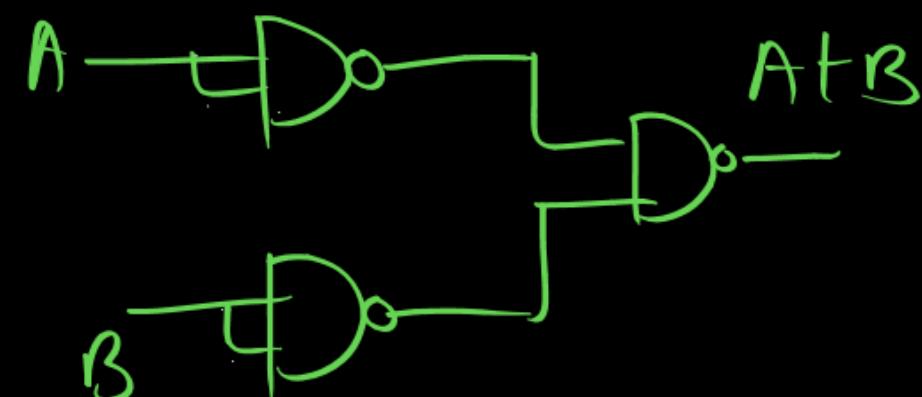
$$f = A + B \rightarrow \underline{\text{OR}}$$




$$A+B \Rightarrow 3$$

$$AB+CD \Rightarrow ③$$

Q2. Find the minimum number of two input NAND required to implement the function given below:

$$f(A, B, C) = A\bar{B} + BC$$

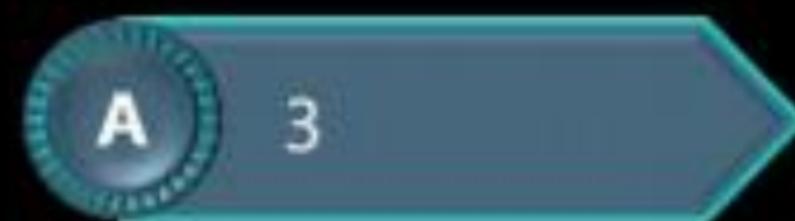

$$\frac{\overline{AB} + BC}{(3)+1}$$

④

B 4

D 7

The diagram shows the Boolean expression $\overline{AB} + BC$ with a green bracket grouping it. Above the bracket is the number 3 in a circle, with a green arrow pointing from the bracket to the circle. Below the bracket is the number 1 in a circle, with a green arrow pointing from the bracket to the circle. To the left of the bracket is the expression $\overline{AB} + BC$. To the right of the bracket is the result $(3)+1$. Below the result is the number 4 in a circle, with a green arrow pointing from the result to the circle. At the bottom right is a blue arrow pointing right with a circle containing 'D' and the number '7'.




Q3. Find the minimum number of two input NAND GATE required to implement the Boolean function-

$$f = AB + CD + F$$

$$f = X + F$$



$$X = AB + CD$$

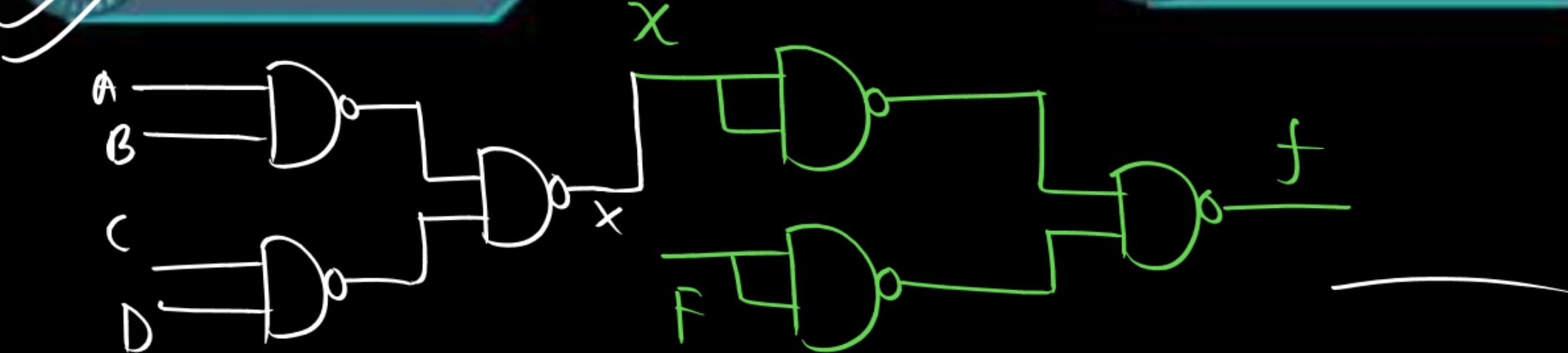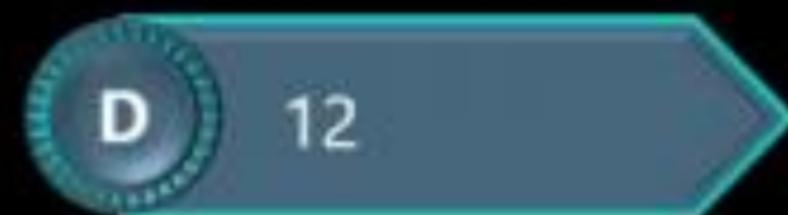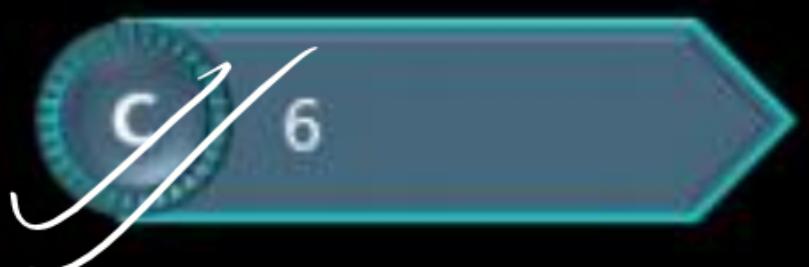

$$\left\{ \begin{array}{l} AB + CD \rightarrow ③ \\ A + B - ③ \end{array} \right.$$

Q.4. Find the minimum number of two input NAND GATE required to implement the function-



$$f(A, B, C, D) = AB + BC + CD + DA$$

A 9

C 6

B 8

D 12

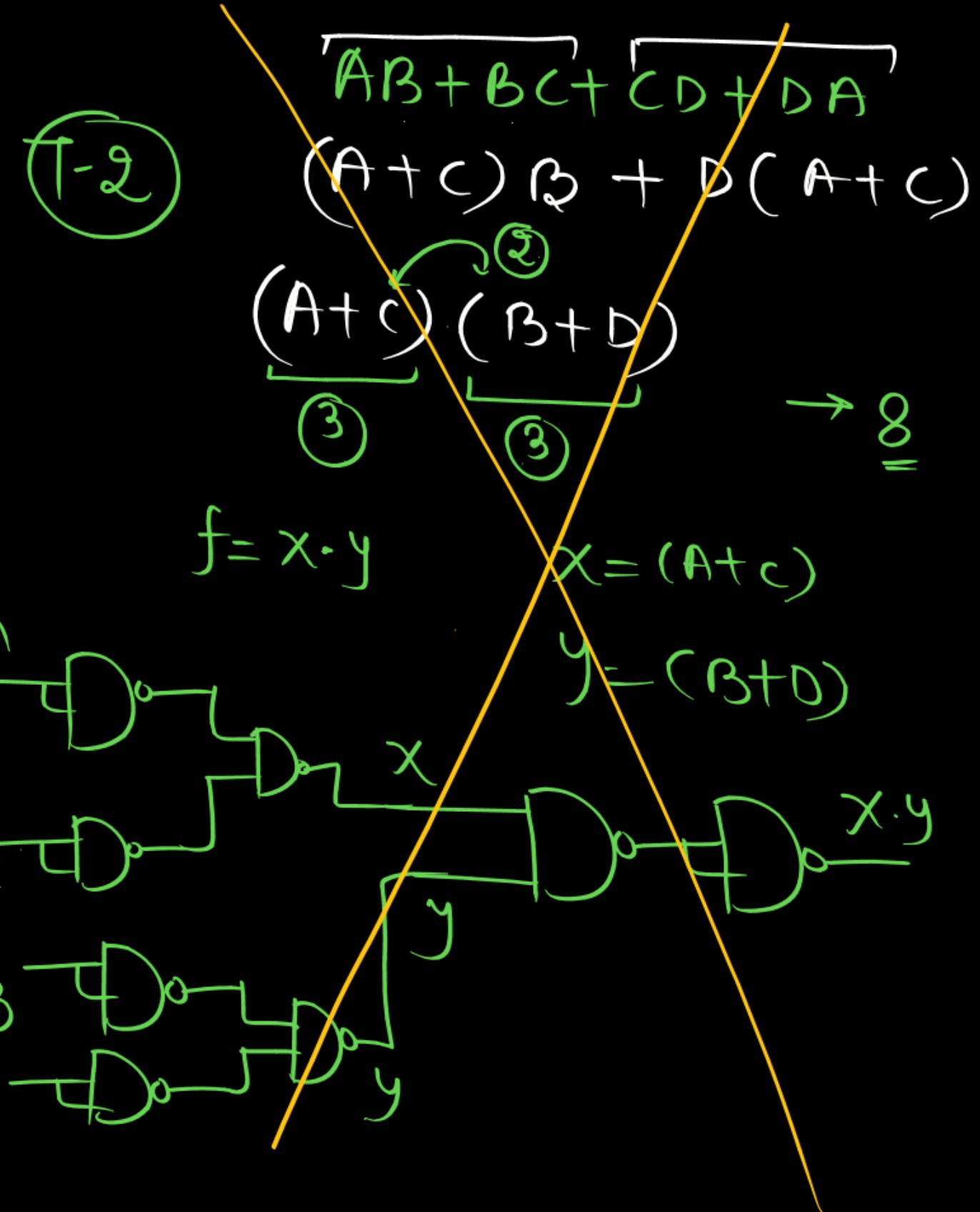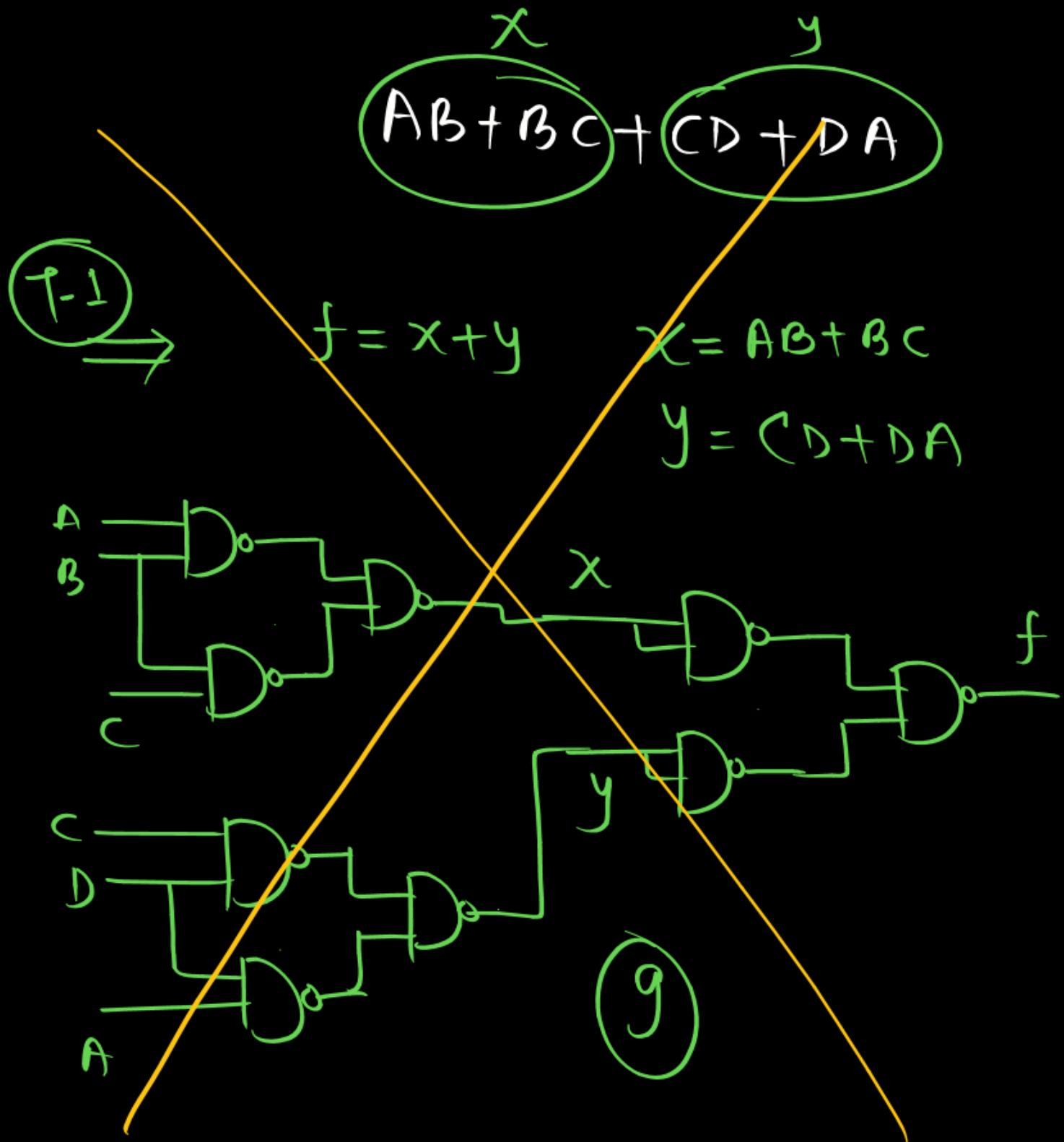


7-3

$$f = AB + BC + CD + DA$$
$$= B(A+C) + D(A+C)$$

$$A+C = X$$



$$f = \underline{BX + DX}$$

(3) $\xleftarrow{+}$ (3) \rightarrow 6

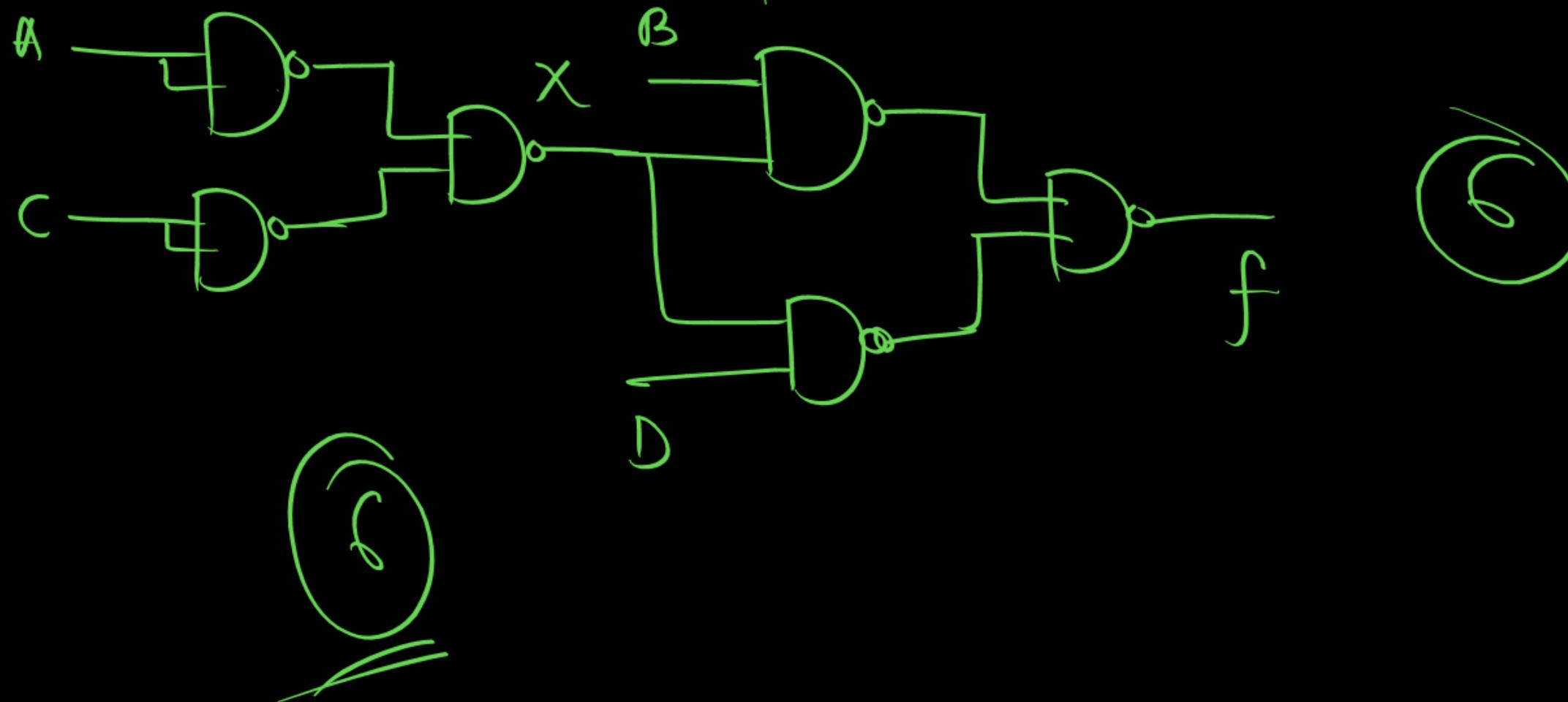

NAND GATE


1. Symbol

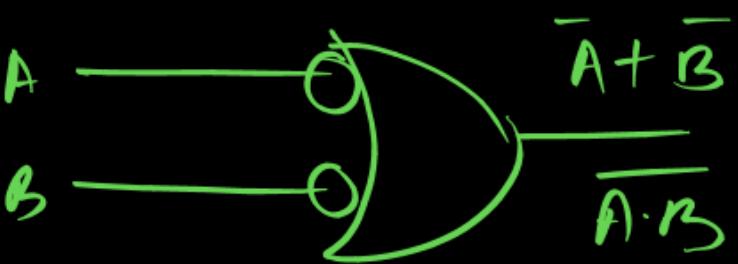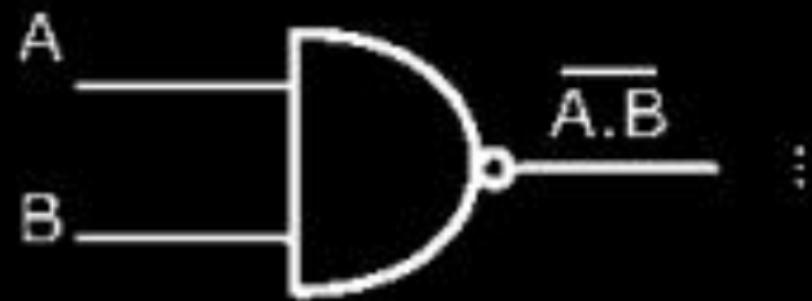


2. Truth Table

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Minimum
no. of
NAND?

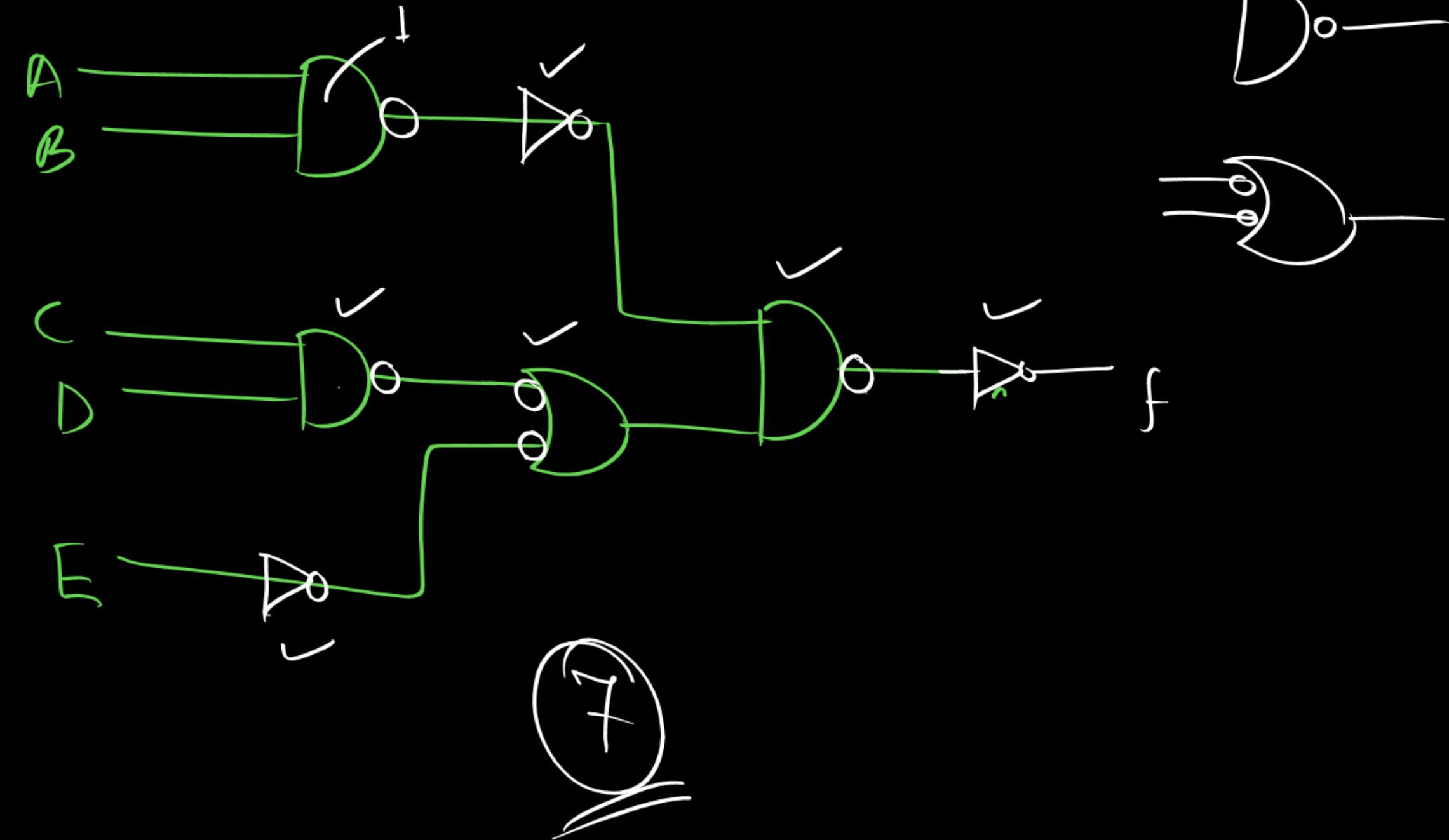
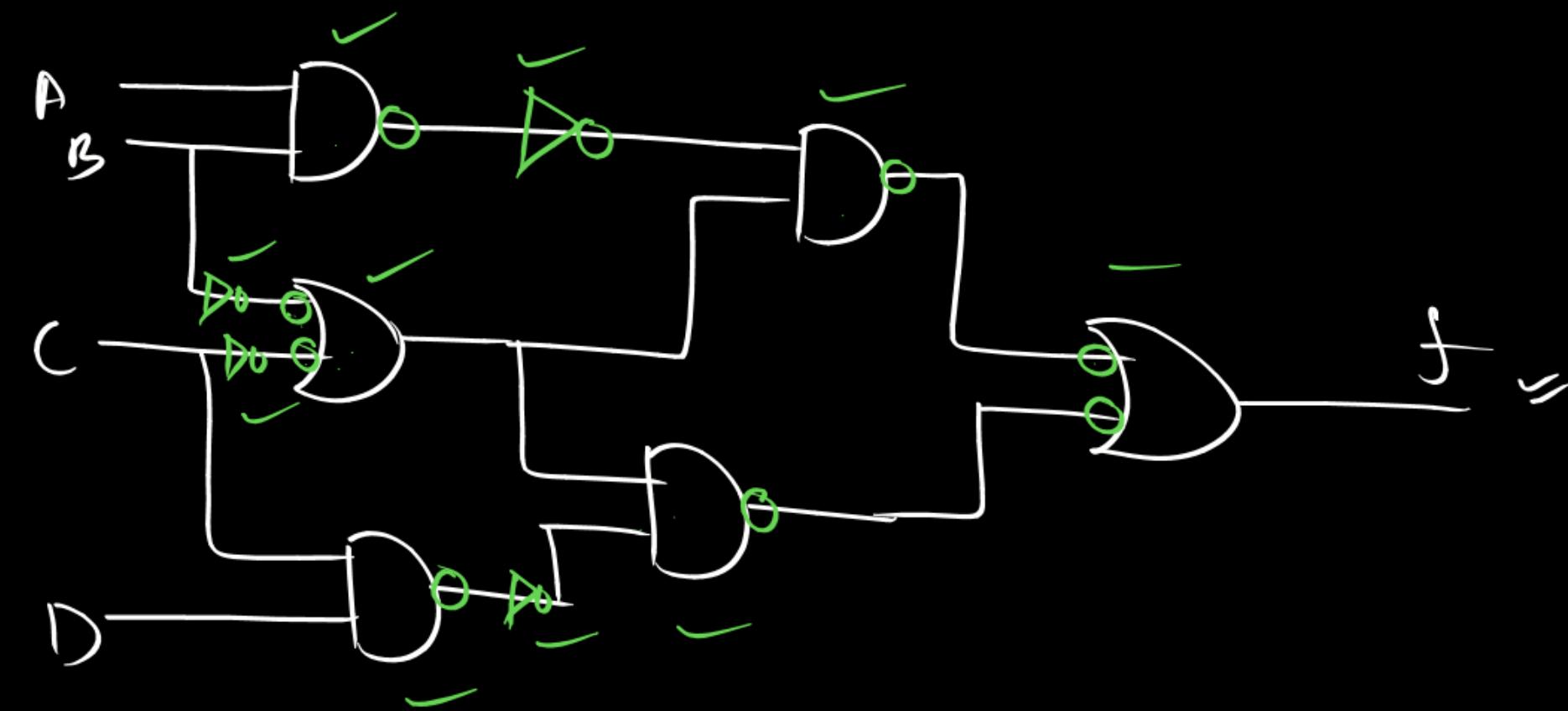
$$\underline{Q} =$$


Case-(1)

A · B · C · D · · ·

Case(2)

A + B + C + · · ·

Case(3)



AB+CD
→ ③

Case(4)

function Implementation
→ Bubbled

NOR GATE

1. Symbol

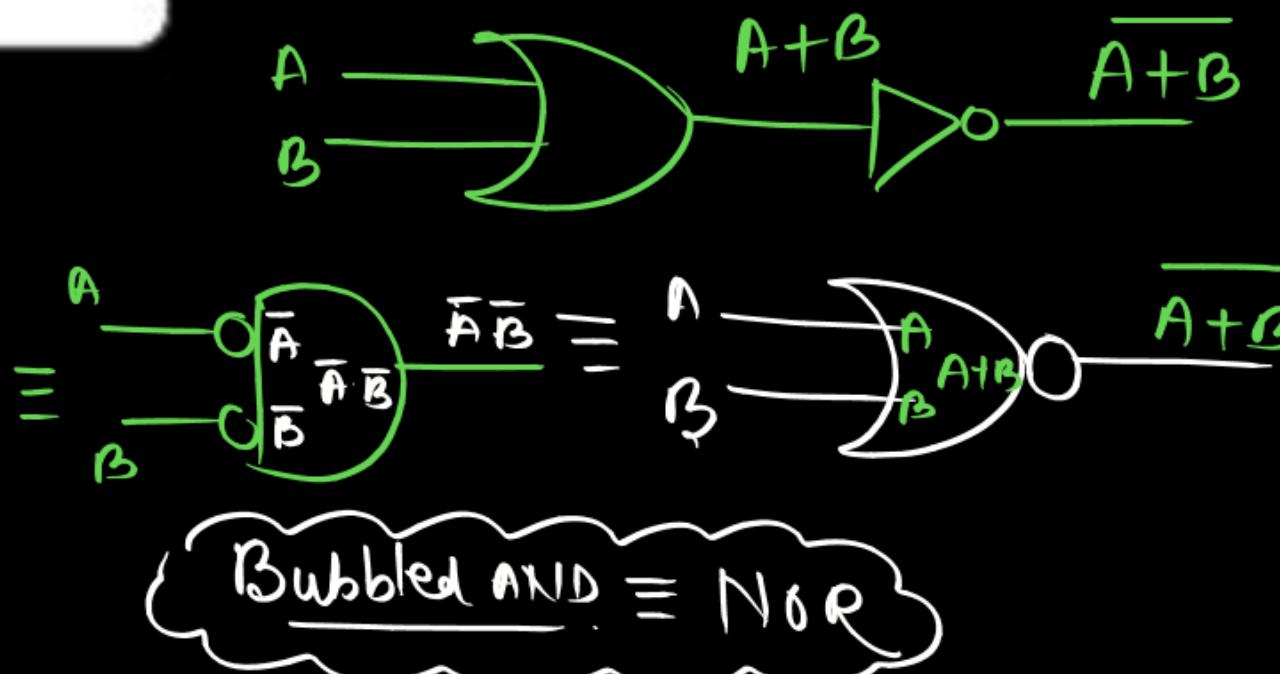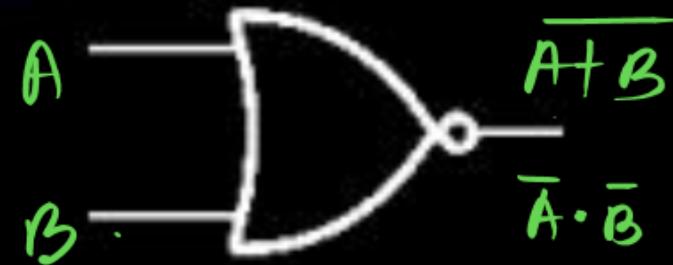

2. Truth table

| A | B | Y |
|---|---|-----|
| 0 | 0 | 1 ✓ |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


(N)OR

D-Morgan's Law


$$\left\{ \begin{array}{l} \overline{A+B} = \overline{A} \cdot \overline{B} \\ \overline{A \cdot B} = \overline{A} + \overline{B} \end{array} \right.$$

NOR GATE

3. Enable/Disable

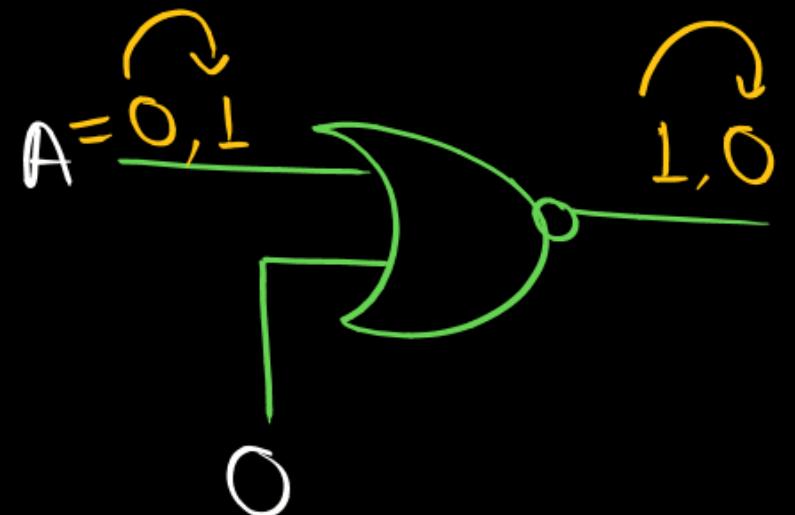

Control '0' Enabled

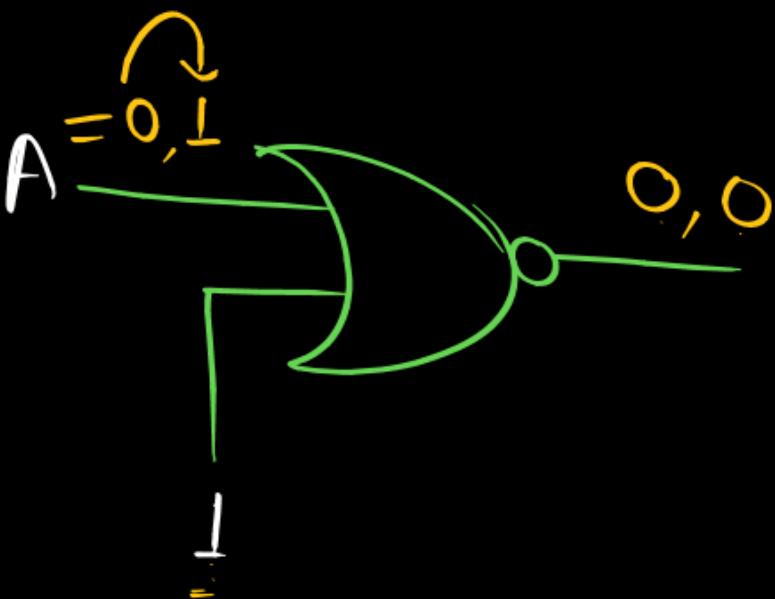

Control '1' Disabled

NOR GATE






4. Commutative law ✓

$$\overline{A+B} \equiv \overline{B+A}$$

Associative Law ✗
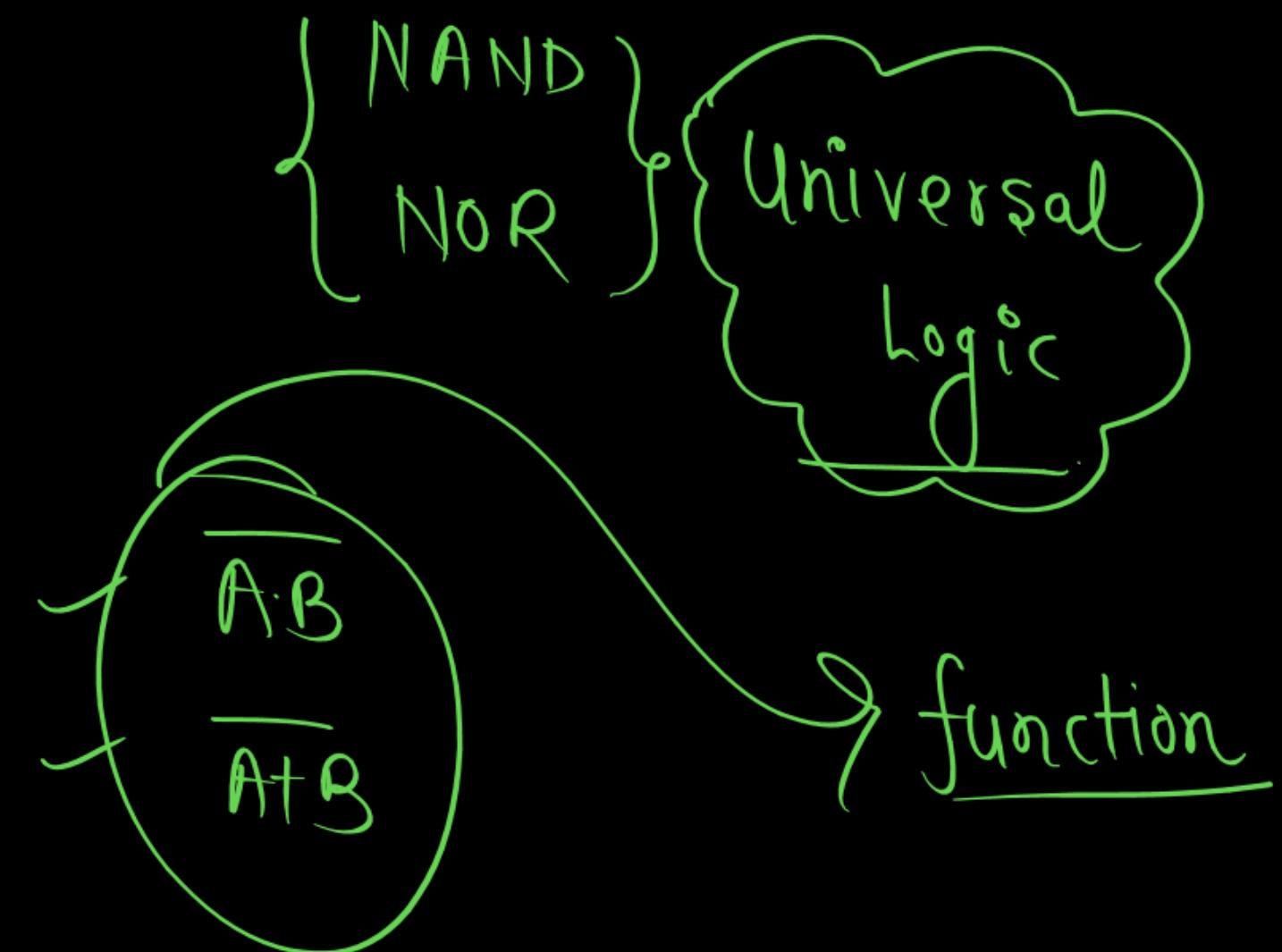
$$\overline{(A+B)+C} \neq \overline{A+(B+C)}$$



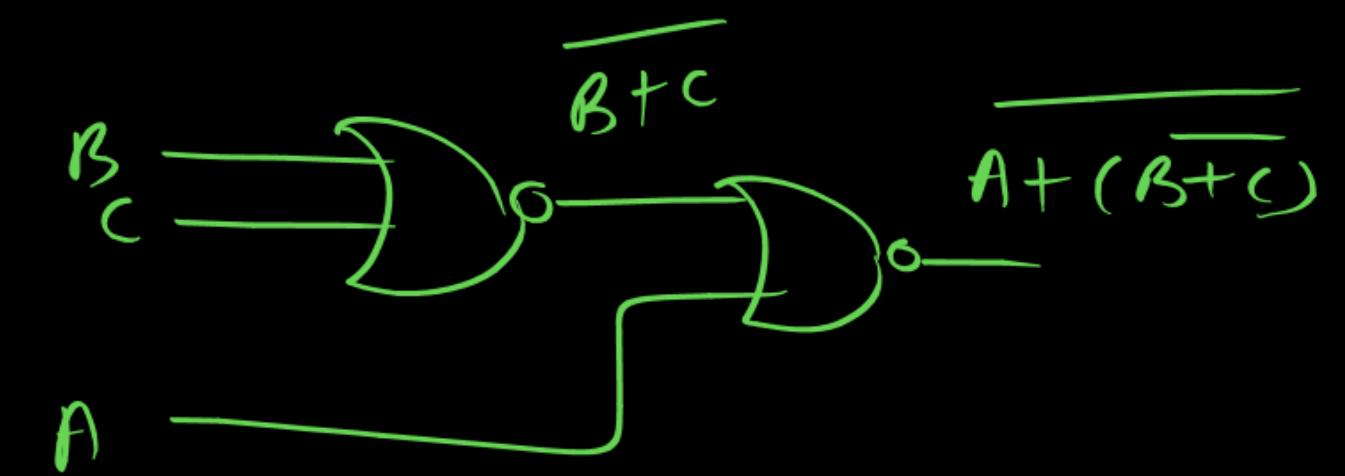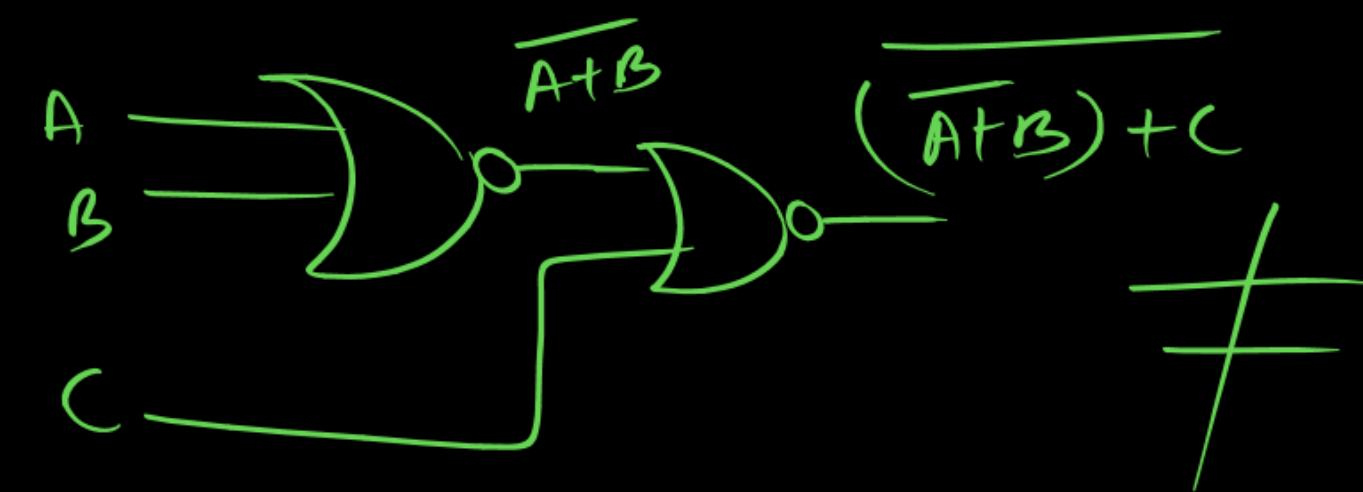

NOR GATE

MCQ

Ex.1. Which of the following option(s) is/are called universal logic?

A NAND

C Both A & B

B NOR

D None

NAND
NOR

NOR GATE

MCQ



Ex.2. Which of the following option(s) is/are called universal logic?

A

NAND

C

AND

B

NOR

D

OR

NOR GATE

MSQ

Ex.3. Which of the following option(s) is/are called universal logic?

A $(\overline{A} + \overline{B})$

$\overbrace{\quad}$ NOR

C $(A + \overline{B})$

$\overbrace{\quad}$

B $(\overline{A} \cdot \overline{B})$

$\overbrace{\quad}$ NAND


D All of the above



$\overbrace{\quad}$ $\overline{A} \cdot \overline{B}$


$$A + \bar{B}$$



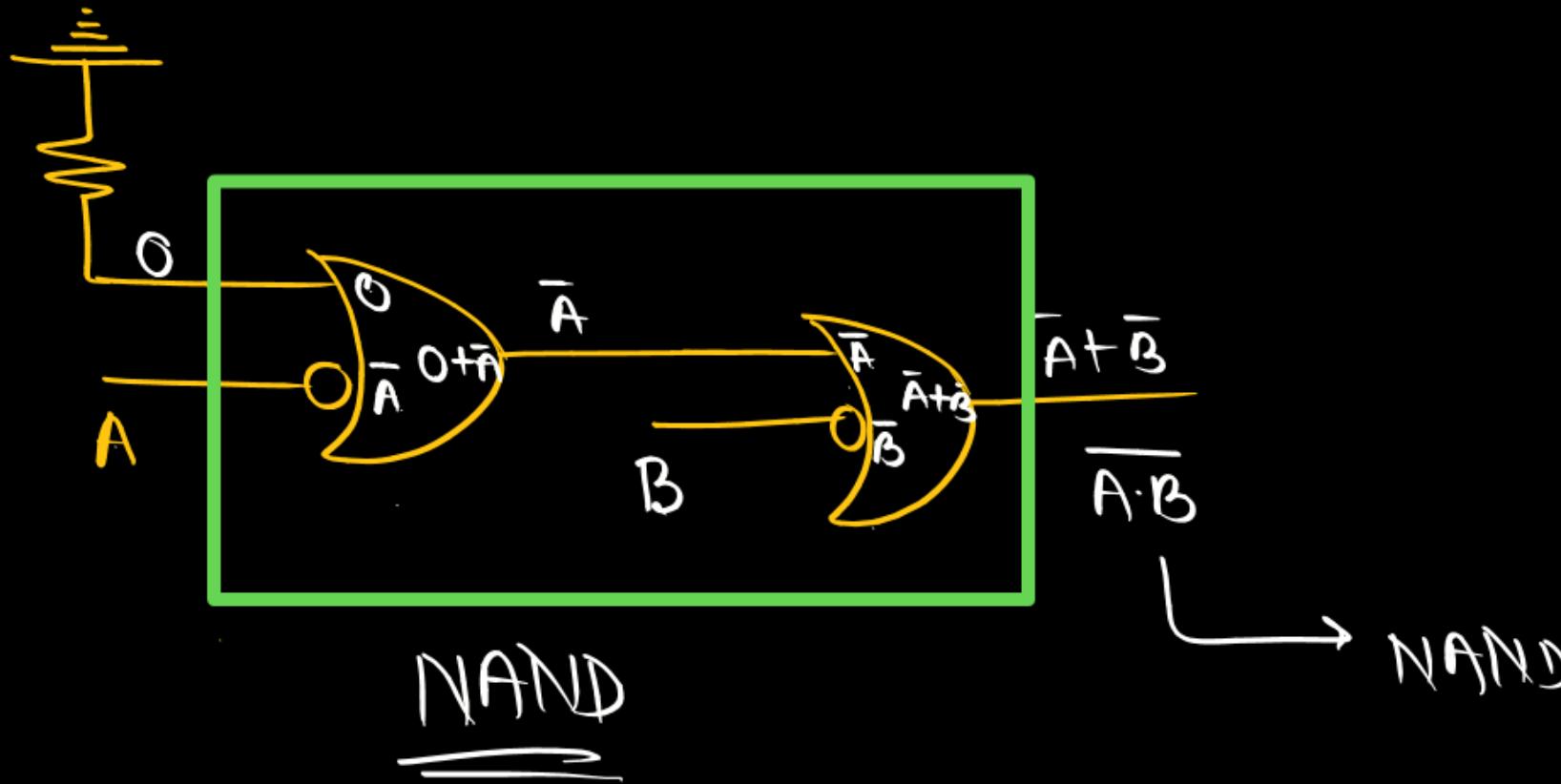
$$\begin{array}{c} \overline{A \cdot B} \\ \overline{\overline{A} + \overline{B}} \end{array}$$



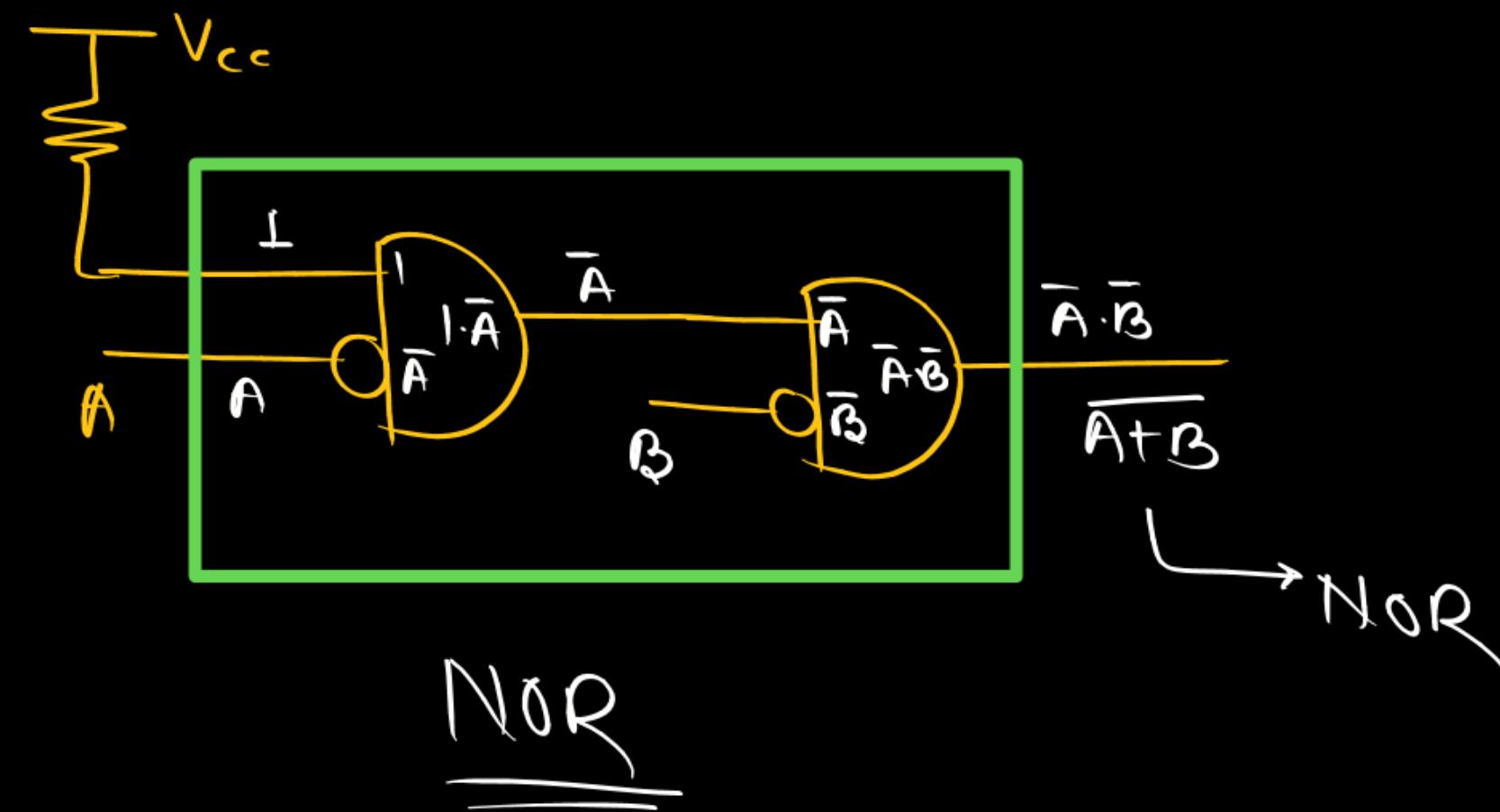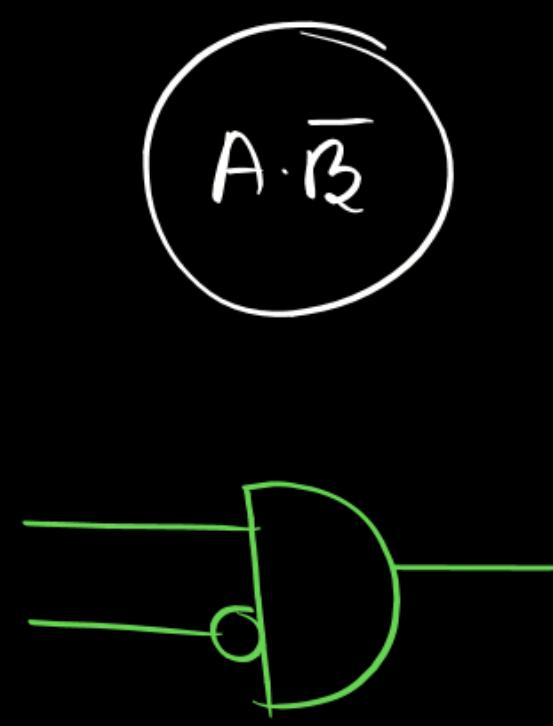

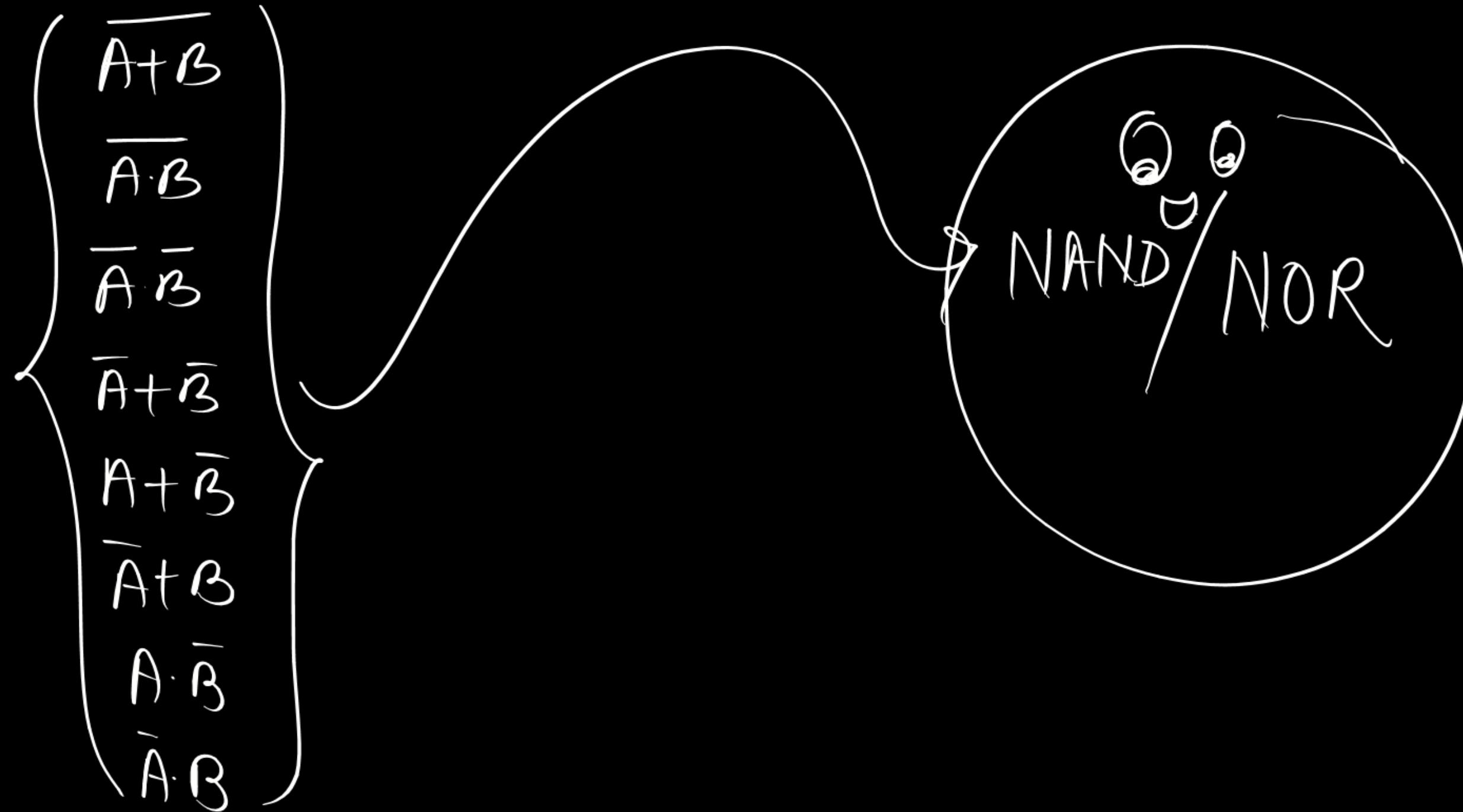

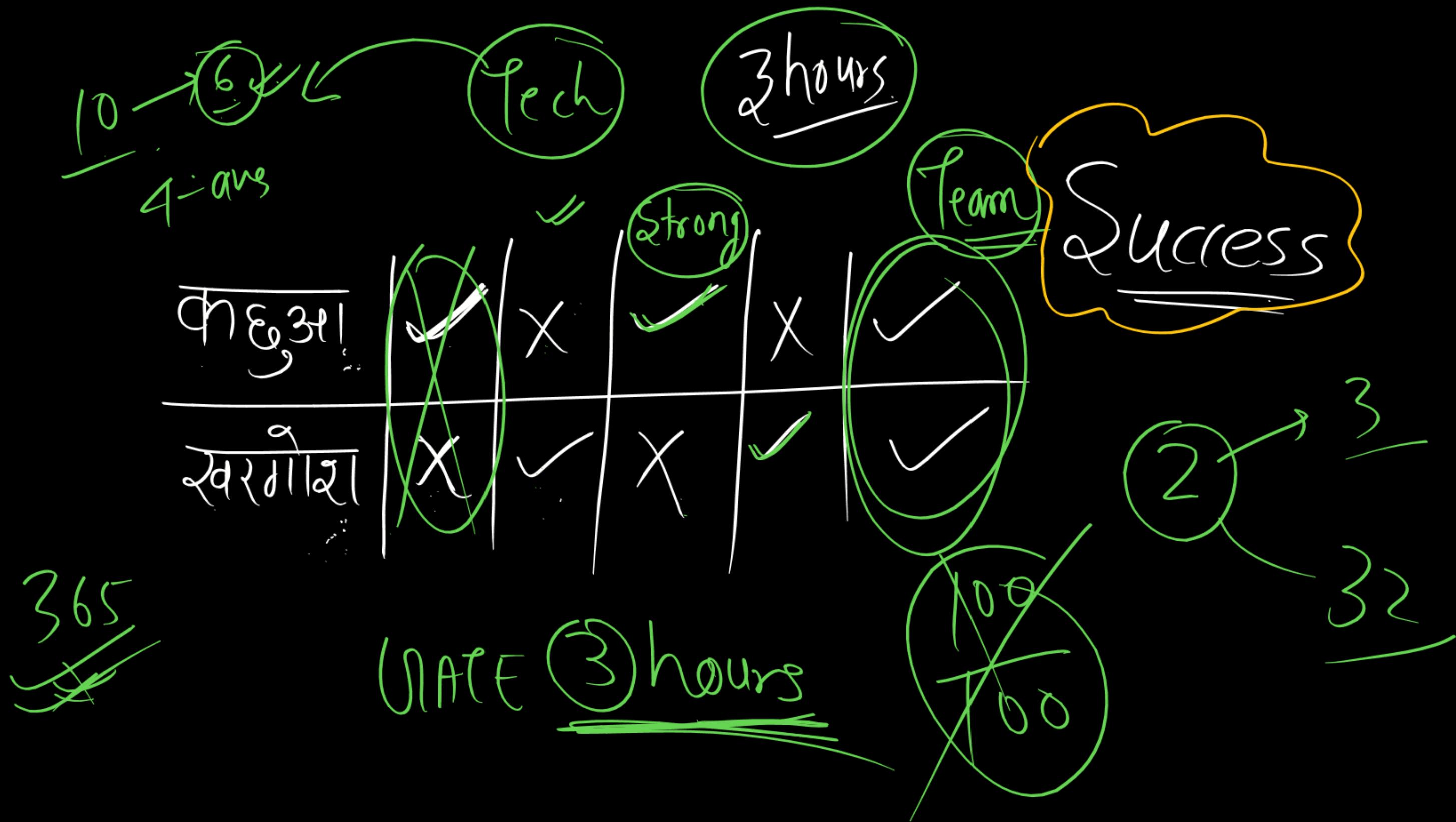

XOR GATE



| A | B | $y = A \oplus B$ |
|---|---|------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 ✓ |
| 1 | 0 | 1 ✓ |
| 1 | 1 | 0 |

$$\begin{cases} A = B & y = 0 \\ A = \overline{B} & y = 1 \end{cases}$$

O/P = 1 when odd no. of 1's
are present in the inputs.

$$A \oplus A = 0$$

$$A \oplus 0 = A$$

$$A \oplus \bar{A} = 1$$

$$A \oplus 1 = \bar{A}$$

$$0 \oplus 0 = \bar{0} \cdot 0 + 0 \cdot \bar{0}$$

$$1 \cdot 0 + 0 \cdot 1$$


$$0 + 0 = 0$$

If
 $A \oplus B = C$


Then $A \oplus C = ?$

$$A \oplus C = B$$


$$B \oplus C = A$$

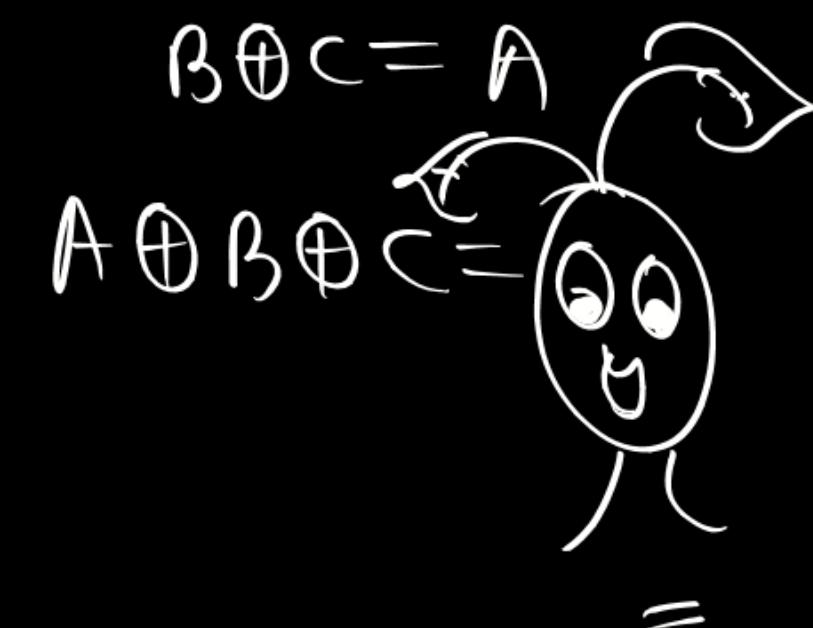

XOR GATE

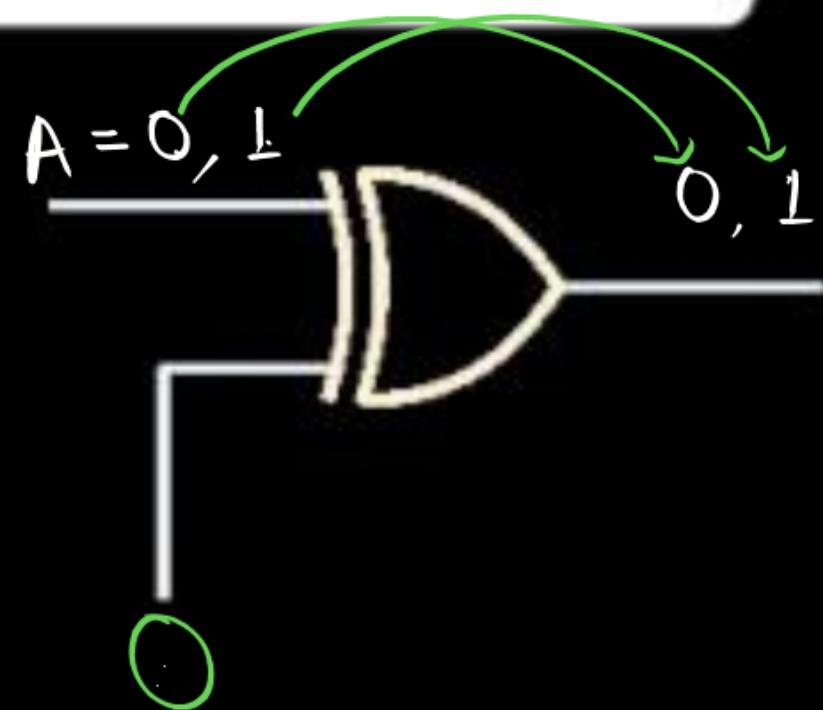

"BUFFER"

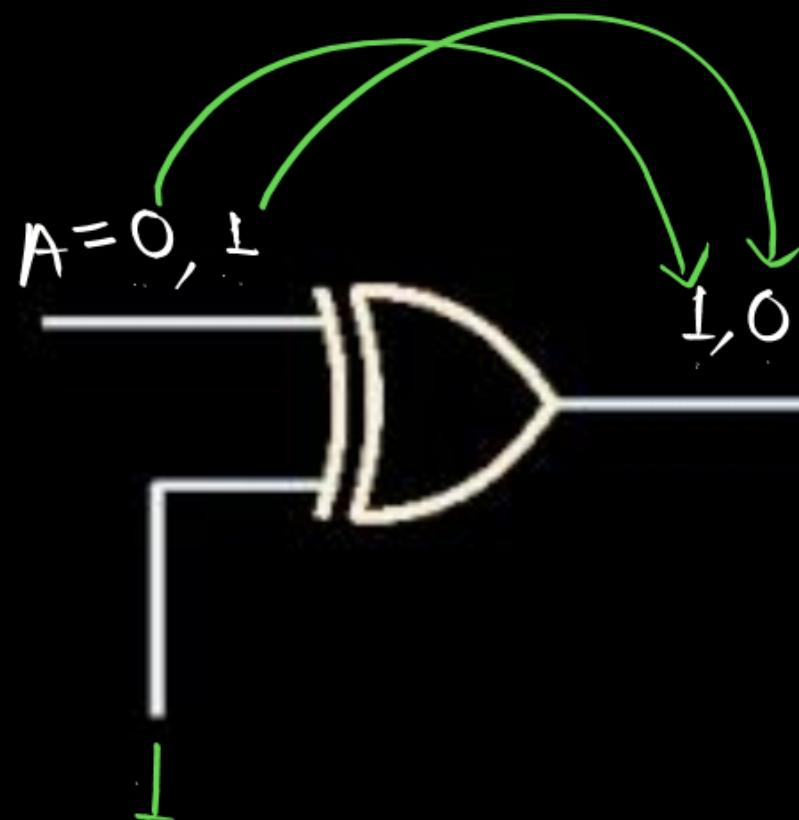

"INVETER"


$$A \oplus A = 0$$

$$A \oplus A \oplus A = A$$

$$A \oplus A \oplus A \oplus A = 0$$


$$A \oplus A \oplus A \cdots \oplus A = \begin{cases} 0 & \text{Even no. of } A \\ A & \text{Odd no. of } A \end{cases}$$

Q

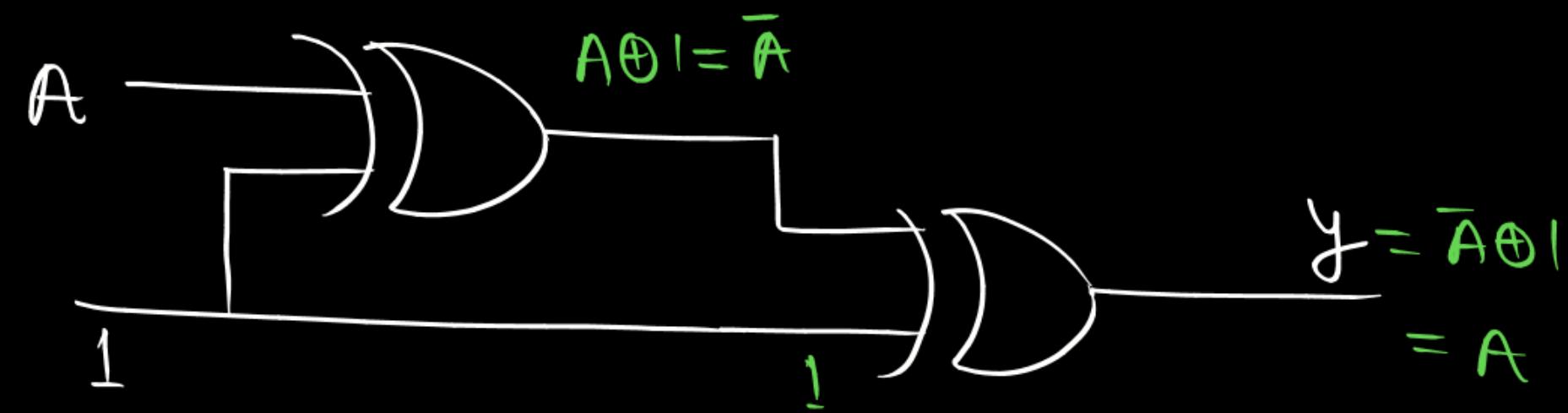


XOR GATE

Ex. 1

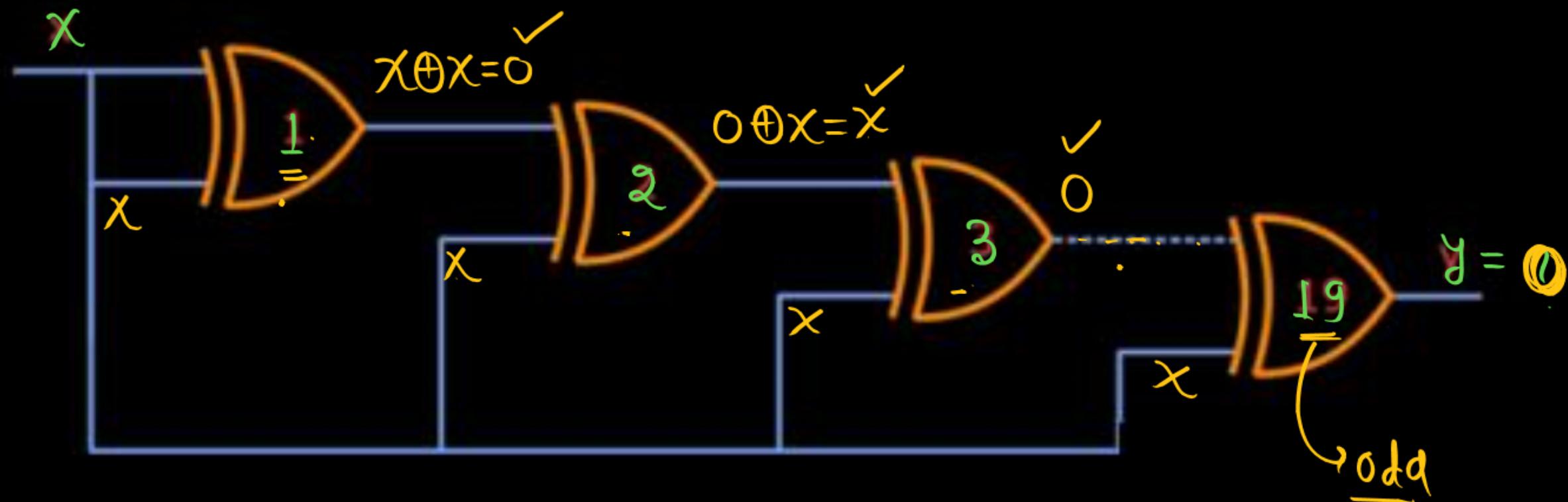

XOR GATE

Ex. 2

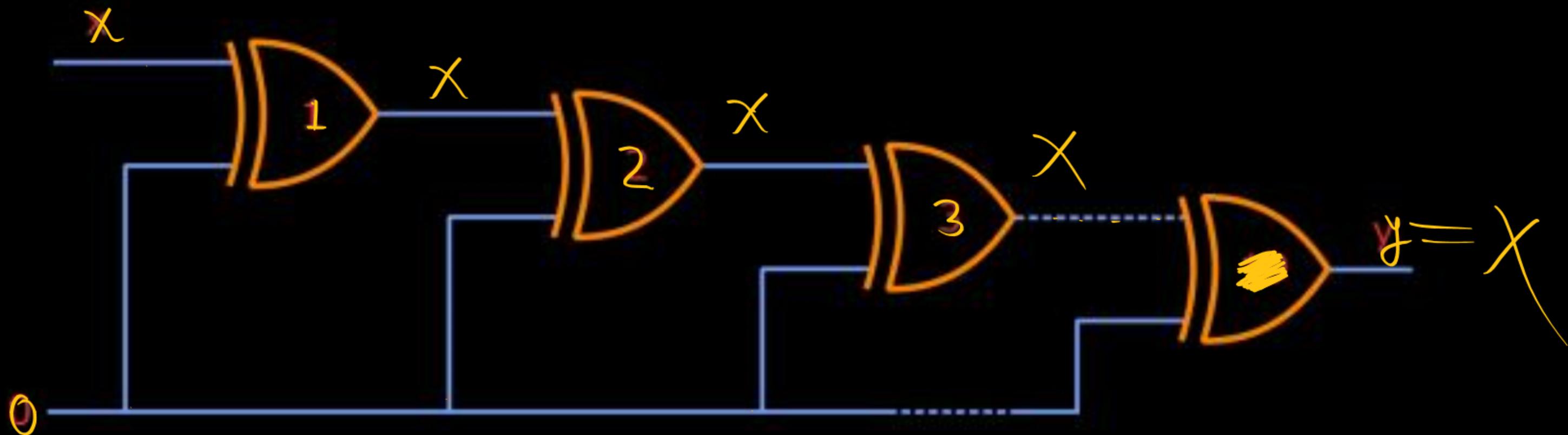


XOR GATE

Ex. 3

$$1 \oplus x = \bar{x}$$

$$\bar{x} \oplus 1 = x$$

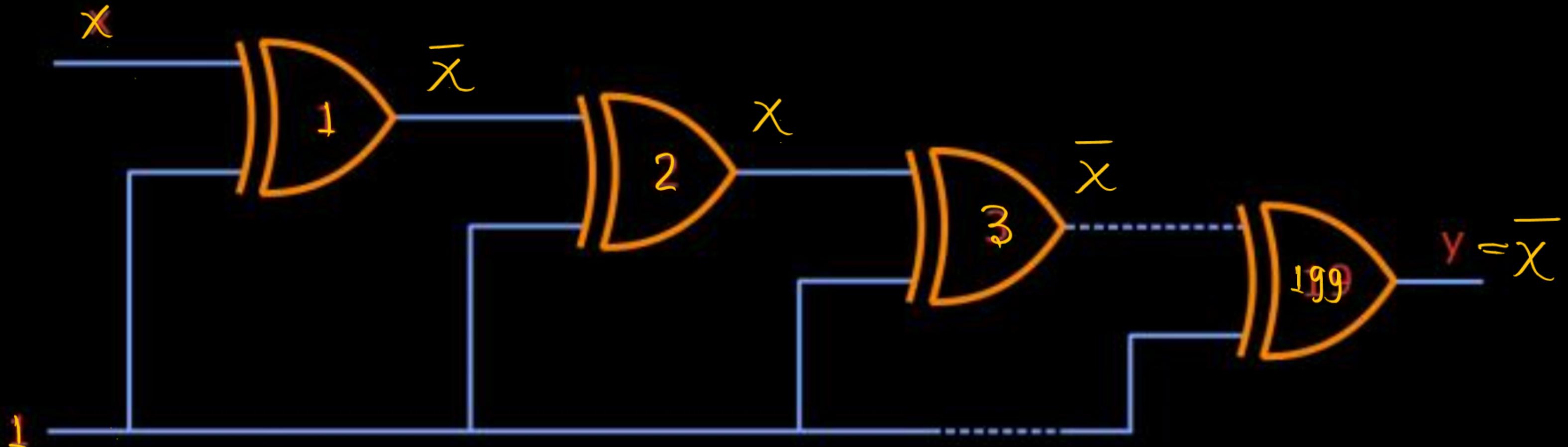

XOR GATE

7. X-OR follows the commutative as well as associative Law

$$A \oplus B = B \oplus A \Rightarrow \text{commutative Law}$$

$$A \oplus B \oplus C = (A \oplus B) \oplus C \quad \text{Associative Law}$$

$$(A \oplus B) \oplus C = A \oplus (B \oplus C)$$


Associative law

XOR GATE

| Decimal | ABC | $A \oplus B \oplus C$ | $(A \oplus B) \oplus C$ |
|---------|---------|-----------------------|-------------------------|
| 0 | 000 | 0 | 0 |
| 1 | 001 → 1 | 1 | 1 |
| 2 | 010 → 1 | 1 | 1 |
| 3 | 011 | 0 | 0 |
| 4 | 100 → 1 | 1 | 1 |
| 5 | 101 | 0 | 0 |
| 6 | 110 | 0 | 0 |
| 7 | 111 → 1 | 1 | 1 |

$A \oplus B \oplus C = \sum m(1, 3, 4, 7)$
 minimized

XNOR GATE

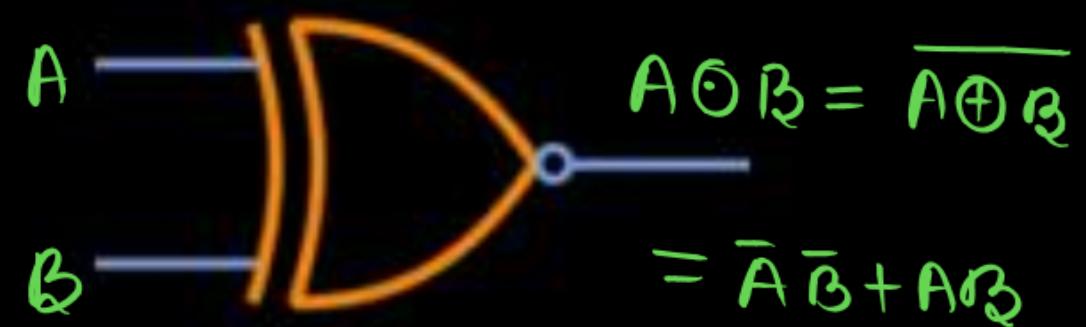

$$\left\{ \begin{array}{ll} A = B & y = 1 \\ A = \overline{B} & y = 0 \end{array} \right.$$

| A | B | y = A ⊙ B |
|---|---|-----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

→ Equivalence logic
 → Coincidence logic


$$A \odot A = 1$$

$$A \odot 1 = A$$


$$A \odot \bar{A} = 0$$

$$A \odot 0 = \bar{A}$$

XNOR GATE

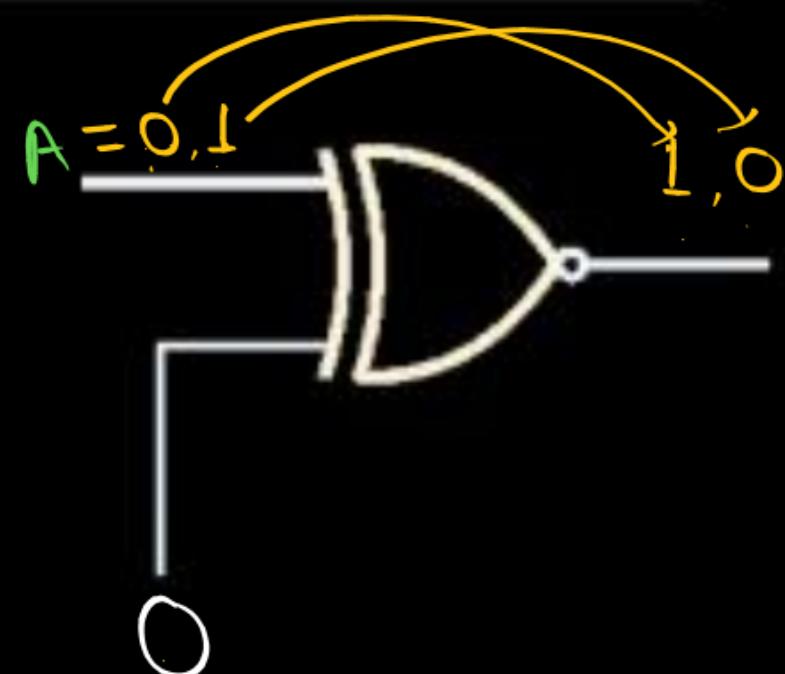

INVERTER

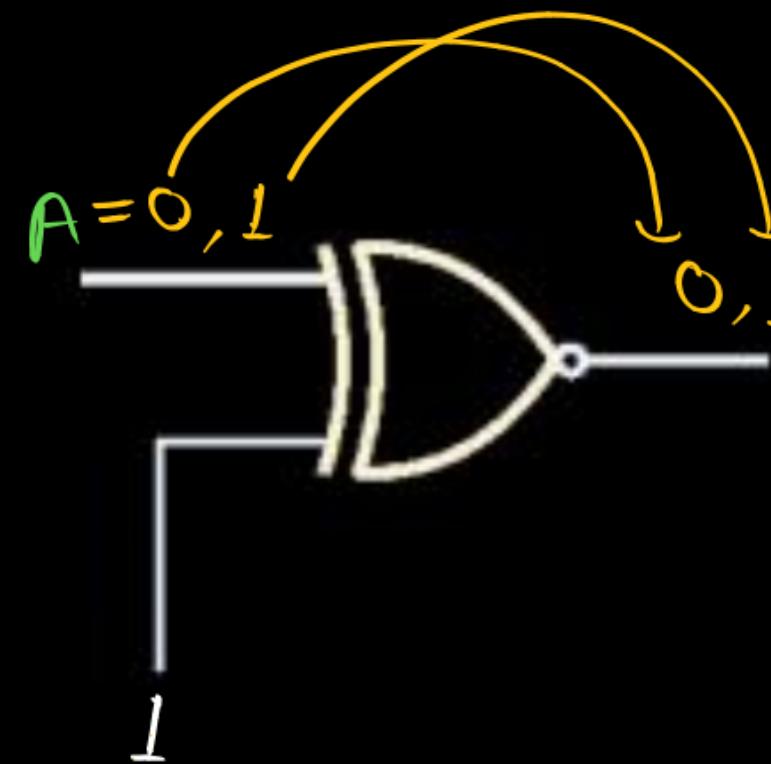

BUFFER

X-NOR



Commutative Law ✓


Associative law ✓

$$A \oplus B = \overline{A \oplus B}$$

$$(A \oplus B) \oplus C = A \oplus B \oplus C$$

$$A \oplus B \oplus C \oplus D = \overline{A \oplus B \oplus C \oplus D}$$

$$\Rightarrow D^o -$$

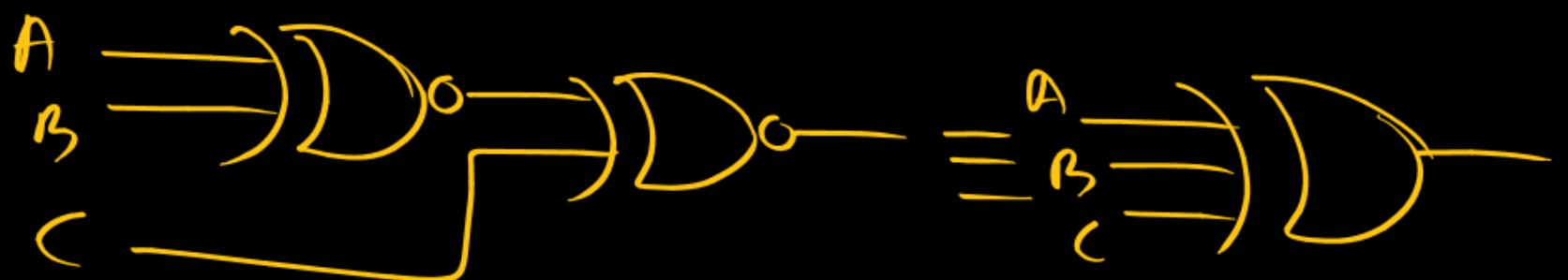

31 Oct

XNOR GATE



A B C

A ⊕ B ⊕ C

(A ⊕ B) ⊕ C

0 0 0

0

① 0 0 1

1

② 0 1 0

1

3 0 1 1

0

④ 1 0 0

1

5 1 0 1

0

6 1 1 0

0

7 1 1 1

1

$$\begin{aligned}(A \oplus B) \oplus C &= \sum m(1, 2, 4, 7) \\ &= A \oplus B \oplus C\end{aligned}$$

Even Variable X-NOR

$$A \oplus B = \overline{A \oplus B}$$

$$A \oplus B \oplus C \oplus D = \overline{A \oplus B \oplus C \oplus D}$$

Bind.



Output will be high when
Even no. of inputs are high.

Odd Variables X-NOR

$$(A \oplus B) \oplus C = A \oplus B \oplus C$$

Output will be high when
Odd no. of 1's are present in
the inputs.


Q1. The Boolean function given below:

$$f(A, B) = A \oplus B \oplus AB = A + B$$

which statement is/are correct?

OR

A, C

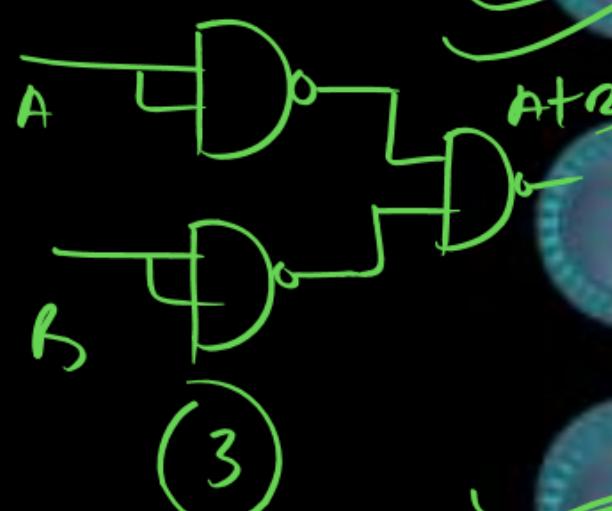

A It is a OR GATE

B It is a NAND GATE

③ B It requires 3 NAND gate to implement the function

B It required 2 NAND gates to implement the function

$$f = A \oplus B \oplus AB$$

$$\Rightarrow A \oplus B = X$$

$$= X \oplus AB$$

$$= \bar{X} \cdot AB + X \cdot \bar{AB}$$

$$= \overline{A \oplus B} \cdot AB + (A \oplus B) \cdot \bar{AB}$$

$$= (A \oplus B) \cdot AB + (A \oplus B) \bar{AB}$$

$$= (\bar{A}\bar{B} + AB)AB + (\bar{A}B + A\bar{B})(\bar{A} + \bar{B}) = (A + B)(B + \bar{B})$$

$$\bar{A}A = 0$$

$$\begin{aligned} &= \cancel{\bar{A}\bar{B}} \cdot AB + \cancel{AB} \cdot \bar{A}B + \cancel{\bar{A}B} \cdot \bar{A} + \cancel{\bar{A}B} \cdot \bar{B} \\ &= 0 + AB + \bar{A}B + 0 + \bar{A}\bar{B} \\ &= AB + \bar{A}B \\ &= B(A + \bar{A}) + A\bar{B} \\ &= B + A\bar{B} \end{aligned}$$

$\circlearrowleft A + B$

$\circlearrowleft A + B$

Q2. Minimized expression will be $Y = A \oplus (A + B)$

A

$A \oplus B$

B

$A \odot B$

C

$\bar{A} \cdot B$

D

$A + B$



$$\begin{array}{c}
 A \oplus (A+B) \\
 \diagdown \quad \diagup \\
 A \oplus A + A \oplus B \\
 \diagup \quad \diagdown \\
 0 + A \oplus B \\
 \diagup \quad \diagdown \\
 A \oplus B
 \end{array}$$

$$= \underline{\underline{A \oplus (A+B)}}$$

.

$$\overline{A}(A+B) + A(\overline{A+B})$$

$$\overline{A} \cdot A + \overline{A}B + A(\overline{A} \cdot \overline{B})$$

$$0 + \overline{A}B + 0$$

$$= \underline{\underline{\overline{A}B}}$$

$$A \oplus (A + B) = A + B = X$$

$$A \oplus X$$

$$\frac{\overline{A}X + A\overline{X}}{\overline{A}(A+B) + A(\overline{A}+B)}$$

Q.3 If the output $y = 1$

Then correct input is/are -

$$\overbrace{A}^1 \quad \overbrace{B}^1$$


A 1111, 0000

B 1010, 0111

C 0101, 0101


D 1100, 1110

A, C

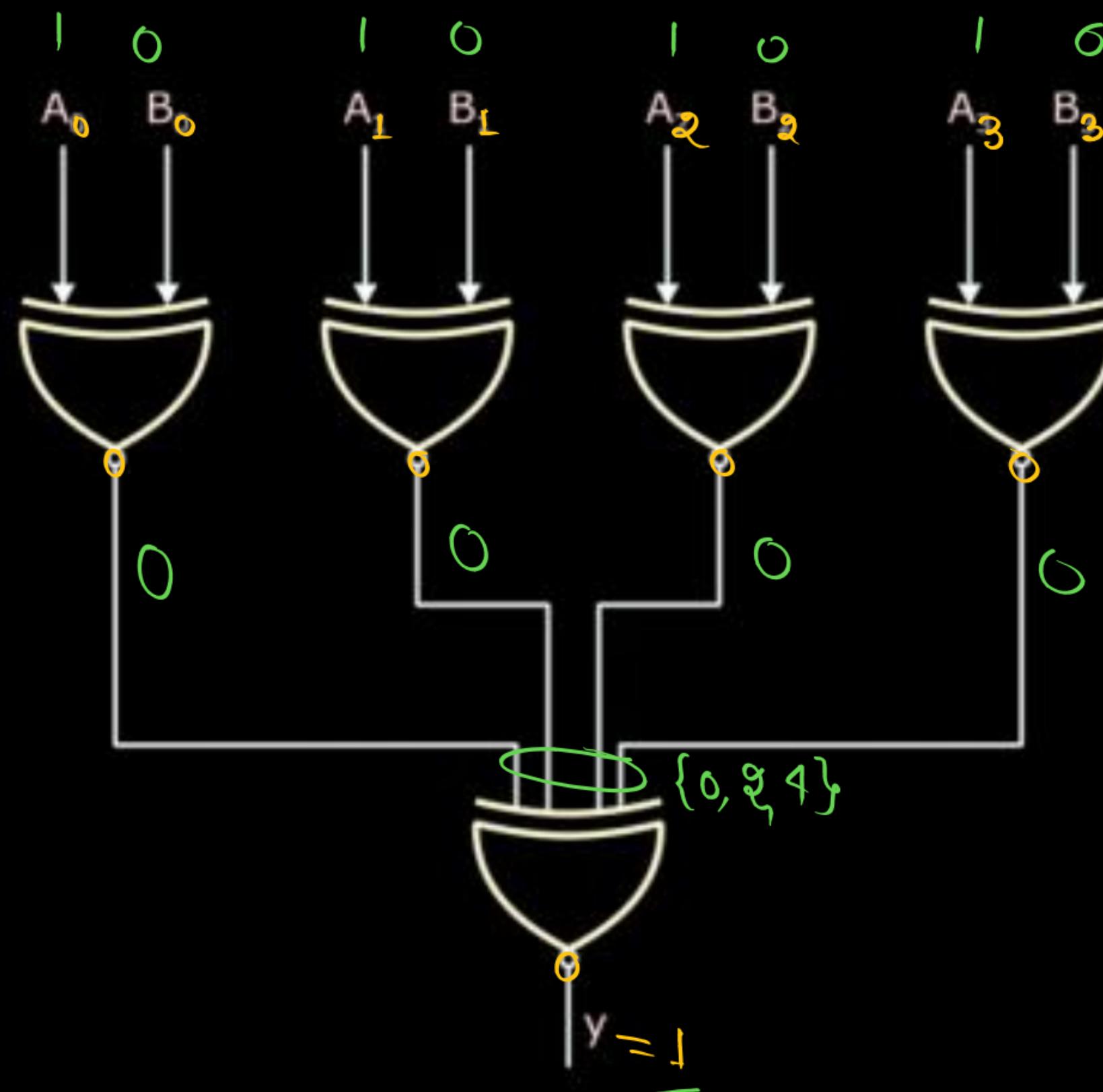



NOTE

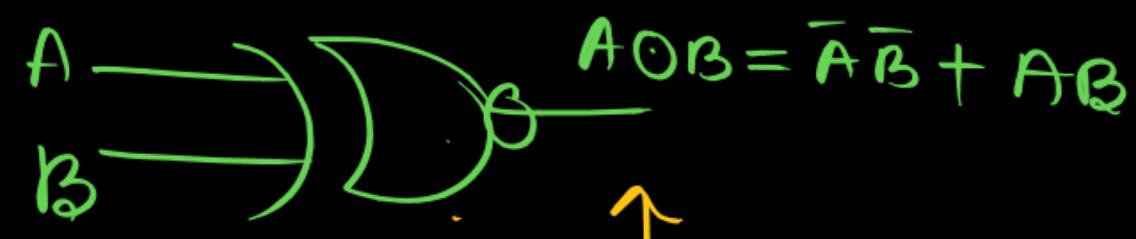

$$A \odot B = \bar{A} \bar{B} + AB$$

X-NOR



$$\bar{A} = X$$

$$\bar{A} \oplus B$$


$$X \oplus B$$

$$\bar{X}B + X\bar{B}$$

$$= \bar{A}B + \bar{A}\bar{B}$$

$$AB + \bar{A}\bar{B} = A \odot B$$
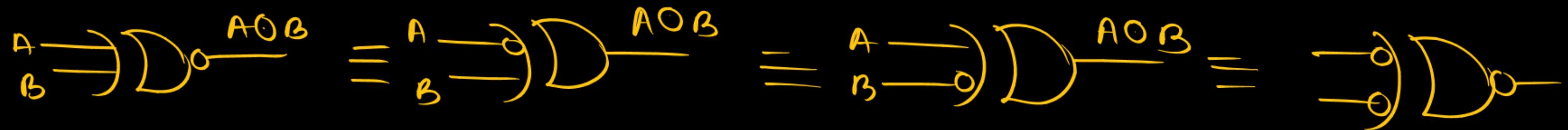
$$\# \quad A \odot B = \overline{A \oplus B} = \bar{A} \oplus B = A \oplus \bar{B} = \overline{\bar{A} \odot \bar{B}}$$




$$\# \quad A \oplus B = \overline{\bar{A} \odot B} = A \odot \bar{B} = \bar{A} \oplus \bar{B}$$



$$A \oplus B = X$$

$\stackrel{Q}{\equiv}$

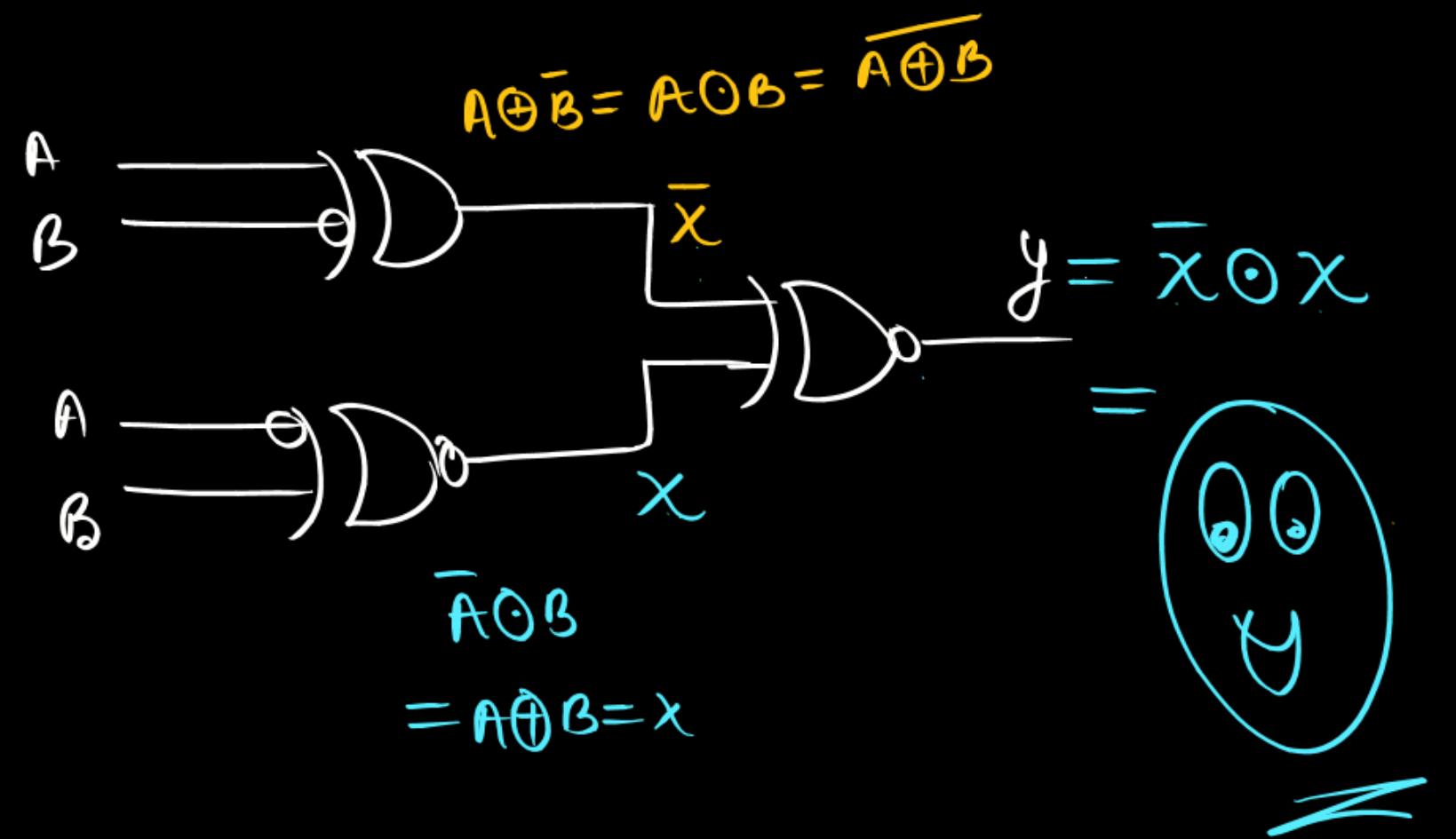




Q.4. Output y will be-

A 0

B 1

C $A \oplus B$

D $A \oplus B \oplus C \oplus D$

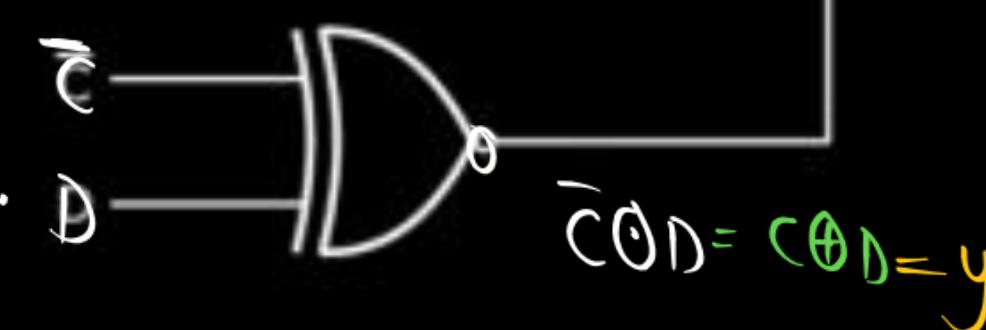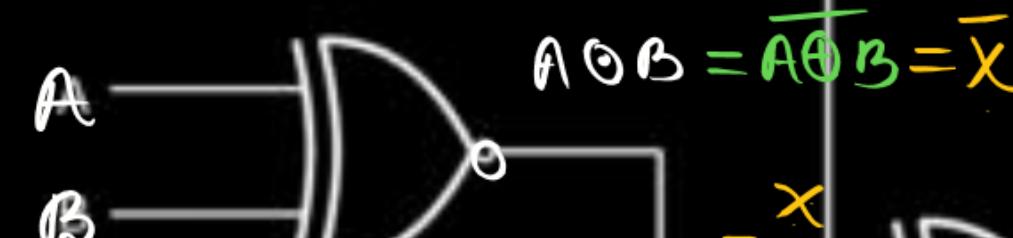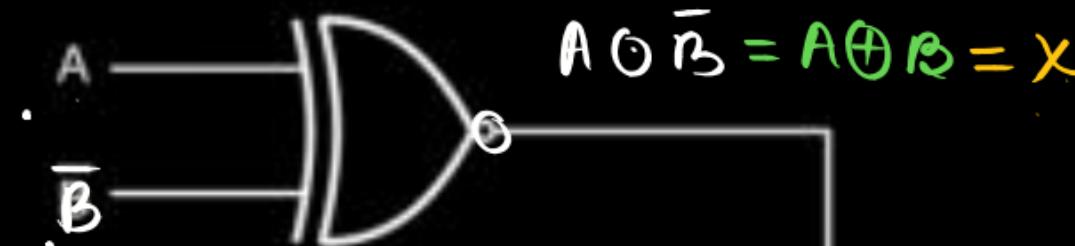

$$A \oplus B = x$$

$$C \oplus D = y$$

$$\begin{aligned} z &= x \oplus \bar{x} \oplus \bar{y} \oplus y \\ &= 0 \oplus 0 \oplus 0 \oplus 0 \\ &= 1 \end{aligned}$$

THANK
You! ☺



FOAM

Digital with Cf sin^o